
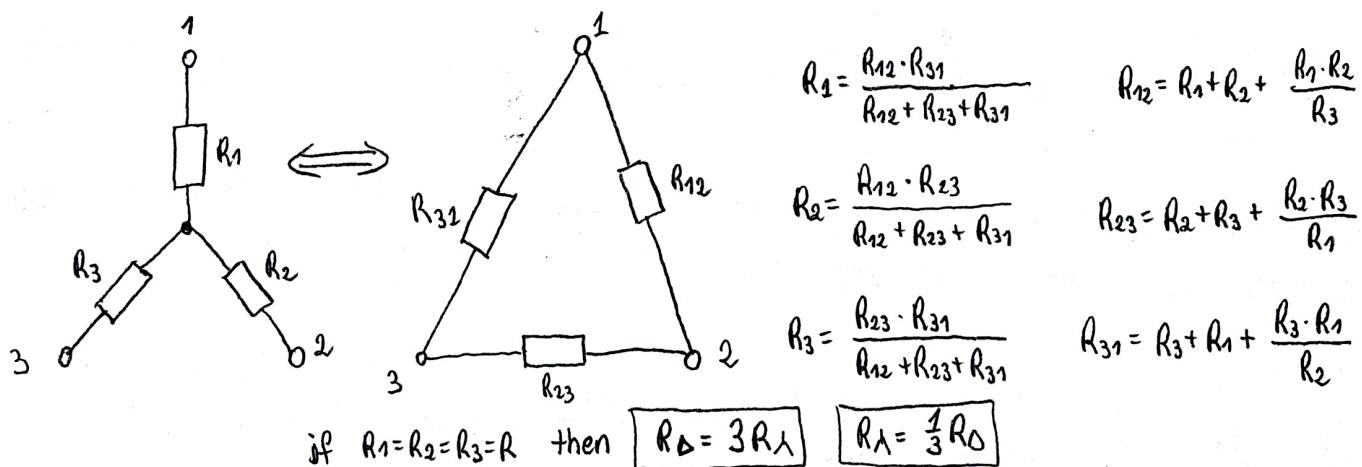


WYE-DELTA TRANSFORMATION

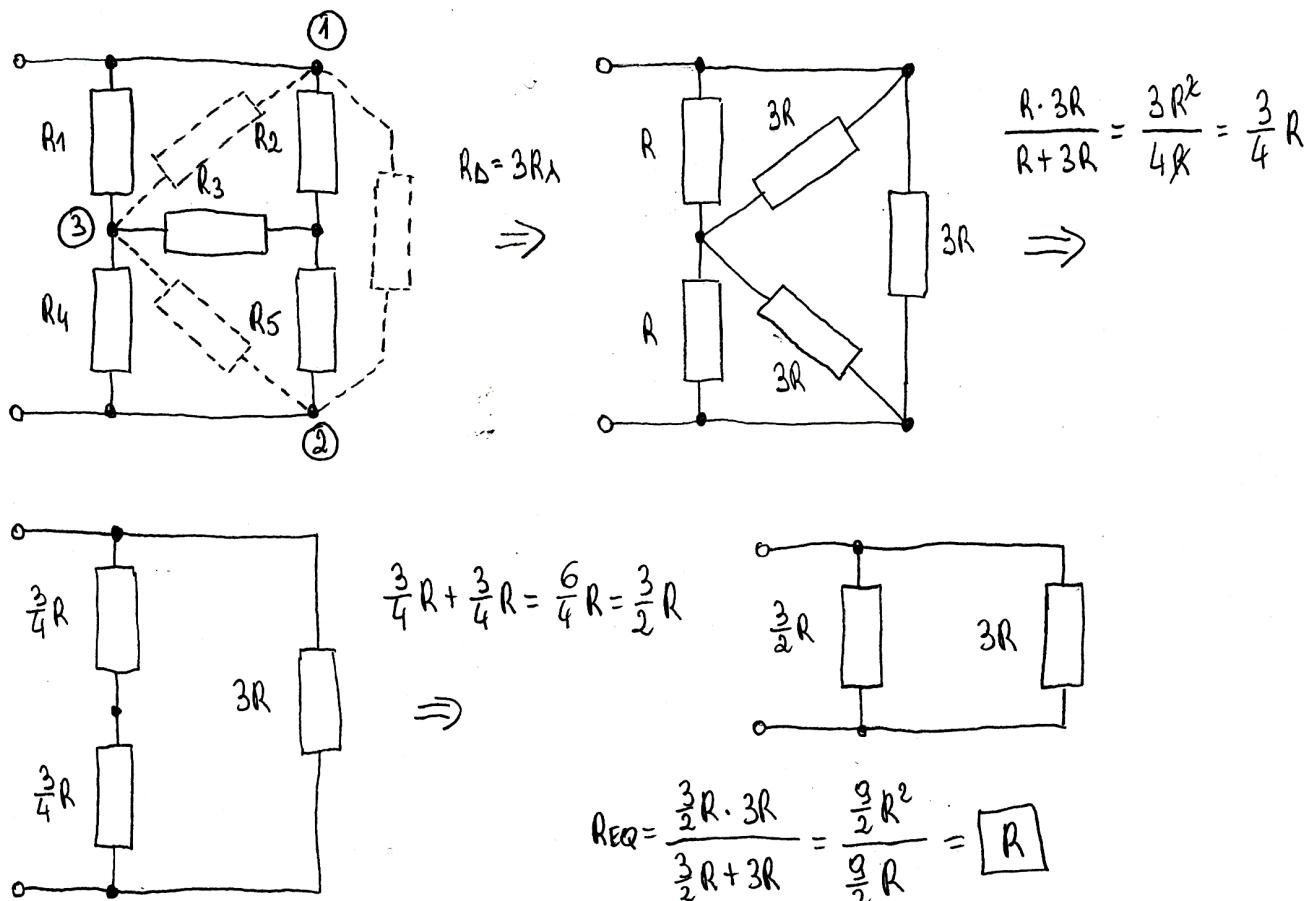


PROBLEM #1

Calculate the equivalent resistance of the circuit. $R_1 = R_2 = R_3 = R_4 = R_5 = R$




OHM'S LAW

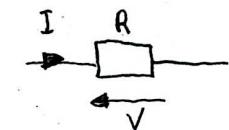


* for given resistance, the current is directly proportional to voltage

$$I = \frac{V}{R} \text{ or } V = R \cdot I \text{ or } R = \frac{V}{I}$$

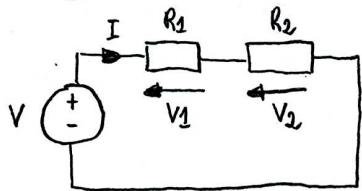* the simplest method to memorize Ohm's law is to use pyramid



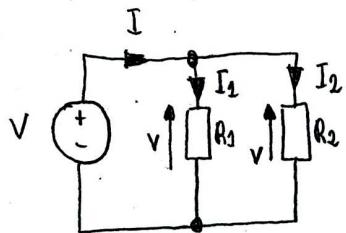
$$I = \frac{V}{R_1 + R_2} \quad V_1 = I \cdot R_1 \quad V_2 = I \cdot R_2 \quad R_1 \neq R_2 \rightarrow V_1 \neq V_2$$



$$I_1 = \frac{V}{R_1} \quad I_2 = \frac{V}{R_2} \quad I = I_1 + I_2$$

KCL - KIRCHHOFF'S CURRENT LAW

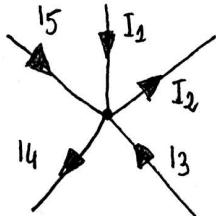

* the algebraic sum of the currents in a node is zero

$$\sum_k I_k = 0 \quad I_1 - I_2 + I_3 - I_4 + I_5 = 0$$

* if the current direction is into the node, we assign a positive sign to this current in an algebraic sum


* if the current direction is away from the node, we assign a negative sign to this current in an algebraic sum

* the sum of currents entering a node equals the sum of the currents leaving the node

$$I_1 + I_3 + I_5 = I_2 + I_4$$

* the algebraic sum of the currents entering a node is zero at every instant

KVL - KIRCHHOFF'S VOLTAGE LAW

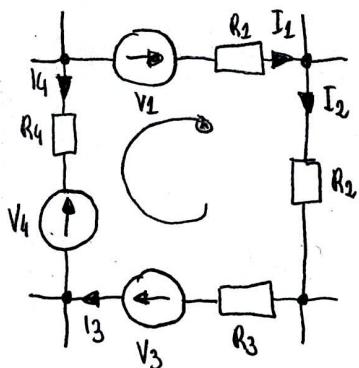

* the algebraic sum of all the voltages around a loop is 0 (zero)


$$V_1 - R_1 \cdot I_1 - R_2 \cdot I_2 - R_3 \cdot I_3 + V_3 + V_4 + I_4 \cdot R_4 = 0$$

* in any complete electrical circuits, the algebraic sum of applied voltages must equal the algebraic sum of voltage drops

PROBLEM #2

Calculate the voltage drops and currents in the branches of the circuit shown in the figure. $E = 12V$, $R_1 = 1\text{ k}\Omega$, $R_2 = 5\text{ k}\Omega$, $R_3 = 10\text{ k}\Omega$.

a)

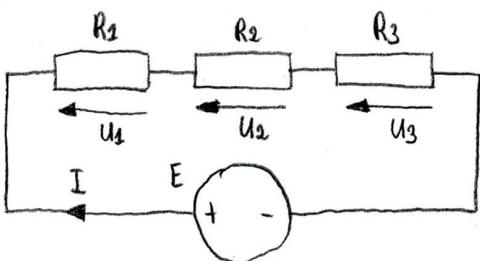

$$I = \frac{E}{R_1 + R_2 + R_3} = \frac{12}{1000 + 5000 + 10000} = \frac{12}{16000} = 0.75\text{ mA}$$


$$U_1 = R_1 \cdot I = 1000 \cdot 0.75\text{ mA} = 0.75\text{ V}$$

$$U_2 = R_2 \cdot I = 5000 \cdot 0.75\text{ mA} = 3.75\text{ V}$$

$$U_3 = R_3 \cdot I = 10000 \cdot 0.75\text{ mA} = 7.5\text{ V}$$

$$U_1 + U_2 + U_3 = 0.75 + 3.75 + 7.5 = 12\text{ V} = E$$

b)

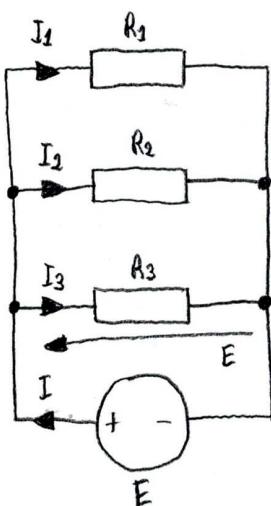

$$I_1 = \frac{E}{R_1} = \frac{12}{1000} = 12\text{ mA}$$

$$I_2 = \frac{E}{R_2} = \frac{12}{5000} = 2.4\text{ mA}$$


$$I_3 = \frac{E}{R_3} = \frac{12}{10000} = 1.2\text{ mA}$$

$$I = I_1 + I_2 + I_3 = 12\text{ mA} + 2.4\text{ mA} + 1.2\text{ mA} = 15.6\text{ mA}$$

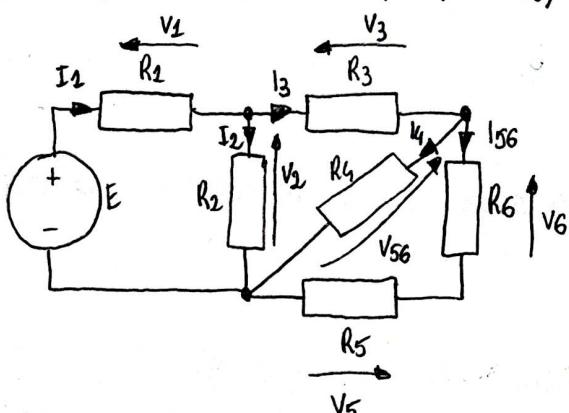PROBLEM #3

The voltage drop across R_6 is 30V. Calculate the voltage E , the current through a voltage source and the equivalent resistance of the circuit.

$$R_1 = 2.4\Omega, R_2 = 4\Omega, R_3 = 1\Omega, R_4 = 2.5\Omega, R_5 = 2\Omega, R_6 = 3\Omega.$$



$$V_6 = 30\text{ V}$$

$$I_{56} = \frac{V_6}{R_6} = \frac{30}{3} = 10\text{ A} \quad V_5 = R_5 \cdot I_{56} = 2 \cdot 10 = 20\text{ V}$$

$$V_{56} = V_5 + V_6 = 20 + 30 = 50\text{ V}$$

$$I_4 = \frac{V_{56}}{R_4} = \frac{50}{2.5} = 20\text{ A} \quad I_3 = I_4 + I_{56} = 20 + 10 = 30\text{ A}$$

$$V_3 = I_3 \cdot R_3 = 30 \cdot 1 = 30\text{ V} \quad V_2 = V_3 + V_{56} = 30 + 50 = 80\text{ V}$$

$$I_2 = \frac{V_2}{R_2} = \frac{80}{4} = 20\text{ A} \quad I_1 = I_2 + I_3 = 20 + 30 = \boxed{50\text{ A}}$$


$$V_1 = R_1 \cdot I_1 = 2.4 \cdot 50 = 120\text{ V}$$

$$E = V_1 + V_2 = 120 + 80 = \boxed{200\text{ V}}$$

$$R_{EQ} = \frac{E}{I_1} = \frac{200}{5} = \boxed{40\Omega}$$

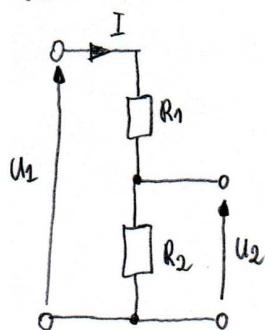PROBLEM #4

Calculate the voltage U_2 for the circuit shown in figure. $U_1 = 100V$, $R_1 = 70\Omega$, $R_2 = 30\Omega$.



$$I = \frac{U_1}{R_1 + R_2} = \frac{100}{70 + 30} = \frac{100}{100} = 1 \text{ A}$$

$$U_2 = R_2 \cdot I = 30 \cdot 1 = 30 \text{ V}$$


$$U_2 = \frac{R_2}{R_1 + R_2} U_1$$

$$U_2 = \frac{30}{70 + 30} \cdot 100 = 30 \text{ V}$$

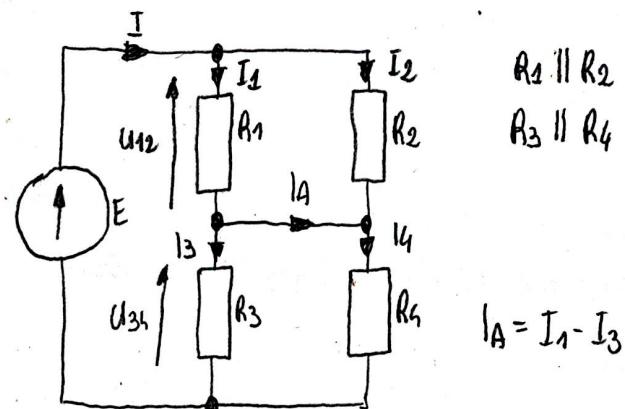PROBLEM #5

Calculate the current I_A in the circuit presented in the figure.


$E = 120V$, $R_1 = 10\Omega$, $R_2 = 15\Omega$, $R_3 = 60\Omega$, $R_4 = 40\Omega$



$$R_1 \parallel R_2$$

$$R_3 \parallel R_4$$

$$I_A = I_1 - I_3$$

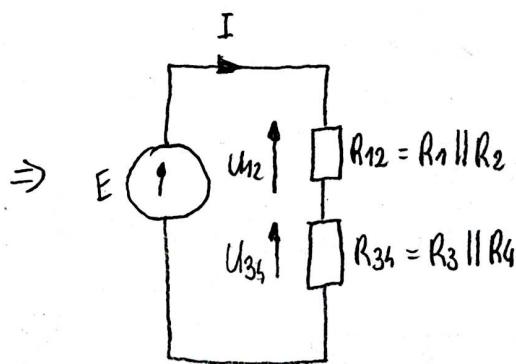

$$R_{12} = \frac{R_1 \cdot R_2}{R_1 + R_2} = \frac{10 \cdot 15}{10 + 15} = \frac{150}{25} = 6 \Omega$$

$$I = \frac{E}{R_{12} + R_{34}} = \frac{120}{6 + 24} = \frac{120}{30} = 4 \text{ A}$$

$$R_{34} = \frac{R_3 \cdot R_4}{R_3 + R_4} = \frac{60 \cdot 40}{60 + 40} = \frac{2400}{100} = 24 \Omega$$

$$U_{12} = R_{12} \cdot I = 6 \cdot 4 = 24 \text{ V}$$

$$I_1 = \frac{U_{12}}{R_1} = \frac{24}{10} = 2.4 \text{ A}$$

$$U_{34} = R_{34} \cdot I = 24 \cdot 4 = 96 \text{ V}$$

$$I_3 = \frac{U_{34}}{R_3} = \frac{96}{60} = 1.6 \text{ A}$$

$$I_A = I_1 - I_3 = 2.4 - 1.6 = 0.8 \text{ A}$$