


Module name: **Electrical Circuits 1**
Module ID: **IS-FEE-10070W**
Module type: **Class**
Semester: **winter 2024/2025**
Instructor: **Jarosław Forenc, j.forenc@pb.edu.pl**

Class 06 (18.11.2024)

1. Measure the internal resistance of a **9V** battery using the following method:
 - **Step 1:** Use a multimeter to measure the battery's voltage, **E**.
 - **Step 2:** Measure the actual resistance of a **R = 220 Ω** resistor with a multimeter. Connect this resistor in series with the battery and then measure the voltage **U** across the resistor.
 - **Step 3:** Calculate the battery's internal resistance, **R_{int}**, using the following formula:

$$R_{int} = R \cdot \frac{E - U}{U}$$

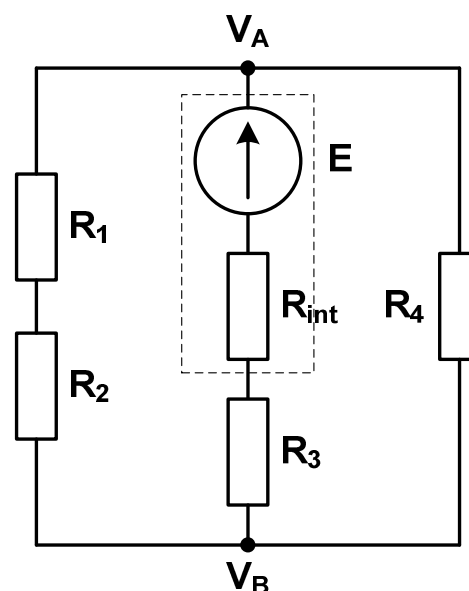2. Measure the actual resistances of the resistors:
 $R_1 = 220 \Omega$, $R_2 = 100 \Omega$, $R_3 = 470 \Omega$, $R_4 = 470 \Omega$.
Using these measured values and **9V** battery, calculate the potential **V_A** with the **Node-Voltage Method**. Consider two cases: a) $R_{int} = 0 \Omega$, and b) R_{int} as the value calculated in problem no. 1.
Build the circuit shown in the figure. Using a multimeter, measure the voltage between points **V_A** and **V_B**, and compare the measured results with the calculated values.




3. Calculate the power dissipated in resistor R_5 using **Thevenin's theorem**.

$$R_1 = 2 \Omega, R_2 = 3 \Omega, R_3 = 4 \Omega,$$

$$R_4 = 2 \Omega, R_5 = 6 \Omega,$$

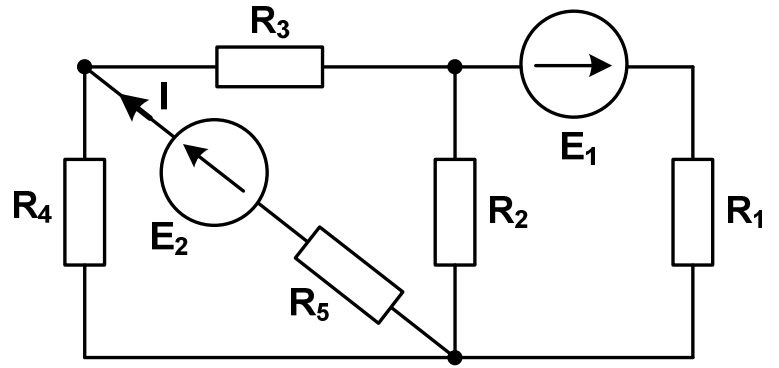
$$E_1 = 14 \text{ V}, E_2 = 20 \text{ V}.$$



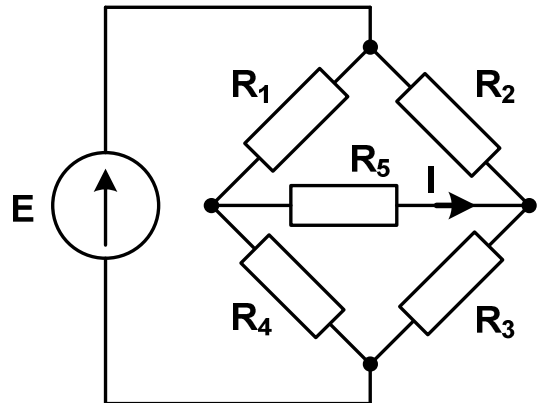4. What should be the minimum power rating of resistor R_5 in the circuit shown in the figure? Use **Thevenin's theorem**.

$$R_1 = 4 \Omega, R_2 = 12 \Omega, R_3 = 4 \Omega,$$

$$R_4 = 4 \Omega, R_5 = 1 \Omega, E = 12 \text{ V}$$



5. Use **Thevenin's theorem** to determine the voltage source E_5 that will make the current through R_3 equal to 0 A .

$$R_1 = R_4 = 1 \Omega, R_2 = R_3 = 2 \Omega,$$

$$J_4 = 1 \text{ A}, E_1 = 3 \text{ V}$$

