

Module name: **Electrical Circuits 1**

Module ID: **IS-FEE-10070W**

Module type: **Class**


Semester: **winter 2024/2025**

Instructor: **Jarosław Forenc, [j.forenc@pb.edu.pl](mailto:j.forenc@pb.edu.pl)**
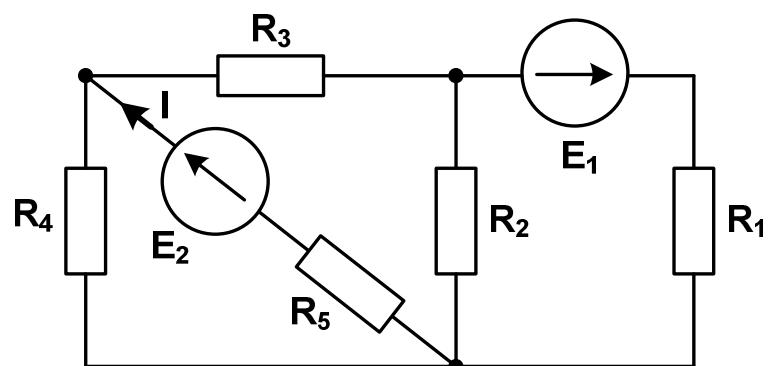
### Class 08 (02.12.2024)


- Calculate the power dissipated in resistor  $R_5$  using **Thevenin's theorem**.

$$R_1 = 2 \Omega, R_2 = 3 \Omega, R_3 = 4 \Omega, \\ R_4 = 2 \Omega, R_5 = 6 \Omega, \\ E_1 = 14 \text{ V}, E_2 = 20 \text{ V}.$$




- What should be the minimum power rating of resistor  $R_5$  in the circuit shown in the figure?  
Use **Thevenin's theorem**.
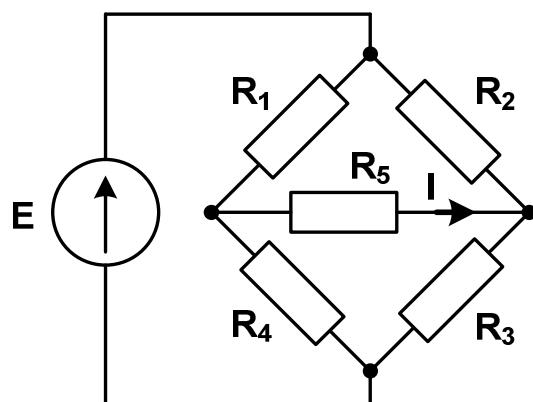
$$R_1 = 4 \Omega, R_2 = 12 \Omega, R_3 = 4 \Omega, \\ R_4 = 4 \Omega, R_5 = 1 \Omega, E = 12 \text{ V}$$



- Use **Thevenin's theorem** to determine the voltage source  $E_5$  that will make the current through  $R_3$  equal to 0 A.
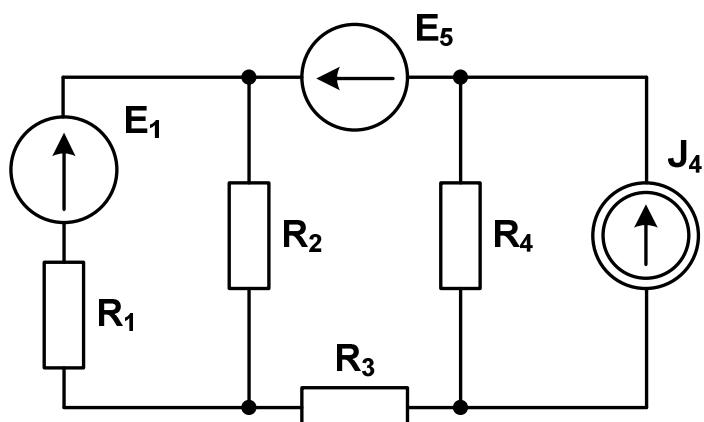
$$R_1 = R_4 = 1 \Omega, R_2 = R_3 = 2 \Omega, \\ J_4 = 1 \text{ A}, E_1 = 3 \text{ V}$$



4. Determine the phasor representation (the complex form) of the following signals.

- a)  $u_1(t) = 230\sqrt{2} \sin(314 \cdot t) V$       d)  $i_2(t) = \cos(314 \cdot t - 30^\circ) A$   
b)  $i_1(t) = 10 \sin(314 \cdot t - 45^\circ) A$       e)  $u_3(t) = 100 \sin(t) V$   
c)  $u_2(t) = 25 \cos(314 \cdot t) V$

5. Based on phasor representation, express the voltage and current signals as time functions in the form  $f(t) = F_m \sin(\omega t + \varphi)$ .

- a)  $\underline{U}_1 = 100e^{j30^\circ} V$       c)  $\underline{U}_2 = (20 + j45) V$   
b)  $\underline{I}_1 = e^{j90^\circ} A$       d)  $\underline{I}_2 = (5 - j5) A$