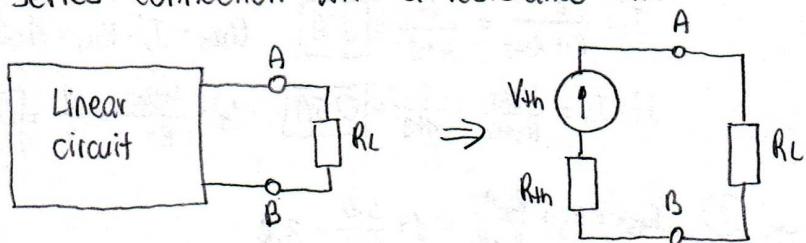


THEVENIN'S THEOREM




- * any linear circuit containing only voltage sources, current sources, resistances can be replaced at terminals A-B by an equivalent combination of a voltage source V_{th} in a series connection with a resistance R_{th}



V_{th} - the voltage obtained at terminals A-B of the circuit with terminals A-B open circuited

R_{th} - the resistance between terminals A-B when all ideals voltage sources are replaced by a short circuit and all current sources are replaced by an open circuit


PROBLEM #1

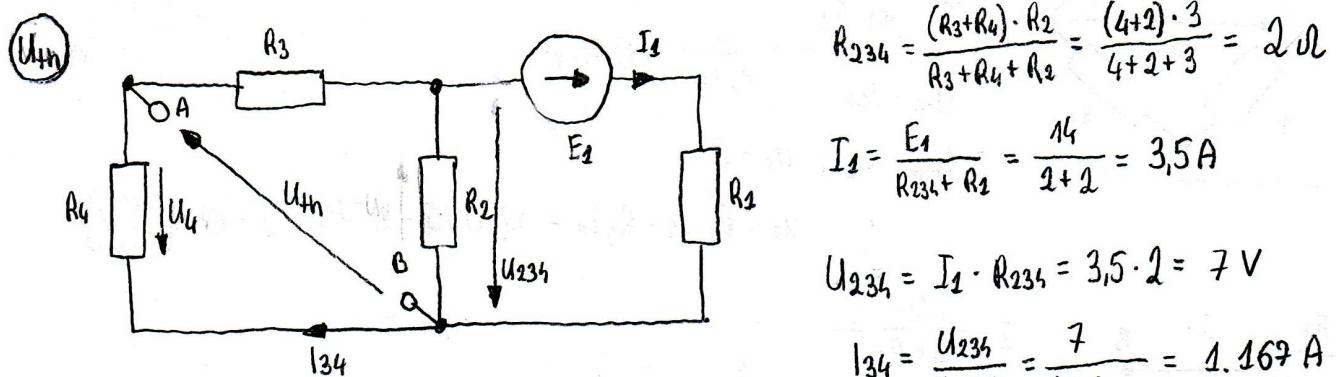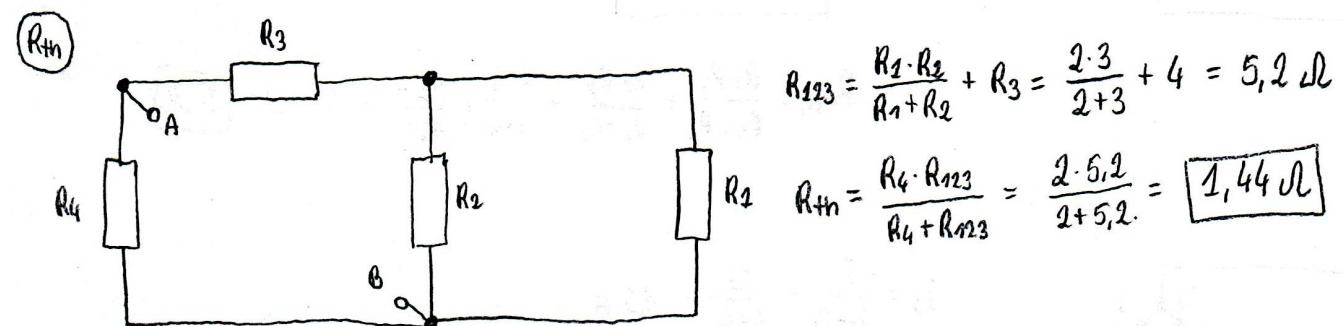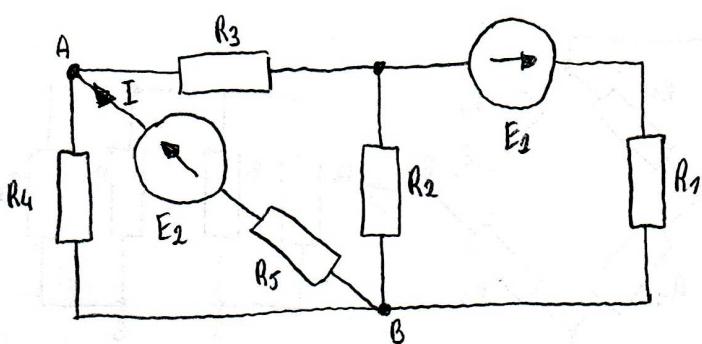

$$U_{234} = I_1 \cdot R_{234} = 3,5 \cdot 2 = 7 V$$

$$I_{34} = \frac{U_{234}}{R_3 + R_4} = \frac{7}{4+2} = 1,167 A$$
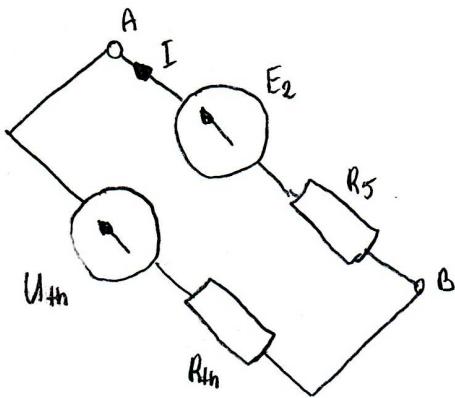
$$U_4 = I_{34} \cdot R_4 = 1,167 \cdot 2 = 2,33 V$$



KVL: $U_{th} + U_4 = 0$
 $U_{th} = -U_4 = \boxed{-2.33 \text{ V}}$



$$I = \frac{E_2 - U_{th}}{R_5 + R_{th}} = \frac{20 - (-2.33)}{6 + 1.44} = \frac{22.33}{7.44} = \boxed{3 \text{ A}}$$

$$P_5 = R_5 \cdot I^2 = 6 \cdot 3^2 = 6 \cdot 9 = \boxed{54 \text{ W}}$$

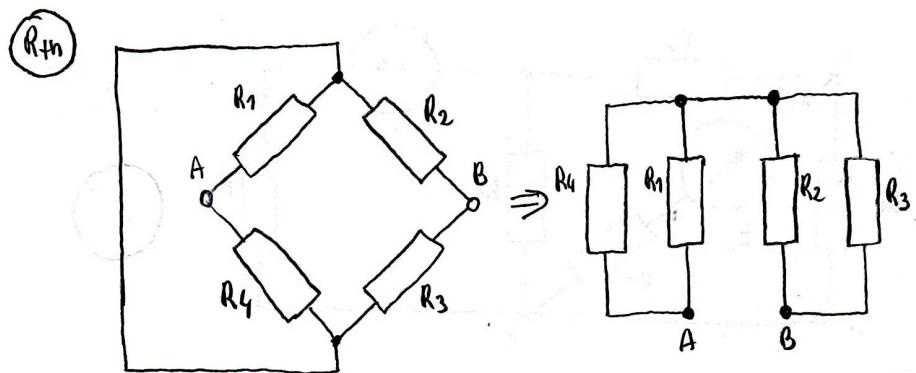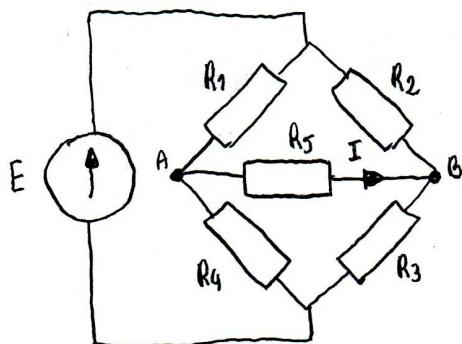
PROBLEM #2

What should be the minimum power rating of the resistor R_5 in the circuit shown in the figure?
 Use Thevenin's theorem.

$$R_1 = 4 \Omega, R_2 = 12 \Omega, R_3 = 4 \Omega, R_4 = 4 \Omega, R_5 = 1 \Omega, E = 12 \text{ V}$$


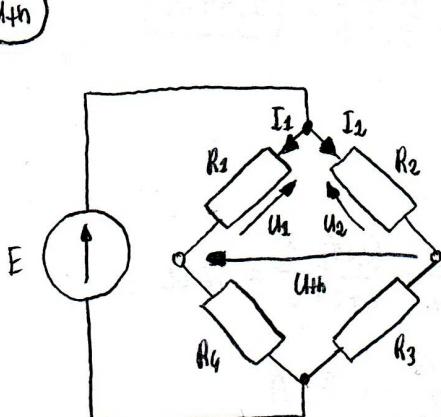
$$R_{th} = \frac{R_1 \cdot R_4}{R_1 + R_4} + \frac{R_2 \cdot R_3}{R_2 + R_3} = \frac{4 \cdot 4}{4+4} + \frac{12 \cdot 4}{12+4} = 2 + 3 = \boxed{5 \Omega}$$




$$I_1 = \frac{E}{R_1 + R_4} = \frac{12}{4+4} = 1.5 \text{ A}$$

$$I_2 = \frac{E}{R_2 + R_3} = \frac{12}{12+4} = 0.75 \text{ A}$$

$$U_{th} + U_1 - U_2 = 0$$
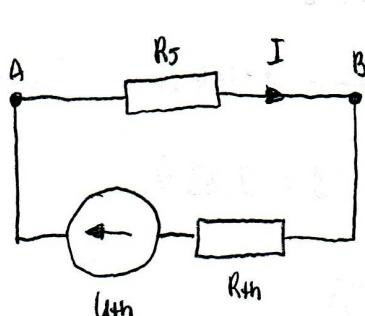
$$U_{th} = U_2 - U_1 = R_2 \cdot I_2 - R_1 \cdot I_1 = 12 \cdot 0.75 - 4 \cdot 1.5 = 9 - 6 = \boxed{3 \text{ V}}$$





$$I = \frac{U_{th}}{R_{th} + R_5} = \frac{3}{5+1} = \boxed{0.5 \text{ A}}$$


$$P_{min} = R_5 \cdot I^2 = 1 \cdot 0.5^2 = \boxed{0.25 \text{ W}}$$

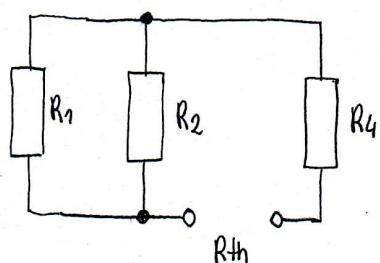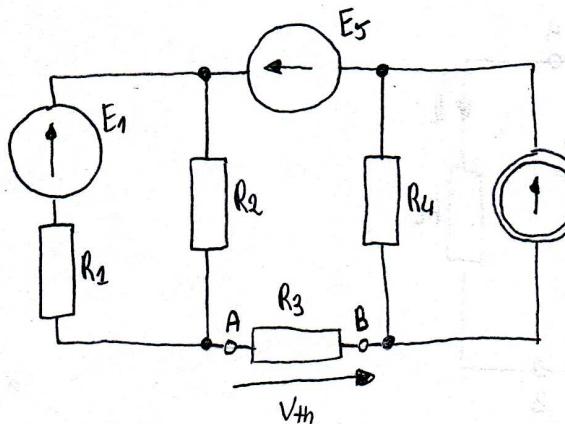PROBLEM #3

Use Thevenin's theorem to determine the voltage source E_5 that will make the current through R_3 equal to 0A. $R_1 = R_4 = 1\ \Omega$, $R_2 = R_3 = 2\ \Omega$, $J_4 = 1\ A$, $E_1 = 3\ V$.


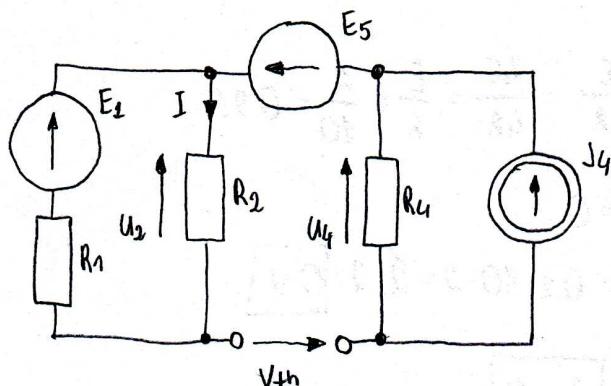
$$R_{th} = \frac{R_1 \cdot R_2}{R_1 + R_2} + R_4 = \frac{1 \cdot 2}{1+2} + 1 = \frac{2}{3} + 1 = \frac{5}{3} \Omega$$




$$I = \frac{E_1}{R_1 + R_2} \quad U_2 = I \cdot R_2 = \frac{E_1 \cdot R_2}{R_1 + R_2} = \frac{2 \cdot 2}{1+2} = \frac{6}{3} = 2\ V$$

$$U_4 = R_4 \cdot J_4 = 1 \cdot 1 = 1\ V$$

$$V_{th} + U_4 + E_5 - U_2 = 0$$
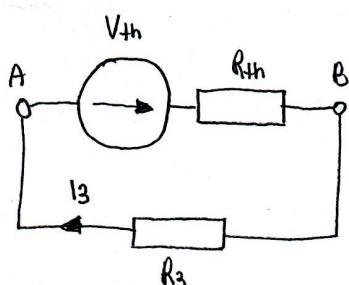
$$V_{th} = U_2 - U_4 - E_5 = 2 - 1 - E_5 = 1 - E_5$$




$$I_3 = \frac{V_{th}}{R_{th} + R_3} = 0$$

$$\frac{1 - E_5}{R_{th} + R_3} = 0 \Rightarrow 1 - E_5 = 0 \rightarrow E_5 = 1\ V$$

A SINE WAVE
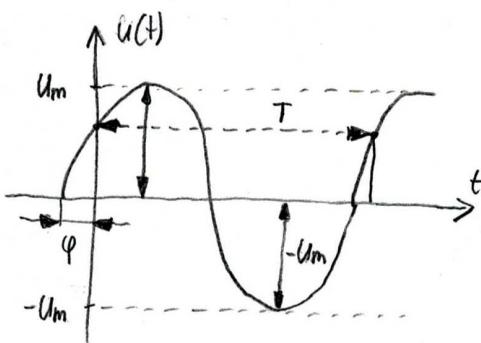
$$u(t) = U_m \cdot \sin(\omega t + \varphi)$$



$u(t)$ - the instantaneous value of the signal

U_m - the maximum value of the signal

the peak value of the signal (amplitude)

the letter symbol for the peak value of an alternating source voltage is U_m (m for maximum)

T - period [s]

f - frequency [Hz] - the inverse of T , $f = \frac{1}{T}$

ω - angular velocity [rad/s] - radian per second

$$\omega = 2\pi f = \frac{2\pi}{T}$$

φ - phase angle or phase shift

U_{rms} - rms value (root-mean square), the effective value

$$U_{rms} = \sqrt{\frac{1}{T} \int_0^T u^2(t) dt}$$

$U_{rms} = \frac{U_m}{\sqrt{2}}$ the rms value of a sine wave of voltage is $1/\sqrt{2}$ of the peak value

COMPLEX NUMBERS


* complex number can be represented in the form:

- algebraic form (rectangular form): $z = a + jb$
- trigonometric form (polar form): $z = r(\cos \varphi + j \sin \varphi)$
- exponential form: $z = r \cdot e^{j\varphi}$

* algebraic (rectangular) form of complex number

$$z = a + jb$$

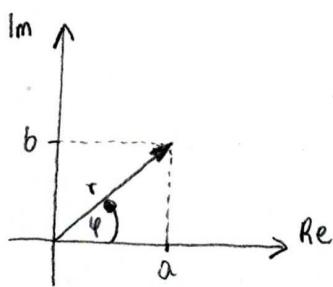- complex numbers have a real part and an imaginary part
- a - real part ($\operatorname{Re}(z)$) of complex number, $\operatorname{Re}[z]$
- b - imaginary part of complex number, $\operatorname{Im}[z]$
- j - imaginary unit (number) $j^2 = -1$, $j = \sqrt{-1}$ - square root of minus one
- graphical representation of complex number



- we use horizontal axis for the real part and vertical axis for the imaginary part

- $r = |z| = \sqrt{a^2 + b^2}$ - the absolute value of complex number (modulus)

- φ - argument of complex number

$$\varphi = \arctan \frac{b}{a}$$

* trigonometric (polar) form of complex number

$$\underline{z} = r(\cos \varphi + j \sin \varphi)$$

$$r = \sqrt{a^2 + b^2} \quad \varphi = \arctg \frac{b}{a}$$


$$\underline{z} = a + jb = r \left(\underbrace{\frac{a}{r}}_{\cos \varphi} + j \underbrace{\frac{b}{r}}_{\sin \varphi} \right) = r (\cos \varphi + j \sin \varphi)$$

* exponential form of complex number

$$\underline{z} = r e^{j\varphi} \quad e^{j\varphi} = \cos \varphi + j \sin \varphi$$

* complex conjugate of \underline{z}
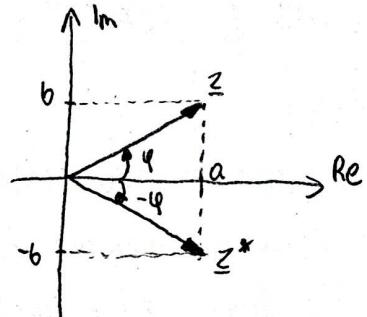
$$\left. \begin{array}{l} \underline{z} = a + jb \\ \underline{z} = r(\cos \varphi + j \sin \varphi) \\ \underline{z} = r e^{j\varphi} \end{array} \right\} \Rightarrow \begin{array}{l} \underline{z}^* = a - jb \\ \underline{z}^* = r(\cos \varphi - j \sin \varphi) \\ \underline{z}^* = r e^{-j\varphi} \end{array}$$



BASIC OPERATIONS ON COMPLEX NUMBERS

$$\underline{z}_1 = a_1 + jb_1 \quad \underline{z}_2 = a_2 + jb_2$$

* sum of complex numbers


$$\underline{z} = \underline{z}_1 + \underline{z}_2 = a_1 + jb_1 + a_2 + jb_2 = \underbrace{a_1 + a_2}_{\text{Re}} + j \underbrace{(b_1 + b_2)}_{\text{Im}}$$

we can add complex numbers graphically ['graefikl[]']

$$\underline{z}_1 = 3 + j2$$

$$\underline{z}_2 = 1 - j4$$
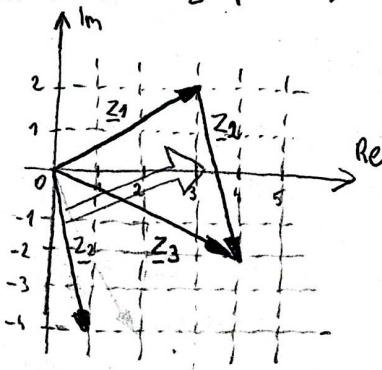
$$\underline{z}_1 + \underline{z}_2 = 4 - j2$$



o we move vector \underline{z}_2 to the end of vector \underline{z}_1

* difference of complex numbers

$$\underline{z} = \underline{z}_1 - \underline{z}_2 = \underbrace{a_1 - a_2}_{\text{Re}} + j \underbrace{(b_1 - b_2)}_{\text{Im}}$$

* product of complex number

$$\underline{z} = \underline{z}_1 * \underline{z}_2 = (a_1 + jb_1) * (a_2 + jb_2) = \underbrace{a_1 \cdot a_2 - b_1 \cdot b_2}_{\text{Re}} + j \underbrace{(a_1 b_2 + b_1 a_2)}_{\text{Im}}$$

* division of complex number

$$\underline{Z} = \frac{\underline{Z}_1}{\underline{Z}_2} = \frac{a_1 + j b_1}{a_2 + j b_2} = \frac{(a_1 + j b_1) \cdot (a_2 - j b_2)}{(a_2 + j b_2) \cdot (a_2 - j b_2)} = \underbrace{\frac{a_1 \cdot a_2 + b_1 \cdot b_2}{a_2^2 + b_2^2}}_{\text{Re}} + j \underbrace{\frac{b_1 \cdot a_2 - a_1 \cdot b_2}{a_2^2 + b_2^2}}_{\text{Im}}$$

□ We multiply numerator and denominator by the conjugate of the denominator

PROBLEM #4

Find the complex form (phasor representation) of the following signals.

a) $u_1(t) = 230\sqrt{2} \sin(314 \cdot t) V$

$$u(t) = U_m \cdot \sin(\omega t + \varphi) \rightarrow \underline{U} = U (\cos \varphi + j \sin \varphi) \quad U_m = 230\sqrt{2} \quad \varphi = 0^\circ \quad U = \frac{U_m}{\sqrt{2}} = \frac{230\sqrt{2}}{\sqrt{2}} = 230$$

$$\underline{U}_1 = 230 (\cos 0^\circ + j \sin 0^\circ) = 230 (1+j0) = \boxed{230 V}$$

b) $i_1(t) = 10 \sin(314t - 45^\circ) A \quad \varphi = -45^\circ$

$$\underline{I}_1 = \frac{10}{\sqrt{2}} \left(\cos(-45^\circ) + j \sin(-45^\circ) \right) = \frac{10}{\sqrt{2}} \left(\frac{\sqrt{2}}{2} + j \frac{-\sqrt{2}}{2} \right) = \frac{10\sqrt{2}}{\sqrt{2} \cdot 2} - j \frac{10\sqrt{2}}{\sqrt{2} \cdot 2} = \boxed{5-j5 A}$$

c) $u_2(t) = 25 \cos(314 \cdot t) V \quad \cos \varphi = \sin(\varphi + 90^\circ)$

$$u_2(t) = 25 \sin(314 \cdot t + 90^\circ) V$$

$$\underline{U}_2 = \frac{25}{\sqrt{2}} \left(\cos 90^\circ + j \sin 90^\circ \right) = j \frac{25}{\sqrt{2}} = j \frac{25\sqrt{2}}{2} = \boxed{j 17.68 V}$$

d) $i_2(t) = \cos(314 \cdot t - 30^\circ) A \quad \cos(\alpha) = \sin(\alpha + 90^\circ)$

$$i_2(t) = \sin(314 \cdot t - 30^\circ + 90^\circ) A$$

$$i_2(t) = \sin(314 \cdot t + 60^\circ) A$$

$$\underline{I}_2 = \frac{1}{\sqrt{2}} \left(\cos 60^\circ + j \sin 60^\circ \right) = \frac{1}{\sqrt{2}} \left(\frac{1}{2} + j \frac{\sqrt{3}}{2} \right) = \frac{1}{2\sqrt{2}} + j \frac{\sqrt{3}}{2\sqrt{2}} = \frac{\sqrt{2}}{4} + j \frac{\sqrt{6}}{4} = \boxed{(0.353 + j 0.612) A}$$

e) $u_3(t) = 100 \sin(t) V$

$$\underline{U}_3 = \frac{100}{\sqrt{2}} \left(\cos 0^\circ + j \sin 0^\circ \right) = \frac{100}{\sqrt{2}} = \boxed{70.71 V}$$