

# ELECTRICAL CIRCUITS 1 - CLASS NO. 09 (09.12.2024)

## PROBLEM #1

Based on phasor representation, express the voltage and current signals as time functions in the form  $f(t) = F_m \sin(\omega t + \varphi)$ .

a)  $\underline{U}_1 = 100e^{j30^\circ} V$

$$u(t) = U_m \sin(\omega t + \varphi) \quad U_m = 100\sqrt{2} \quad \varphi = 30^\circ$$

$$\underline{u}_1(t) = 100\sqrt{2} \sin(\omega t + 30^\circ) V$$

b)  $\underline{I}_2 = e^{j80^\circ} A$

$$I_m = \sqrt{2} \quad \varphi = 80^\circ$$

$$\underline{i}_2(t) = \sqrt{2} \sin(\omega t + 80^\circ)$$

c)  $\underline{U}_2 = (20 + j45) V$

$$U_m = \sqrt{20^2 + 45^2} \cdot \sqrt{2} = 48.24\sqrt{2}$$

$$\varphi = \arctan \frac{45}{20} = 66.037^\circ$$

$$\underline{u}_2(t) = 48.24\sqrt{2} \sin(\omega t + 66.037^\circ) V$$

d)  $\underline{I}_2 = (5 - j5) A$


$$I_m = \sqrt{2} \cdot \sqrt{5^2 + 5^2} = \sqrt{2} \cdot \sqrt{25+25} = \sqrt{100} = 10$$

$$\varphi = \arctan \frac{-5}{5} = -45^\circ$$

$$\underline{i}_2(t) = 10 \sin(\omega t - 45^\circ) A$$

## RESISTOR

\* Resistor, Resistance [ $\Omega$ ]

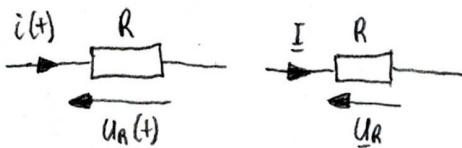


R - resistance [ $\Omega$ ]

G - conductance [S]

Z - impedance

Y - admittance

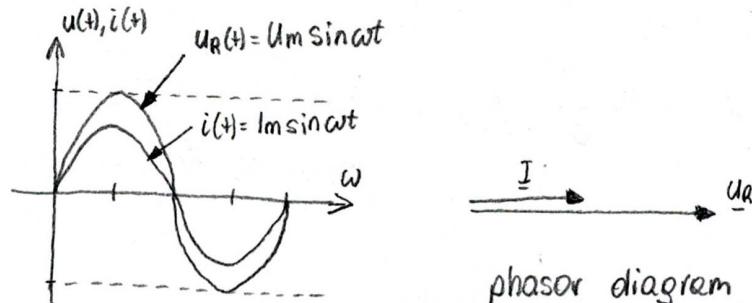


\* the voltage across a resistance is in phase with the current

$$G = \frac{1}{R} \quad Z = R \quad Y = \frac{1}{Z} = \frac{1}{R} = G \quad \Psi_u = \Psi_i$$


## CAPACITOR

\* Capacitor, Capacitance [F]

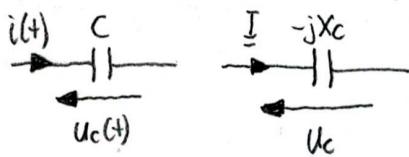

$X_C$  - capacitive reactance [ $\Omega$ ]

$B_C$  - capacitive susceptance [S]

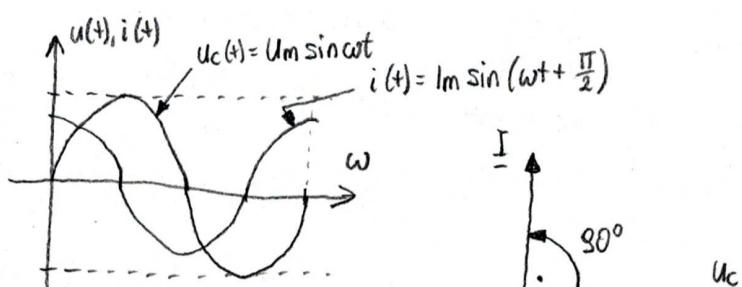

$$X_C = \frac{1}{\omega C} \quad \omega = 2\pi f$$

$$Z = -jX_C \quad Y = \frac{1}{-jX_C} = jB_C$$

$$u_C(t) = \frac{1}{C} \int i(t) dt \quad u_C = -jX_C \cdot I$$


phasor diagram

\* the voltage across a capacitor lags the current by  $90^\circ$  ( $\frac{\pi}{2}$ )

$$\Psi_i = \Psi_u + 90^\circ$$



## INDUCTOR

\* Inductor, Inductance [H]

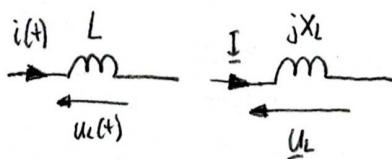

$X_L$  - inductive reactance [ $\Omega$ ]

$B_L$  - inductive susceptance [s]

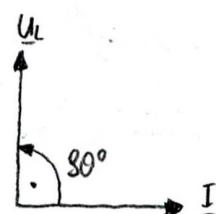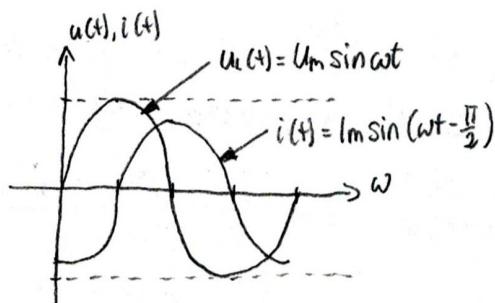

$$X_L = \omega L \quad \omega = 2\pi f$$


$$\underline{Z} = jX_L \quad Y = \frac{1}{\underline{Z}} = \frac{1}{jX_L} = -jB_L$$

$$U_L(t) = L \frac{di(t)}{dt} \quad U_L = jX_L \cdot I$$

\* the voltage across an inductor leads the current by  $90^\circ$  ( $\frac{\pi}{2}$ )

$$\Psi_u = \Psi_i + 90^\circ$$

## IMPEDANCE / ADMITTANCE

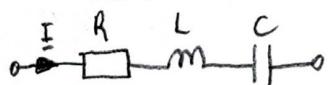


$$\underline{Z} = R + jX_L - jX_C \quad I = \frac{U}{\underline{Z}} = Y \cdot U$$

$$Y = \frac{1}{\underline{Z}}$$

$$|Z| = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\Phi = \arctan \frac{X_L - X_C}{R}$$

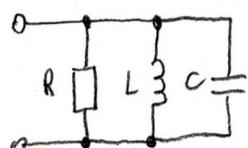


$$Y = G + jB_C - jB_L$$

$$I = Y \cdot U$$
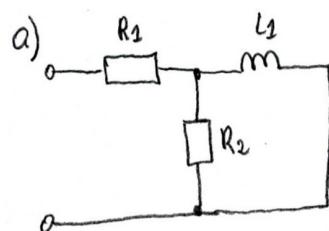
## PROBLEM #2

Find the equivalent impedance and admittance of circuits shown below.



$$R_1 = 5\Omega$$

$$R_2 = 2\Omega$$


$$L_1 = 100mH$$

$$f = 50\text{Hz}$$

$$X_{L1} = 2\pi f L_1 = 2 \cdot 3.14 \cdot 50 \cdot 0.1 = 31.4 \Omega$$

$$\underline{Z}_{eq} = R_1 + \frac{R_2 - jX_{L1}}{R_2 + jX_{L1}} = 5 + \frac{20 - j31.4}{20 + j31.4} = \boxed{19.2320 + j9.0604 \Omega}$$
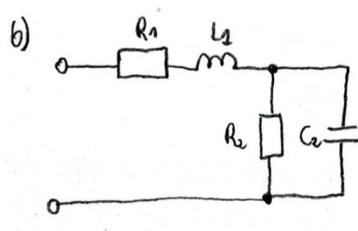
$$Y_{eq} = 1/\underline{Z}_{eq} = \boxed{0.0426 - j0.02 S}$$



$$R_1 = 25\Omega$$

$$L_1 = 50mH$$

$$R_2 = 100\Omega$$

$$C_2 = 10\mu F$$

$$f = 50\text{Hz}$$

$$X_{L1} = 2\pi f \cdot L_1 = 2 \cdot 3.14 \cdot 50 \cdot 0.05 = 15.708 \Omega$$


$$X_{C2} = \frac{1}{2\pi f C_2} = \frac{1}{2 \cdot 3.14 \cdot 50 \cdot 10 \cdot 10^{-6}} = 318.3088 \Omega$$

$$\underline{Z}_{eq} = R_1 + jX_{L1} + \frac{R_2 - jX_{C2}}{R_2 + jX_{C2}} = 25 + j15.708 + \frac{100 - (-j318.3088)}{100 + j318.3088} =$$

$$= \boxed{116.017 - j12.886 \Omega}$$

$$Y = 1/\underline{Z}_{eq} = \boxed{0.0085 + j0.009 S}$$

c)

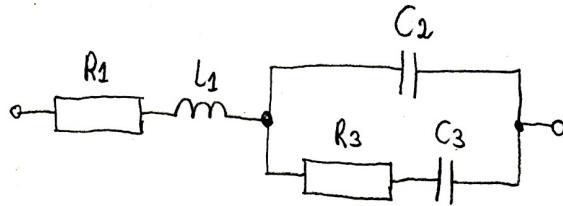

$$R_1 = 10\Omega, R_3 = 20\Omega, L_1 = 50mH$$

$$C_2 = 2mF, C_3 = 1mF$$

$$\omega = 100 \text{ rad/s}$$

$$X_{L1} = \omega L_1 = 100 \cdot 0.05 = 5\Omega$$

$$Z_1 = R_1 + jX_{L1} = (10 + j5)\Omega$$

$$Z_2 = Z_1 + \frac{Z_2 \cdot Z_3}{Z_2 + Z_3}$$

$$X_{C2} = \frac{1}{\omega C_2} = \frac{1}{100 \cdot 0.002} = 5\Omega$$

$$Z_2 = -jX_{C2} = -j5\Omega$$

$$Z_2 = 10 + j5 + \frac{(-j5)(20 - j10)}{-j5 + 20 - j10}$$


$$X_{C3} = \frac{1}{\omega C_3} = \frac{1}{100 \cdot 0.001} = 10\Omega$$

$$Z_3 = R_3 - jX_{C3} = (20 - j10)\Omega$$

$$Z_2 = 10 + j5 + 0.8 - j4.4$$

$$Z_2 = (10.8 + j0.6)\Omega$$

d)

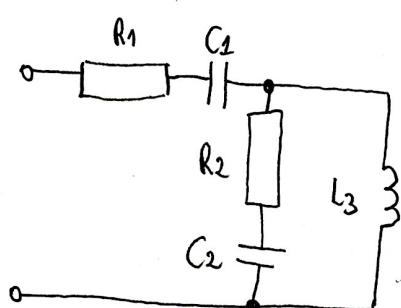

$$R_1 = 10\Omega, R_2 = 5\Omega, X_{C1} = 20\Omega, X_{C2} = 10\Omega, X_{L3} = 20\Omega$$

$$Z_1 = R_1 - jX_{C1} = (10 - j20)\Omega$$

$$Z_2 = R_2 - jX_{C2} = (5 - j10)\Omega$$


$$Z_3 = jX_{L3} = j20\Omega$$

$$Z_{eq} = Z_1 + \frac{Z_2 \cdot Z_3}{Z_2 + Z_3} = (10 - j20) + \frac{(5 - j10)(j20)}{5 - j10 + j20} = 10 - j20 + 16 - j12 = (26 - j32)\Omega$$
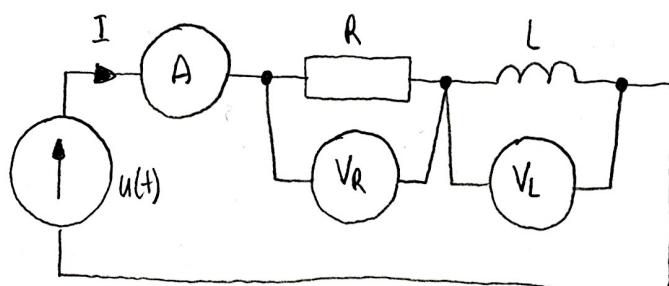
### PROBLEM #3

Calculate the meter readings in the circuit shown in the figure.

$$u(t) = 230\sqrt{2} \sin \omega t \text{ V}, R = 40\Omega, L = 0.2\text{H}, f = 50\text{Hz}$$



$$\omega = 2\pi f$$

$$X_L = \omega L = 2\pi f L = 2 \cdot 3.14 \cdot 50 \cdot 0.2 = 62.8318\Omega$$

#### Method 1

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{40^2 + 62.8318^2} = 74.4838\Omega$$

$$I = \frac{U}{Z} = \frac{230}{74.4838} = 3.0878 \text{ A} \quad I_A = I = 3.0878 \text{ A}$$

$$U_R = R \cdot I = 40 \cdot 3.0878 = 123.5167 \text{ V} \quad V_R = U_R = 123.5167 \text{ V}$$

$$U_L = X_L \cdot I = 62.8318 \cdot 3.0878 = 184.0186 \text{ V} \quad V_L = U_L = 184.0186 \text{ V}$$

## Method 2

$$u(t) = U_m \sin(\omega t + \varphi) \quad \underline{U} = U_{rms} \cdot (\cos \varphi + j \sin \varphi) \quad U_{rms} = \frac{U_m}{\sqrt{2}}$$

$$U_{rms} = \frac{230\sqrt{2}}{\sqrt{2}} = 230 \quad \varphi = 0^\circ$$

$$\underline{U} = 230 (\cos 0^\circ + j \sin 0^\circ) = 230 (1+j0) = 230 \text{ V}$$

$$Z = R + jX_L = (40 + j62.8319) \Omega$$

$$\underline{I} = \frac{\underline{U}}{Z} = \frac{230}{40 + j62.8319} = (1.6583 - j2.6048) A \quad |I| = \sqrt{1.6583^2 + 2.6048^2} = 3.0879 \text{ A}$$

$$I_A = |I| = 3.0879 \text{ A}$$

$$U_R = R \cdot I = 40 \cdot (1.6583 - j2.6048) = (66.3321 - j104.1942) \text{ V} \quad V_R = |U_R| = 123.5167 \text{ V}$$

$$U_L = jX_L \cdot I = j62.8319 \cdot (1.6583 - j2.6048) = (163.6679 + j104.1942) \text{ V} \quad V_L = |U_L| = 194.0196 \text{ V}$$

## Phasor diagram

$$\underline{U} = 230 = 230 e^{j0^\circ} \text{ V}$$

$$U_R = 66.3321 - j104.1942 = 123.52 e^{-j57.52^\circ} \text{ V}$$

$$U_L = 163.6679 + j104.1942 = 194.02 e^{j39.48^\circ} \text{ V}$$

$$\underline{I} = 1.6583 - j2.6048 = 3.08 e^{-j57.52^\circ} \text{ A}$$

$$\underline{U} = \underline{U}_R + \underline{U}_L$$

