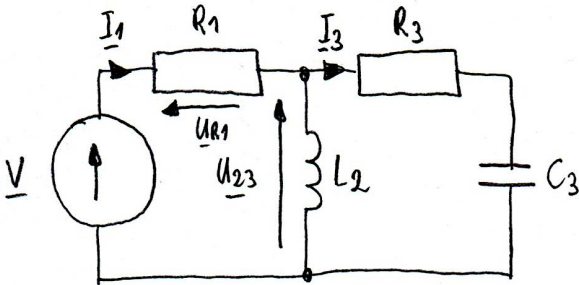


ELECTRICAL CIRCUITS 1 - CLASS NO. 10 (09.01.2025)

PROBLEM #1

In the circuit as shown in the figure, the resistor R_3 has the maximum power of $P_3 = 8 \text{ W}$. Check if this is sufficient for the correct operation of the system.

$$\underline{V} = 24 \angle 60^\circ \text{ V}, R_1 = 4 \Omega, X_{L2} = 6 \Omega, R_3 = 8 \Omega, X_{C3} = 4 \Omega.$$



$$\underline{V} = V (\cos 60^\circ + j \sin 60^\circ) = 24 \left(\frac{1}{2} + j \frac{\sqrt{3}}{2} \right) = 12 + j 12\sqrt{3} = (12 + j 20.78) \text{ V}$$

$$\underline{Z}_1 = R_1 = 4 \Omega \quad \underline{Z}_3 = R_3 - j X_{C3} = (8 - j 4) \Omega$$

$$\underline{Z}_2 = j X_{L2} = j 6 \Omega$$

$$\underline{Z}_{23} = \frac{\underline{Z}_2 \cdot \underline{Z}_3}{\underline{Z}_2 + \underline{Z}_3} = \frac{j 6 (8 - j 4)}{j 6 + 8 - j 4} = (4.24 + j 4.84) \Omega \quad \underline{Z} = \underline{Z}_1 + \underline{Z}_{23} = 4 + 4.24 + j 4.84 = (8.24 + j 4.84) \Omega$$

$$\underline{I}_1 = \frac{\underline{V}}{\underline{Z}} = \frac{12 + j 20.78}{8.24 + j 4.84} = (2.18 + j 1.21) \text{ A}$$

$$U_{23} = ? \quad \text{KVL: } \underline{U}_{R1} + \underline{U}_{23} = \underline{V} \Rightarrow \underline{U}_{23} = \underline{V} - \underline{U}_{R1} = \underline{V} - R_1 \cdot \underline{I}_1 = (12 + j 20.78) - 4 \cdot (2.18 + j 1.21) = (3.26 + j 15.83) \text{ V}$$

$$\text{Ohm's Law: } \underline{U}_{23} = \underline{Z}_{23} \cdot \underline{I}_1 = (4.24 + j 4.84)(2.18 + j 1.21) = (3.26 + j 15.83) \text{ V}$$


$$\underline{I}_3 = \frac{\underline{U}_{23}}{\underline{Z}_3} = \frac{3.26 + j 15.83}{8 - j 4} = (-0.47 + j 1.76) \text{ A} \quad |\underline{I}_3| = \sqrt{(-0.47)^2 + (1.76)^2} = 1.82$$

$$P_3 = R_3 \cdot I_3^2 = 8 \cdot 1.82^2 = \boxed{26.45 \text{ W}} > 8 \text{ W}$$

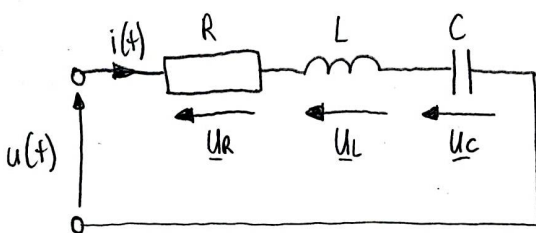PROBLEM #2

Calculate the current $i(t)$ and the voltage drops u_R , u_L , and u_C in the circuit shown below.

Draw a phasor diagram for this circuit. $R = 20 \Omega$, $L = 20 \text{ mH}$, $C = 100 \mu\text{F}$, $u(t) = 100\sqrt{2} \cos \omega t \text{ V}$, $\omega = 10^3 \text{ rad/s}$.



$$X_L = \omega L = 1000 \cdot 0.02 = 20 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{1000 \cdot 100 \cdot 10^{-6}} = 10 \Omega$$

$$\underline{Z} = R + j X_L - j X_C = 20 + j 20 - j 10 = (20 + j 10) \Omega$$

Method 1

$$u(t) = U_m \cos(\omega t + \varphi) \quad U_m = 100\sqrt{2} \quad \varphi = 0^\circ \quad U_{rms} = \frac{U_m}{\sqrt{2}} = \frac{100\sqrt{2}}{\sqrt{2}} = 100 \text{ V}$$

$$\underline{U} = U_{rms} (\cos \varphi + j \sin \varphi) = 100 (\cos 0^\circ + j \sin 0^\circ) = 100 (1 + j0) = 100 \text{ V}$$

$$\underline{I} = \frac{\underline{U}}{\underline{Z}} = \frac{100}{20 + j10} = \frac{100(20 - j10)}{(20 + j10)(20 - j10)} = \frac{200 - j100}{20^2 + 10^2} = \frac{2000 - j1000}{500} = (4 - j2) \text{ A} = 4.47 e^{-j26.57^\circ} \text{ A}$$

$$\underline{U}_R = R \cdot \underline{I} = 20(4 - j2) = (80 - j40) \text{ V} = 89.44 e^{-j26.57^\circ} \text{ V}$$

$$\underline{U}_L = jX_L \cdot \underline{I} = j20(4 - j2) = (40 + j80) \text{ V} = 89.44 e^{j63.44^\circ} \text{ V}$$


$$\underline{U}_C = -jX_C \cdot \underline{I} = -j10(4 - j2) = (-20 - j40) \text{ V} = 44.72 e^{-j116.57^\circ} \text{ V}$$

$$i(t) = 4.47\sqrt{2} \cos(\omega t - j26.57^\circ) \text{ A}$$

$$\Rightarrow i(t) = 4.47\sqrt{2} \sin(\omega t + 63.44^\circ) \text{ A}$$

$$\cos \alpha = \sin(\alpha + 90^\circ)$$

Phasor diagram

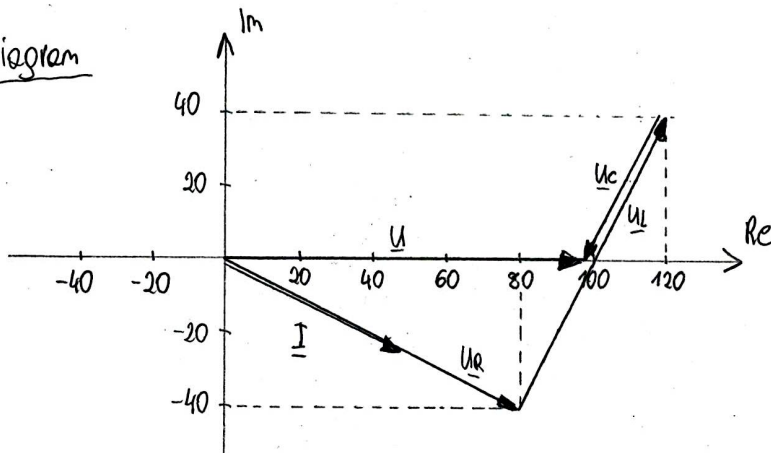

$$U_{Rrms} + U_{Lrms} + U_{Crms} \neq U_{rms}$$

$$89.44 + 89.44 + 44.72 \neq 100$$

$$226.6 \neq 100$$

$$\underline{U}_R + \underline{U}_L + \underline{U}_C = \underline{U}$$

$$80 - j40 + 40 + j80 - 20 - j40 = 100$$

$$100 = 100$$

Method 2

$$\cos \alpha = \sin(\alpha + 90^\circ)$$

$$u(t) = U_m \cos(\omega t + \varphi) = U_m \sin(\omega t + \varphi + 90^\circ)$$

$$u(t) = 100\sqrt{2} \cos \omega t = 100\sqrt{2} \sin(\omega t + 90^\circ) \quad U_{rms} = 100, \quad \varphi = 90^\circ$$

$$\underline{U} = 100 (\cos 90^\circ + j \sin 90^\circ) = 100 (0 + j1) = j100 \text{ V}$$

$$\underline{Z} = (20 + j10) \Omega$$

$$\underline{I} = \frac{\underline{U}}{\underline{Z}} = \frac{j100}{20 + j10} = \frac{j100(20 - j10)}{(20 + j10)(20 - j10)} = \frac{1000 + j2000}{20^2 + 10^2} = \frac{1000 + j2000}{500} = (2 + j4) \text{ A} = 4.47 e^{j63.44^\circ} \text{ A}$$

$$i(t) = 4.47\sqrt{2} \sin(\omega t + 63.44^\circ) \text{ A}$$


$$\underline{U}_R = R \cdot \underline{I} = 20(2 + j4) = (40 + j80) \text{ V} = 89.44 e^{j63.44^\circ} \text{ V}$$

$$\underline{U}_L = jX_L \cdot \underline{I} = j20(2 + j4) = (-80 + j40) \text{ V} = 89.44 e^{j153.44^\circ} \text{ V}$$

$$\underline{U}_C = -jX_C \cdot \underline{I} = -j10(2 + j4) = (40 - j20) \text{ V} = 44.72 e^{-j26.57^\circ} \text{ V}$$

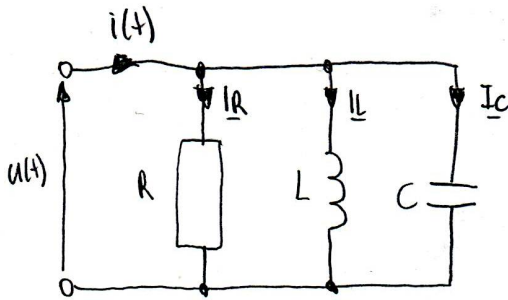PROBLEM #3

Calculate the currents $i(t)$, I_R , I_L , and I_C in the circuit shown below. Draw a phasor diagram for this circuit. $R = 20 \Omega$, $L = 20 \text{ mH}$, $C = 100 \mu\text{F}$, $u(t) = 100\sqrt{2} \cos \omega t \text{ V}$, $\omega = 10^3 \text{ rad/s}$.



$$X_L = \omega L = 1000 \cdot 0.02 = 20 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{1000 \cdot 100 \cdot 10^{-6}} = 10 \Omega$$

$$U = 100 (\cos 0^\circ + j \sin 0^\circ) = 100 \text{ V}$$

$$G = \frac{1}{R} = \frac{1}{20} = 0.05 \text{ S}$$

$$B_C = \omega C = 1000 \cdot 100 \cdot 10^{-6} = 0.1 \text{ S}$$

$$B_L = \frac{1}{\omega L} = \frac{1}{1000 \cdot 0.02} = 0.05 \text{ S}$$

Method 1

$$Y = G + j(B_C - B_L)$$

$$Y = 0.05 + j(0.1 - 0.05) \text{ S}$$

$$Y = (0.05 + j0.05) \text{ S}$$

$$\underline{I} = \frac{U}{Z} = U \cdot Y = 100 \cdot (0.05 + j0.05) = (5 + j5) \text{ A} = 7.07 e^{j45^\circ} \text{ A}$$

$$i(t) = 7.07\sqrt{2} \cos(\omega t + 45^\circ) \text{ A}$$

Method 2

$$I_R = \frac{U}{R} = \frac{100}{20} = 5 \text{ A} = 5e^{j0^\circ} \text{ A}$$


$$I_L = \frac{U}{jX_L} = \frac{100}{j20} = -j5 \text{ A} = 5e^{-j90^\circ} \text{ A}$$

$$I_C = \frac{U}{-jX_C} = \frac{100}{-j10} = j10 \text{ A} = 10e^{j90^\circ} \text{ A}$$

$$\underline{I} = I_R + I_L + I_C = 5 - j5 + j10 = (5 + j5) \text{ A} = 7.07 e^{j45^\circ} \text{ A}$$

$$i(t) = 7.07\sqrt{2} \cos(\omega t + 45^\circ) \text{ A}$$

Phasor diagram

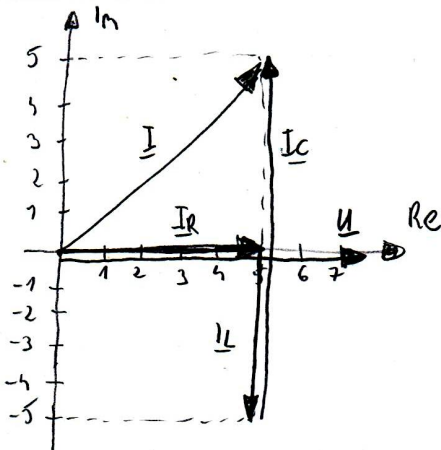

$$I_{R\text{rms}} + I_{L\text{rms}} + I_{C\text{rms}} \neq I_{\text{rms}}$$

$$5 + 5 + 10 \neq 7.07$$

$$20 \neq 7.07$$



$$\underline{I}_R + \underline{I}_L + \underline{I}_C = \underline{I}$$

$$5 - j5 + j10 = 5 + j5$$

$$5 + j5 = 5 + j5$$



PHASOR DIAGRAMS

* RESISTOR (R)

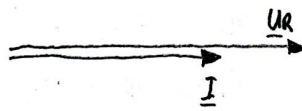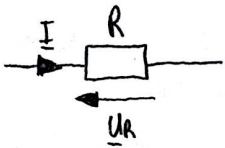



* the voltage \underline{U}_R across a resistance R is in phase with the current \underline{I}

* INDUCTOR (L)

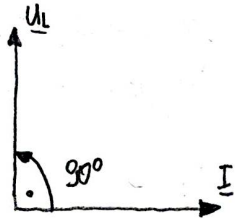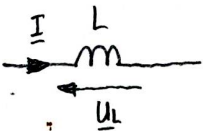

* the voltage \underline{U}_L across an inductor L leads the current \underline{I} by 90° ($\frac{\pi}{2}$)

* CAPACITOR (C)

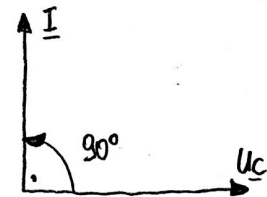
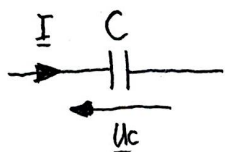


* the voltage \underline{U}_C across a capacitor C lags the current \underline{I} by 90° ($\frac{\pi}{2}$)

PROBLEM #4



Draw phasor diagrams for the following circuits.

a)

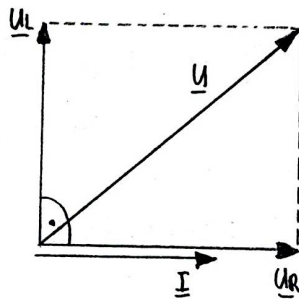
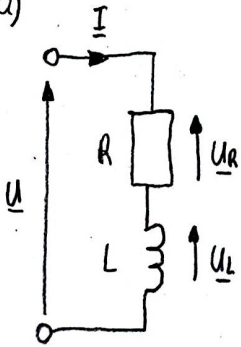


- * we start from the current \underline{I} and we assume a phase angle of 0°
- * the voltage \underline{U}_R across a resistance R is in phase with the current \underline{I}
- * the voltage \underline{U}_L across an inductor L leads the current \underline{I} by 90°
- * the voltage \underline{U} is a sum of voltage drops \underline{U}_R and \underline{U}_L (from KVL)





b)

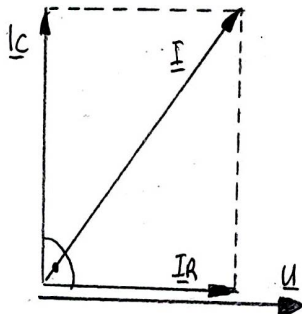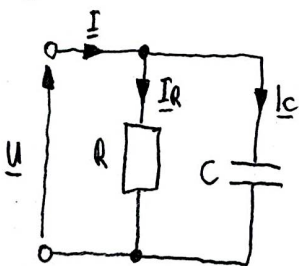

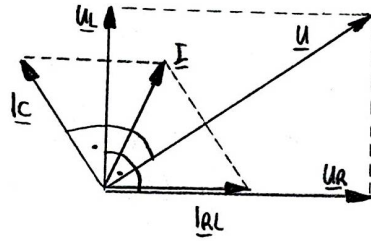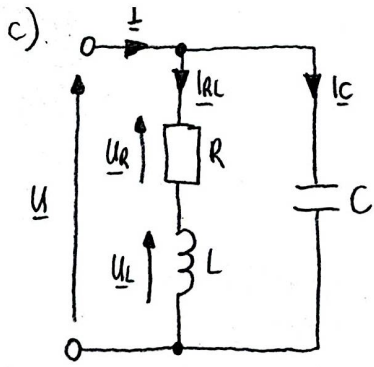- * we start from the current \underline{I}_R and we assume a phase angle of 0°
- * the voltage \underline{U} is in phase with the current \underline{I}_R
- * the current \underline{I}_C through a capacitor C leads the current \underline{I}_R by 90°
- * the current \underline{I} is a sum of currents \underline{I}_R and \underline{I}_C (from KCL)



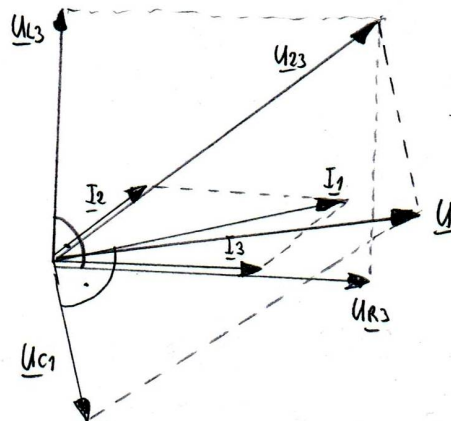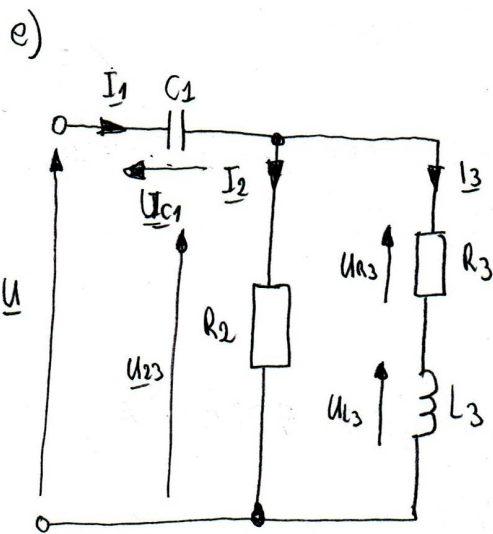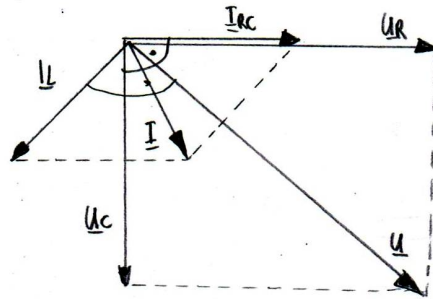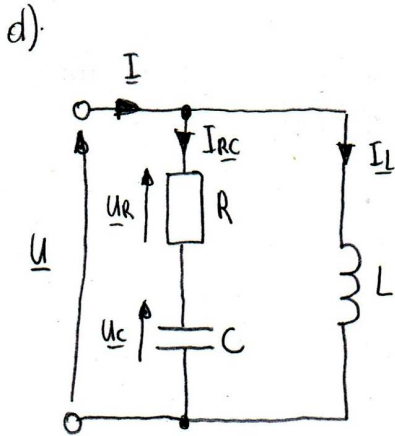- * We start from the current I_{RL} and we assume a phase angle of 0°
- * the voltage U_R is in phase with the current I_{RL}
- * the voltage drop U_L leads the current I_{RL} by 90°
- * the voltage U is a sum of voltage drops U_R and U_L (from KVL)
- * the current I_C leads the voltage U by 90°
- * the current I is a sum of currents I_{RC} and I_C (from KCL)



POWER IN AC CIRCUITS

* P - ACTIVE POWER (TRUE POWER, REAL POWER) unit: Watt [W]

$$P = U_{rms} \cdot I_{rms} \cdot \cos \varphi, \quad \text{where } \varphi = \varphi_u - \varphi_i \text{ (angle between voltage and current)}$$

$$U_{rms} = \frac{U_m}{\sqrt{2}} \quad I_{rms} = \frac{I_m}{\sqrt{2}} \quad \rightarrow \quad P = \frac{U_m \cdot I_m}{2} \cdot \cos \varphi \quad P = R \cdot I_{rms}^2 = \frac{U_{rms}^2}{R}$$

* Q - REACTIVE POWER unit: voltampere (reactive) [var]

$$Q = U_{rms} \cdot I_{rms} \cdot \sin \varphi \quad \varphi = \varphi_u - \varphi_i \text{ (angle between voltage and current)}$$

$$Q = \frac{U_m \cdot I_m}{2} \sin \varphi \quad Q = X \cdot I_{rms}^2 = \frac{U_{rms}^2}{X}$$



* S - APPARENT POWER unit: voltampere [VA]

$$S = U_{rms} \cdot I_{rms} \quad S = I_{rms}^2 \cdot Z = \frac{U_{rms}^2}{Z}$$

* S - PHASOR POWER (COMPLEX POWER)

$$\underline{S} = \underline{U} \cdot \underline{I}^* \quad \underline{S} = P + jQ \quad P = \operatorname{Re}[\underline{S}] \quad Q = \operatorname{Im}[\underline{S}]$$

* THE POWER TRIANGLE

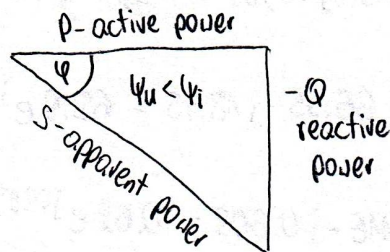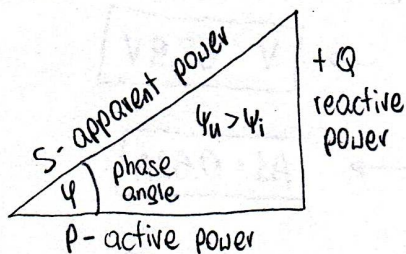


$$S = \sqrt{P^2 + Q^2}$$

* THE POWER FACTOR (pf)

$$(pf) = \frac{P}{S} = \cos \varphi$$

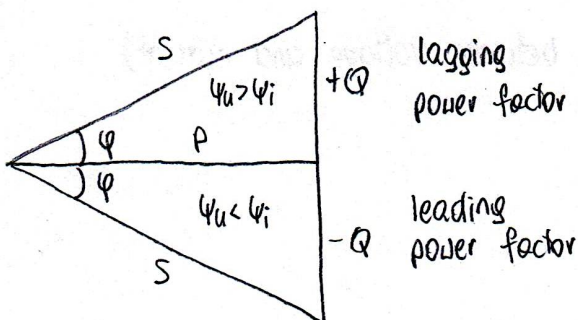* the ratio between the active power and the apparent power of a load is called the power factor of the load




* inductive loads always have a lagging power factor

* capacitive loads always have a leading power factor

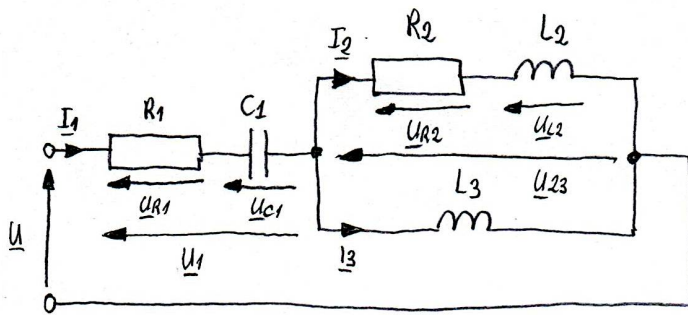PROBLEM #5

Calculate the all currents and voltages in the circuit shown in the figure. Determine the active, reactive, and apparent power consumed by the circuit. Draw a phasor diagram for the circuit.

$$U = (10 + j10) \text{ V}, \quad R_1 = 1 \Omega, \quad R_2 = 5 \Omega, \quad X_{C1} = X_{L2} = X_{L3} = 5 \Omega.$$



$$Z = R_1 - jX_{C1} + \frac{(R_2 + jX_{L2}) \cdot (jX_{L3})}{R_2 + jX_{L2} + jX_{L3}} =$$

$$= 1 - j5 + \frac{(5 + j5)(j5)}{5 + j5 + j5} = (2 - j2) \Omega$$

$$I_1 = \frac{U}{Z} = \frac{10 + j10}{2 - j2} = \boxed{j5 \text{ A}}$$

$$U_1 = (R_1 - jX_{C1}) \cdot I_1 = (1 - j5) \cdot (j5) = \boxed{(25 + j5) \text{ V}}$$

$$U_{23} = U - U_1 = 10 + j10 - 25 - j5 = \boxed{(-15 + j5) \text{ V}}$$

$$I_2 = \frac{U_{23}}{R_2 + jX_{L2}} = \frac{-15 + j5}{5 + j5} = \boxed{(-1 + j2) \text{ A}}$$

$$I_3 = \frac{U_{23}}{jX_{L3}} = \frac{-15 + j5}{j5} = \boxed{(1 + j3) \text{ A}}$$

$$U_{R2} = R_2 \cdot I_2 = 5 \cdot (-1 + j2) = \boxed{(-5 + j10) \text{ V}}$$

$$U_{R1} = R_1 \cdot I_1 = 1 \cdot j5 = \boxed{j5 \text{ V}}$$

$$U_{L2} = jX_{L2} \cdot I_2 = j5 \cdot (-1 + j2) = \boxed{(-10 - j5) \text{ V}}$$

$$U_{C1} = (-jX_{C1}) \cdot I_1 = -j5 \cdot j5 = \boxed{25 \text{ V}}$$

$$S = U \cdot I_1^* = (10 + j10) \cdot (-j5) = \boxed{(50 - j50) \text{ VA}}$$

$$P = \boxed{50 \text{ W}}$$

$$Q = \boxed{-50 \text{ var}}$$

$$S = \boxed{70.71 \text{ VA}}$$

