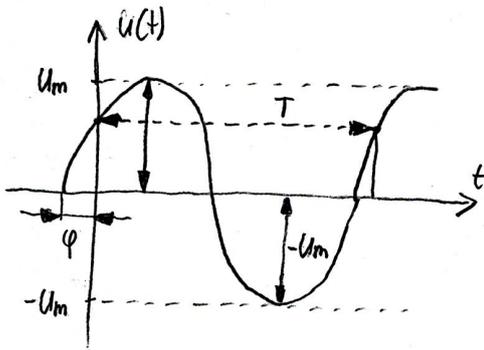


**A SINE WAVE**

$$u(t) = U_m \cdot \sin(\omega t + \varphi)$$



$u(t)$  - the instantaneous value of the signal

$U_m$  - the maximum value of the signal

the peak value of the signal (amplitude)

the letter symbol for the peak value of an alternating source voltage is  $U_m$  (m for maximum)

$T$  - period [s]

$f$  - frequency [Hz] - the inverse of  $T$ ,  $f = \frac{1}{T}$

$\omega$  - angular velocity [rad/s] - radian per second

$$\omega = 2\pi f = \frac{2\pi}{T}$$

$\varphi$  - phase angle or phase shift

$U_{rms}$  - rms value (root-mean square), the effective value

$$U_{rms} = \sqrt{\frac{1}{T} \int_0^T u^2(t) dt}$$

$$U_{rms} = \frac{U_m}{\sqrt{2}}$$

the rms value of a sine wave of voltage is  $1/\sqrt{2}$  of the peak value

**COMPLEX NUMBERS**


\* complex number can be represented in the form:

- algebraic form (rectangular form):  $z = a + jb$
- trigonometric form (polar form):  $z = r(\cos \varphi + j \sin \varphi)$
- exponential form:  $z = r \cdot e^{j\varphi}$

\* algebraic (rectangular) form of complex number

$$z = a + jb$$

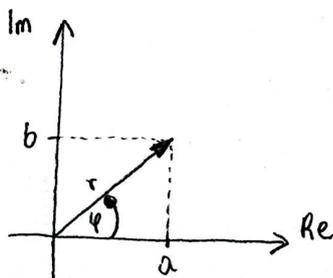- complex numbers have a real part and an imaginary part
- $a$  - real part ( $\text{Re}(z)$ ) of complex number,  $\text{Re}[z]$
- $b$  - imaginary part of complex number,  $\text{Im}[z]$
- $j$  - imaginary unit (number)  $j^2 = -1$ ,  $j = \sqrt{-1}$  - square root of minus one
- graphical representation of complex number



□ we use horizontal axis for the real part and vertical axis for the imaginary part

□  $r = |z| = \sqrt{a^2 + b^2}$  - the absolute value of complex number (modulus)

□  $\varphi$  - argument of complex number  $\varphi = \text{arc tg } \frac{b}{a}$

\* trigonometric (polar) form of complex number

$$z = r(\cos \varphi + j \sin \varphi)$$

$$r = \sqrt{a^2 + b^2} \quad \varphi = \arctan \frac{b}{a}$$

$$z = a + jb = r \left( \underbrace{\frac{a}{r}}_{\cos \varphi} + j \underbrace{\frac{b}{r}}_{\sin \varphi} \right) = r(\cos \varphi + j \sin \varphi)$$

\* exponential form of complex number

$$z = re^{j\varphi} \quad e^{j\varphi} = \cos \varphi + j \sin \varphi$$

\* complex conjugate of z

$$z = a + jb$$

$$z = r(\cos \varphi + j \sin \varphi)$$


$$z = re^{j\varphi}$$



$$z^* = a - jb$$

$$z^* = r(\cos \varphi - j \sin \varphi)$$

$$z^* = re^{-j\varphi}$$

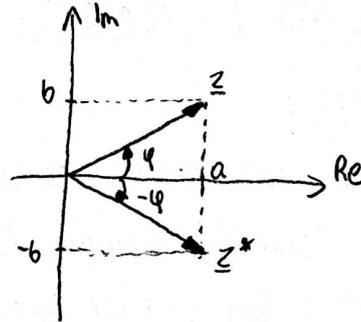

### BASIC OPERATIONS ON COMPLEX NUMBERS

$$\underline{z}_1 = a_1 + jb_1 \quad \underline{z}_2 = a_2 + jb_2$$

\* sum of complex numbers


$$\underline{z} = \underline{z}_1 + \underline{z}_2 = a_1 + jb_1 + a_2 + jb_2 = \underbrace{a_1 + a_2}_{\text{Re}} + j \underbrace{(b_1 + b_2)}_{\text{Im}}$$

we can add complex numbers graphically

$$\underline{z}_1 = 3 + j2$$

$$\underline{z}_2 = 1 - j4$$
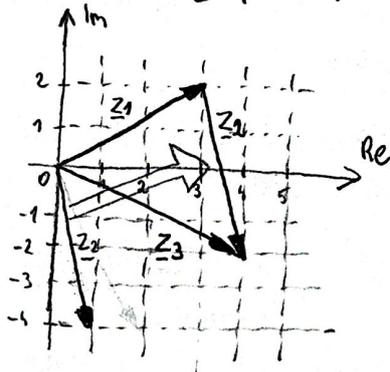
$$\underline{z}_1 + \underline{z}_2 = 4 - j2$$



□ we move vector  $\underline{z}_2$  to the end of vector  $\underline{z}_1$

\* difference of complex numbers

$$\underline{z} = \underline{z}_1 - \underline{z}_2 = \underbrace{a_1 - a_2}_{\text{Re}} + j \underbrace{(b_1 - b_2)}_{\text{Im}}$$

\* product of complex number

$$\underline{z} = \underline{z}_1 * \underline{z}_2 = (a_1 + jb_1) * (a_2 + jb_2) = \underbrace{a_1 \cdot a_2 - b_1 \cdot b_2}_{\text{Re}} + j \underbrace{(a_1 b_2 + b_1 a_2)}_{\text{Im}}$$

\* division of complex number


$$Z = \frac{Z_1}{Z_2} = \frac{a_1 + jb_1}{a_2 + jb_2} = \frac{(a_1 + jb_1) \cdot (a_2 - jb_2)}{(a_2 + jb_2) \cdot (a_2 - jb_2)} = \frac{a_1 \cdot a_2 + b_1 \cdot b_2}{a_2^2 + b_2^2} + j \frac{b_1 \cdot a_2 - a_1 \cdot b_2}{a_2^2 + b_2^2}$$

$\underbrace{\hspace{10em}}_{\text{Re}}$ 
 $\underbrace{\hspace{10em}}_{\text{Im}}$

□ we multiply numerator and denominator by the conjugate of the denominator

**RESISTOR**

\* Resistor, Resistance [Ω]

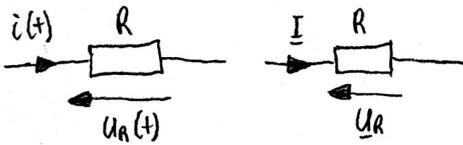

R - resistance [Ω]


G - conductance [S]

Z - impedance

Y - admittance

$$U_R(t) = R \cdot i(t)$$
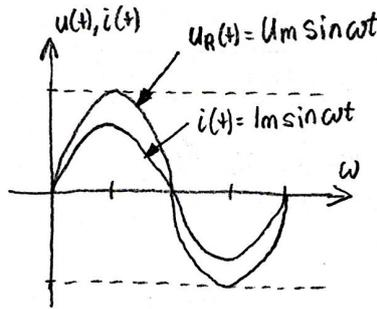
$$\underline{U}_R = R \cdot \underline{I}$$



phasor diagram


\* the voltage across a resistance is in phase with the current

$$G = \frac{1}{R} \quad Z = R \quad Y = \frac{1}{Z} = \frac{1}{R} = G$$

$$\psi_u = \psi_i$$



**CAPACITOR**

\* Capacitor, Capacitance [F]

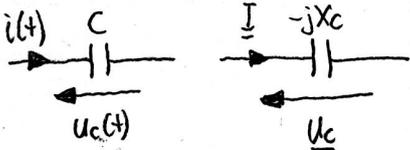

X\_C - capacitive reactance [Ω]

B\_C - capacitive susceptance [S]

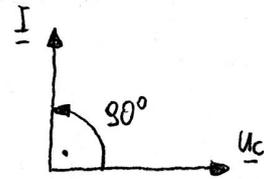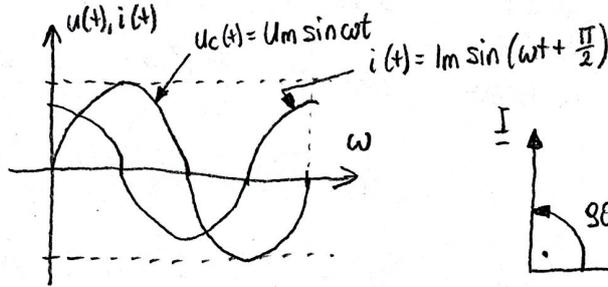

phasor diagram

\* the voltage across a capacitor lags the current by 90° (π/2)

$$X_C = \frac{1}{\omega C} \quad \omega = 2\pi f$$


$$Z = -jX_C \quad Y = \frac{1}{-jX_C} = jB_C$$

$$u_C(t) = \frac{1}{C} \int i(t) dt \quad \underline{U}_C = -jX_C \cdot \underline{I}$$

$$\psi_i = \psi_u + 90^\circ$$



## INDUCTOR

\* Inductor, Inductance [H]

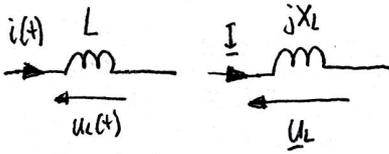

$X_L$  - inductive reactance [ $\Omega$ ]

$B_L$  - inductive susceptance [S]

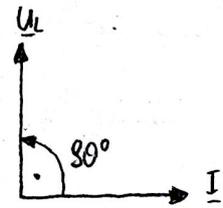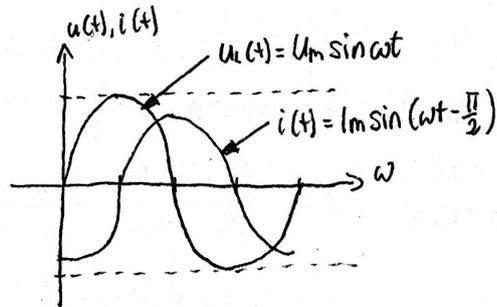

$$X_L = \omega L \quad \omega = 2\pi f$$

$$\underline{Z} = jX_L \quad \underline{Y} = \frac{1}{\underline{Z}} = \frac{1}{jX_L} = -jB_L$$


$$u_L(t) = L \frac{di(t)}{dt} \quad \underline{U}_L = jX_L \cdot \underline{I}$$

\* the voltage across an inductor leads the current by  $90^\circ$  ( $\frac{\pi}{2}$ )

$$\psi_u = \psi_i + 90^\circ$$
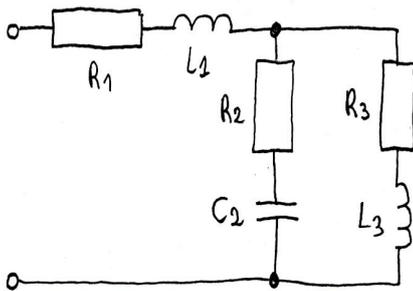
## PROBLEM #1

Calculate the equivalent impedance of the circuit shown in the figure.



$$R_1 = 10 \Omega, R_2 = 5 \Omega, R_3 = 15 \Omega, L_1 = 50 \text{ mH}, L_3 = 200 \text{ mH}, C_2 = 1 \text{ mF}, \omega = 100 \frac{\text{rad}}{\text{s}}$$

$$X_{L1} = \omega L_1 = 100 \cdot 50 \cdot 10^{-3} = 5 \Omega$$

$$X_{L3} = \omega L_3 = 20 \cdot 10^{-3} \cdot 100 = 20 \Omega$$

$$X_{C2} = 1/\omega C_2 = \frac{1}{100 \cdot 1 \cdot 10^{-3}} = 10 \Omega$$

$$\underline{Z}_1 = R_1 + jX_{L1} = (10 + j5) \Omega$$

$$\underline{Z}_{23} = \frac{\underline{Z}_2 \cdot \underline{Z}_3}{\underline{Z}_2 + \underline{Z}_3} = \frac{(5 - j10)(15 + j20)}{5 - j10 + 15 + j20} = (10 - j7.5) \Omega$$

$$\underline{Z}_2 = R_2 - jX_{C2} = (5 - j10) \Omega$$


$$\underline{Z}_3 = R_3 + jX_{L3} = (15 + j20) \Omega$$

$$\underline{Z}_{eq} = \underline{Z}_1 + \underline{Z}_{23} = 10 + j5 + 10 - j7.5 = \boxed{(20 - j2.5) \Omega}$$
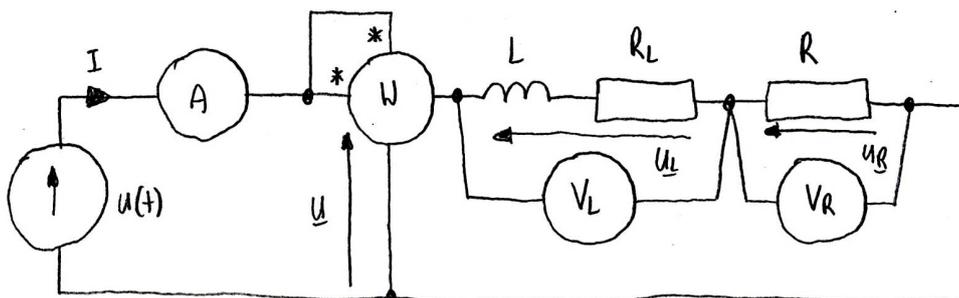
## PROBLEM #2

Calculate meter readings in the circuit shown in the figure.

$$u(t) = 230\sqrt{2} \sin \omega t \text{ V}, L = 0.2 \text{ H}, R_L = 40 \Omega, R = 100 \Omega, f = 50 \text{ Hz}$$



$$u(t) = U_{\text{rms}} \sqrt{2} \sin(\omega t + \varphi)$$

$$\underline{U} = U_{\text{rms}} (\cos \varphi + j \sin \varphi)$$

$$U_{\text{rms}} = 230 \quad \varphi = 0^\circ$$

$$\underline{U} = 230 (\cos 0^\circ + j \sin 0^\circ)$$

$$\underline{U} = 230 (1 + 0j) = 230 \text{ V}$$

$$X_L = \omega L = 2\pi f L = 2 \cdot 3.14 \cdot 50 \cdot 0.2 = 62.83 \Omega$$

$$\underline{Z} = jX_L + R_L + R = 62.83j + 40 + 100 = (140 + 62.83j) \Omega$$

$$\underline{I} = \frac{\underline{U}}{\underline{Z}} = \frac{230}{140 + 62.83j} = (1.37 - 0.61j) \text{ A} \quad |I| = \sqrt{1.37^2 + (-0.61)^2} = \boxed{1.5 \text{ A}}$$

$$\underline{U}_L = (R_L + jX_L) \cdot \underline{I} = (40 + 62.83j)(1.37 - 0.61j) = (93.26 + 61.37j) \text{ V} \quad U_L = |\underline{U}_L| = \boxed{111.64 \text{ V}}$$


$$\underline{U}_R = R \cdot \underline{I} = 100 \cdot (1.37 - 0.61j) = (137 - 61j) \text{ V} \quad U_R = |\underline{U}_R| = \boxed{149.88 \text{ V}}$$

$$\underline{S} = \underline{U} \cdot \underline{I}^* = 230(1.37 + 0.61j) = \underbrace{(314)}_P + \underbrace{(141j)}_Q \text{ VA} \quad P = \text{Re}\{\underline{S}\} = \boxed{314 \text{ W}}$$
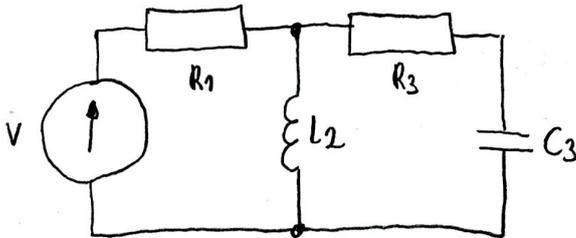
### PROBLEM #3


In the circuit shown in the figure, the resistor  $R_3$  has the maximum power  $P_3 = 8 \text{ W}$ . Check if this is enough for the correct operation of this system.

$$V = 24 \angle 60^\circ \text{ V}, R_1 = 4 \Omega, X_{L2} = 6 \Omega, R_3 = 8 \Omega, X_{C3} = 4 \Omega$$



$$\underline{V} = 24 (\cos 60^\circ + j \sin 60^\circ) = (12 + j 20.7846) \text{ V}$$

#### Method 1 (Loop-Current Method)

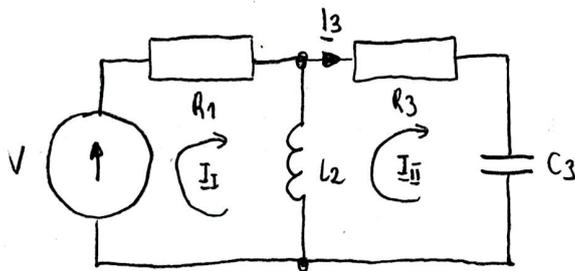

$$\begin{cases} \underline{I}_1 (R_1 + jX_{L2}) - \underline{I}_2 (jX_{L2}) = \underline{V} \\ -\underline{I}_1 (jX_{L2}) + \underline{I}_2 (R_3 + jX_{L2} - jX_{C3}) = 0 \end{cases}$$

$$\begin{cases} (4 + j6) \underline{I}_1 - (j6) \underline{I}_2 = 12 + j 20.7846 \\ -(j6) \underline{I}_1 + (8 + j2) \underline{I}_2 = 0 \end{cases}$$

$$W = \begin{vmatrix} 4 + j6 & -j6 \\ -j6 & 8 + j2 \end{vmatrix} = (4 + j6)(8 + j2) - (-j6)(-j6) = 32 + j8 + j48 - 12 + 36 = 56 + j56$$

$$W_{II} = \begin{vmatrix} 4 + j6 & 12 + j 20.7846 \\ -j6 & 0 \end{vmatrix} = (4 + j6) \cdot 0 - (-j6) \cdot (12 + j 20.7846) = -124.71 + j 72$$


$$\underline{I}_{II} = \frac{W_{II}}{W} = \frac{-124.71 + j 72}{56 + j 56} = (-0.4706 + j 1.7563) \text{ A} \quad I_3 = \underline{I}_{II}$$

$$\underline{U}_3 = R_3 \cdot \underline{I}_3 = 8 \cdot (-0.4706 + j 1.7563) = (-3.7648 + j 14.0505) \text{ V}$$

$$\underline{S} = \underline{U}_3 \cdot \underline{I}_3^* = (-3.7648 + j 14.0505) \cdot (-0.4706 - j 1.7563) = 26.448 \text{ VA} \quad P_{R3} = \text{Re}\{\underline{S}\} = 26.448 \text{ W} > 8 \text{ W}$$

The resistor has too low maximum power.

## Method 2 (Ohm's Law, KCL, KVL)

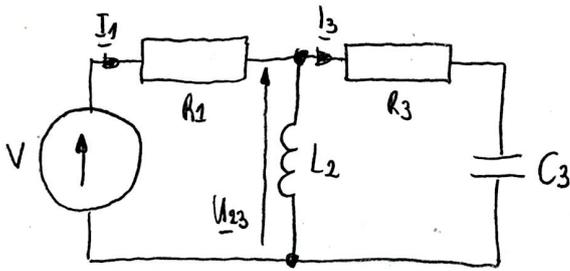

$$Z_1 = R_1 = 4 \Omega$$

$$Z_2 = jX_{L2} = j6 \Omega$$

$$Z_3 = R_3 - jX_{C3} = (8 - j4) \Omega$$

$$Z_{23} = \frac{Z_2 \cdot Z_3}{Z_2 + Z_3} = \frac{j6 \cdot (8 - j4)}{j6 + 8 - j4} = (4.2353 + j4.9412) \Omega$$

$$Z_{eq} = Z_1 + Z_{23} = 4 + 4.2353 + j4.9412 = (8.2353 + j4.9412) \Omega$$

$$\underline{I}_1 = \frac{\underline{V}}{Z_{eq}} = \frac{12 + j20.7846}{8.2353 + j4.9412} = (2.1849 + j1.2129) \text{ A}$$

$$\underline{U}_{23} = Z_{23} \cdot \underline{I}_1 = (4.2353 + j4.9412) \cdot (2.1849 + j1.2129) = (3.2604 + j15.933) \text{ V}$$

$$\underline{I}_3 = \frac{\underline{U}_{23}}{Z_3} = \frac{(3.2604 + j15.933)}{8 - j4} = (-0.4706 + j1.7563) \text{ A}$$

$$\underline{U}_3 = R_3 \cdot \underline{I}_3 = 8 \cdot (-0.4706 + j1.7563) = (-3.7648 + j14.0505) \text{ V}$$

$$\underline{S} = \underline{U}_3 \cdot \underline{I}_3^* = (-3.7648 + j14.0505) \cdot (-0.4706 - j1.7563) = 26.449 \text{ VA}$$

$$P_{R3} = \text{Re}[\underline{S}] = 26.449 \text{ W} > 8 \text{ W}$$


The resistor  $R_3$  has too low maximum power.

### PROBLEM #4

(this problem was not solved during the class)

The circuit as shown in the figure has been protected by a 6A overcurrent circuit breaker. Check that it will ensure continuous operation of this circuit when supplied with a sine wave voltage of 24V rms.

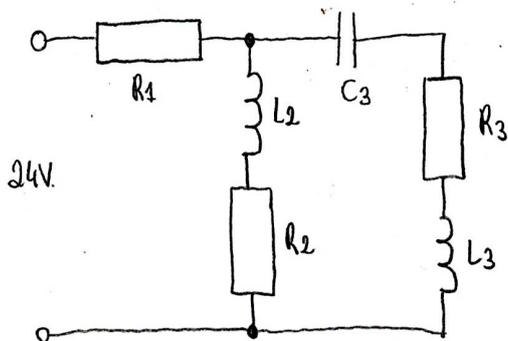$R_1 = 2 \Omega$ ,  $X_{L2} = 2 \Omega$ ,  $R_2 = 2 \Omega$ ,  $X_{C3} = 4 \Omega$ ,  $R_3 = 4 \Omega$ ,  $X_{L3} = 6 \Omega$



$$U = 24 \text{ V}$$

$$Z_1 = R_1 = 2 \Omega$$

$$Z_2 = R_2 + jX_{L2} = (2 + 2j) \Omega$$

$$Z_3 = R_3 - jX_{C3} + jX_{L3} = 4 - 4j + 6j = (4 + 2j) \Omega$$

$$Z_{23} = \frac{Z_2 \cdot Z_3}{Z_2 + Z_3} = \frac{(2 + 2j)(4 + 2j)}{2 + 2j + 4 + 2j} = (1.38 + 1.08j) \Omega$$

$$Z = Z_1 + Z_{23} = 2 + 1.38 + 1.08j = (3.38 + 1.08j) \Omega$$

$$\underline{I} = \frac{U}{Z} = \frac{24}{3.38 + 1.08j} = (6.44 - 2.05j) \text{ A}$$

$$I = |\underline{I}| = \sqrt{6.44^2 + (-2.05)^2} = \boxed{6.76 \text{ A}} > 6 \text{ A}$$

The current of an overcurrent circuit breaker is too low.