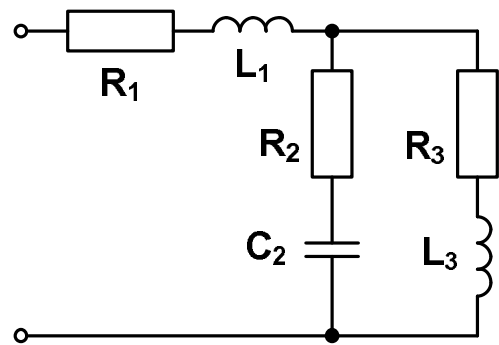


Module name: **Electrical Circuits 2**  
 Module ID: **IS-FEE-10085S**  
 Module type: **Class**  
 Semester: **summer 2024/2025**  
 Instructor: **Jarosław Forenc, [j.forenc@pb.edu.pl](mailto:j.forenc@pb.edu.pl)**

**Class 1 (04.03.2025)**


1. Calculate the **equivalent impedance** of the circuit shown in the figure.

$R_1 = 10 \Omega$ ,  $R_2 = 5 \Omega$ ,  $R_3 = 15 \Omega$ ,  
 $L_1 = 50 \text{ mH}$ ,  $L_3 = 200 \text{ mH}$ ,  $C_2 = 1 \text{ mF}$ ,  
 $\omega = 100 \text{ rad/s}$



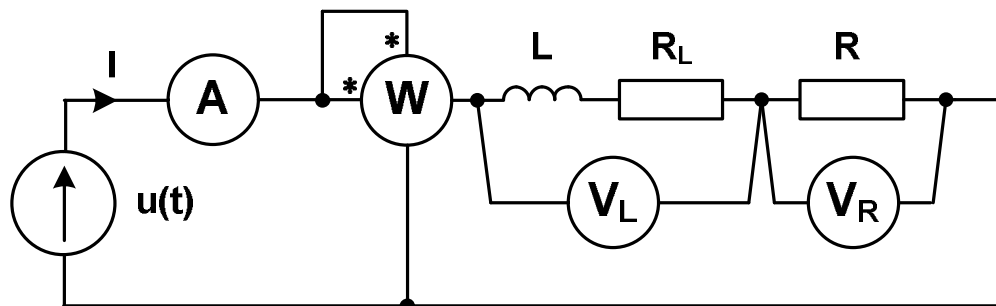
2. Calculate **meter readings** in the circuit shown in the figure.

$u(t) = 230\sqrt{2}\sin\omega t \text{ V}$ ,  $L = 0.2 \text{ H}$ ,  $R_L = 40 \Omega$ ,  $R = 100 \Omega$ ,  $f = 50 \text{ Hz}$ .



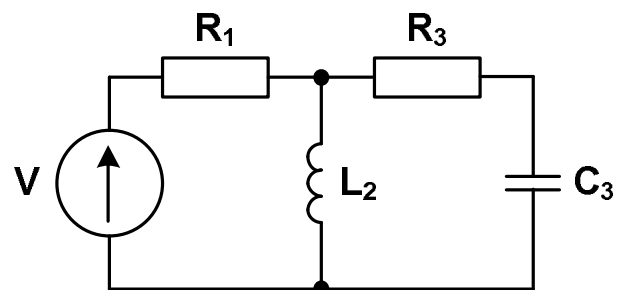
3. In the circuit as shown in the figure, the resistor  $R_3$  has the maximum power  $P_3 = 8 \text{ W}$ . Check if this is enough for the correct operation of this system.

$V = 24 \angle 60^\circ \text{ V}$ ,  $R_1 = 4 \Omega$ ,  $X_{L2} = 6 \Omega$ ,  
 $R_3 = 8 \Omega$ ,  $X_{C3} = 4 \Omega$ .



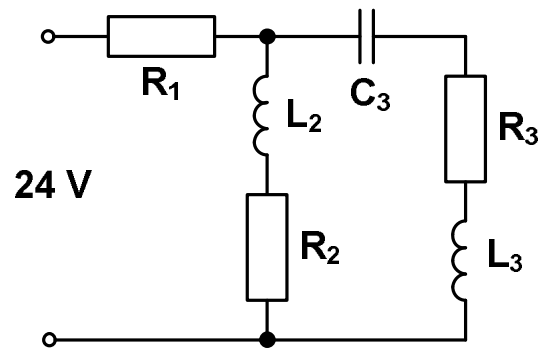4. The circuit as shown in the figure has been protected by a **6 A** overcurrent circuit breaker. Check that it will ensure continuous operation of this circuit when supplied with a sine wave voltage of 24 V rms.

$$R_1 = 2 \Omega, X_{L2} = 2 \Omega, R_2 = 2 \Omega, \\ X_{C3} = 4 \Omega, R_3 = 4 \Omega, X_{L3} = 6 \Omega$$



04.03.2025

Jarosław Forenc, PhD

[j.forenc@pb.edu.pl](mailto:j.forenc@pb.edu.pl)