

**SELF INDUCTANCE**

$L$   
inductance - L

the unit of inductance: henry


the unit symbol: H

$X_L$  - inductive reactance  $Z = jX_L = j\omega L$

$X_L = \omega L$ ,  $\omega = 2\pi f$   $\omega$  - angular velocity


the unit of inductive reactance: ohm [ $\Omega$ ]

**INDUCTORS IN SERIES**

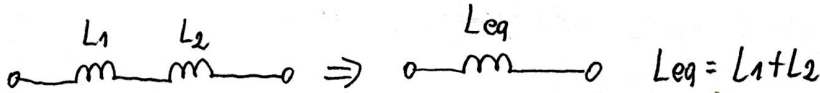


when there is no mutual coupling between inductors in series, the total inductance is the sum of the individual inductances

**INDUCTORS IN PARALLEL**

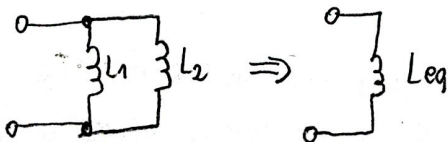

$$L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2}} = \frac{L_1 \cdot L_2}{L_1 + L_2}$$

**MUTUAL INDUCTANCE**

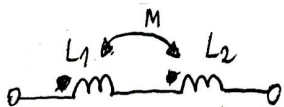

the letter symbol of mutual inductance: M

the unit of mutual inductance: henry

the unit symbol: H

mutual inductance occurs when inductors are placed in close proximity to one another and share a common magnetic flux

$X_M$  - mutual reactance


$X_M = \omega M$   $\omega = 2\pi f$

the unit of mutual reactance: ohm [ $\Omega$ ]

$Z = jX_M = j\omega M$

$M = k \cdot \sqrt{L_1 \cdot L_2}$  k - coefficient of coupling ( $0 \leq k \leq 1$ )

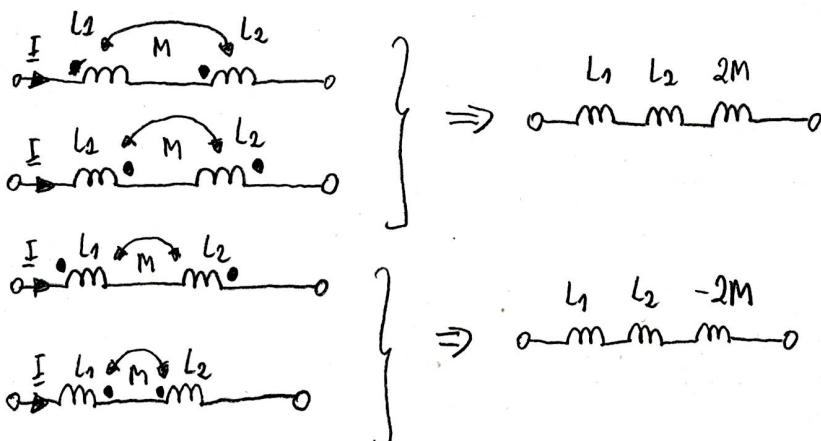**INDUCTORS IN SERIES WITH MUTUAL INDUCTANCE**




\* the coefficient k is an indication of how much flux in one coil is linked with the other coil

\* if all the flux in one coil reaches the other coil, then we have 100% coupling and  $k=1$

\* if there is no coupling  $k=0$

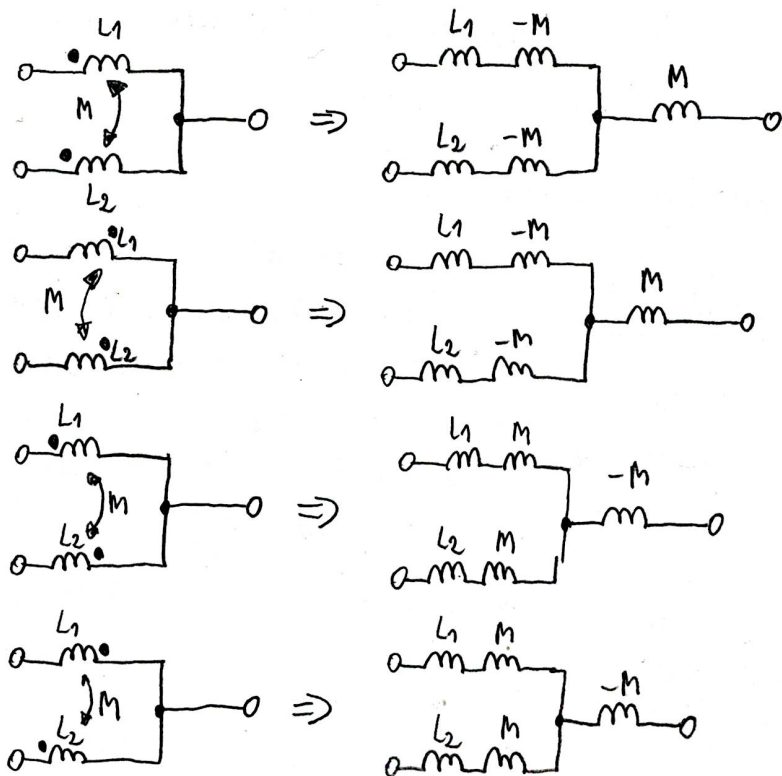
## ELIMINATION OF COUPLING IN ELEMENTS HAVING A COMMON NODE



### PROBLEM #1


Eliminate couplings and calculate the equivalent inductance of the circuits shown in the figures.  $L_1=0.1\text{H}$ ,  $L_2=0.2\text{H}$ ,  $L_3=0.4\text{H}$ ,  $M_{12}=0.1\text{H}$ ,  $M_{23}=0.25\text{H}$ ,  $M_{13}=0.2\text{H}$ .

a)


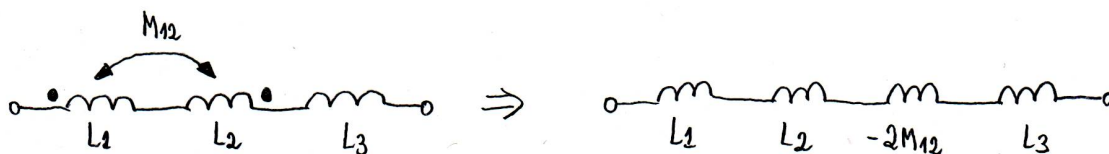


$$L_{eq} = L_1 + L_2 - 2M_{12} + L_3 = 0.1 + 0.2 - 2 \cdot 0.1 + 0.4 = \boxed{0.5\text{H}}$$

b)

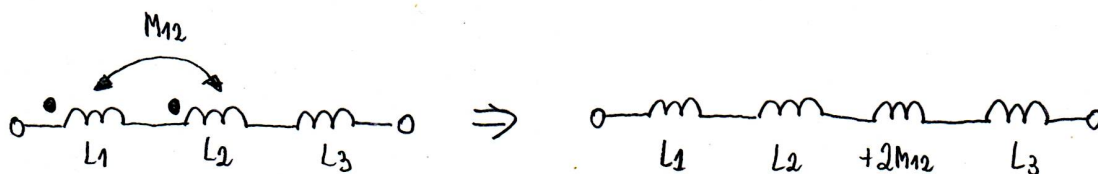

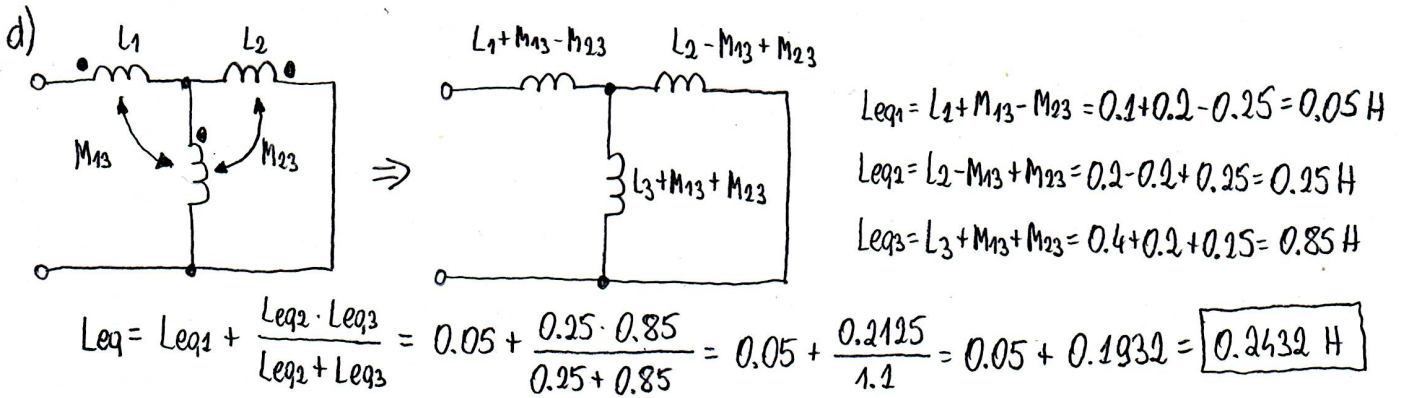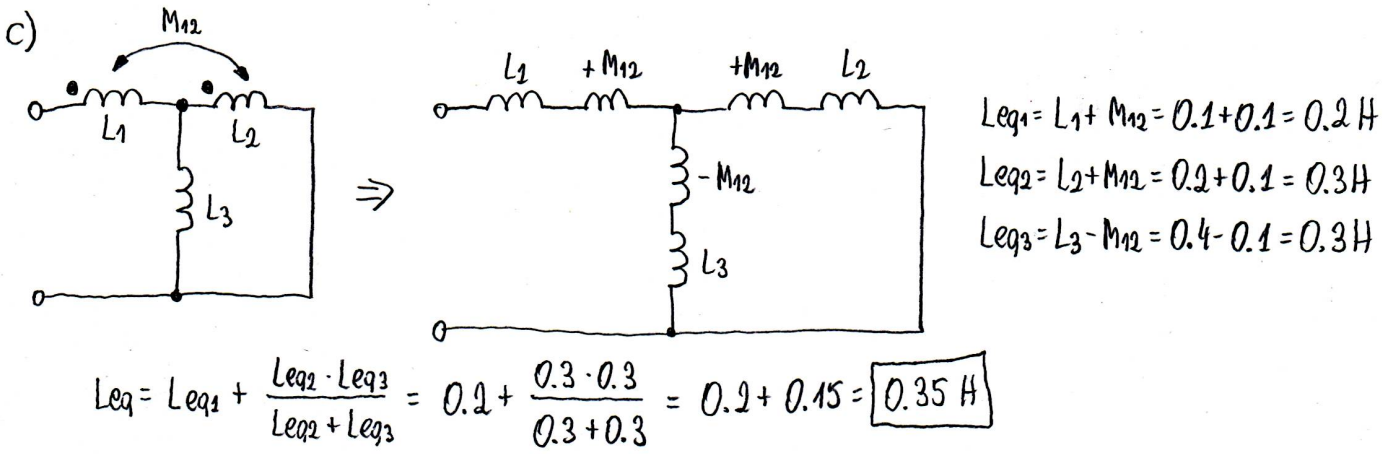
$$L_{eq} = L_1 + L_2 + 2M_{12} + L_3 = 0.1 + 0.2 + 2 \cdot 0.1 + 0.4 = \boxed{0.9\text{H}}$$



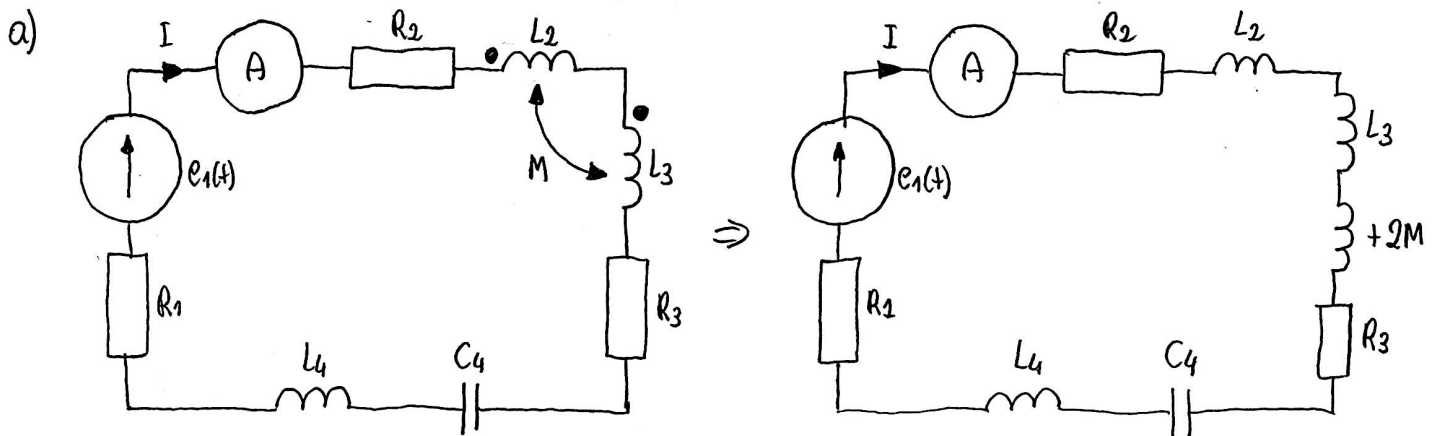
### PROBLEM #2

Calculate ammeter readings in the circuits shown in the figures.  $M = 0.1 \text{ H}$   
 $e_1(t) = 100\sqrt{2} \sin(100t + 90^\circ) \text{ V}$ ,  $R_1 = 15 \Omega$ ,  $R_2 = 30 \Omega$ ,  $L_2 = 0.1 \text{ H}$ ,  $L_3 = 0.4 \text{ H}$ ,  $R_3 = 15 \Omega$ ,  $C_4 = 500 \mu\text{F}$ ,  $L_4 = 0.3 \text{ H}$ .



Elimination of coupling

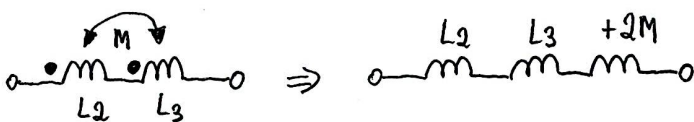

$$Z = R_1 + jX_{L2} + jX_{L3} + 2jX_M + R_3 + jX_{L4} - jX_{C4} + R_2$$

$$Z = 30 + j10 + j40 + j20 + 15 + j30 - j20 + 15 = (60 + j80) \Omega$$

$$I = \frac{U}{Z} = \frac{j100}{60 + j80} = (0.8 + j0.6) \text{ A}$$

$$I_A = |I| = \sqrt{0.8^2 + 0.6^2} = \boxed{1 \text{ A}}$$

$$E_1 = 100 (\cos 90^\circ + j \sin 90^\circ) = j100 \text{ V}$$


$$X_{L2} = \omega L_2 = 100 \cdot 0.1 = 10 \Omega$$

$$X_{L3} = \omega L_3 = 100 \cdot 0.4 = 40 \Omega$$


$$X_M = \omega M = 100 \cdot 0.1 = 10 \Omega$$

$$X_{L4} = \omega L_4 = 100 \cdot 0.3 = 30 \Omega$$
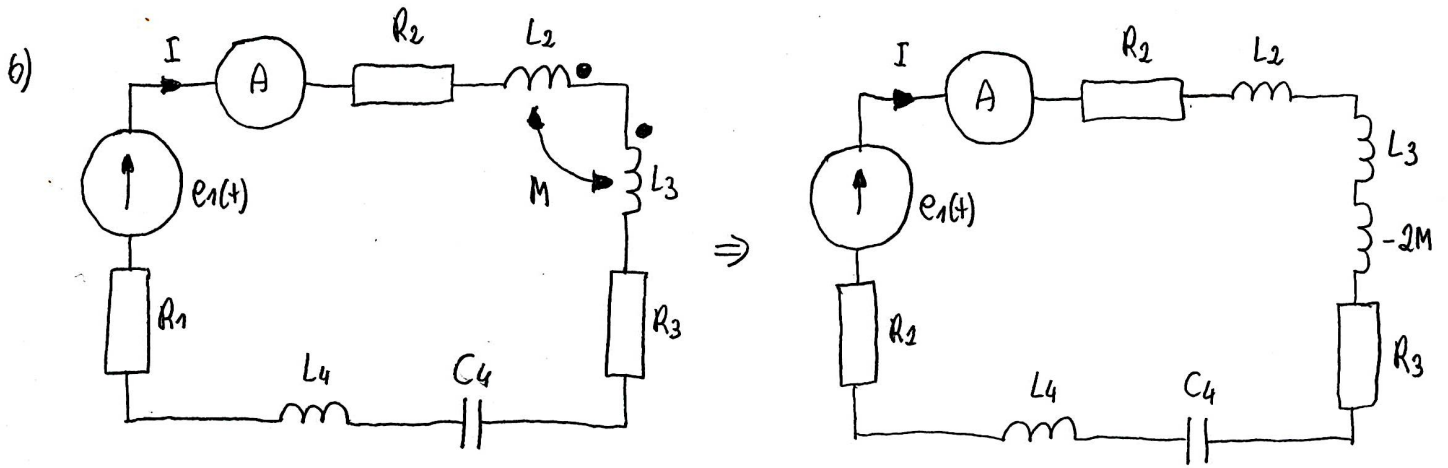
$$X_{C4} = \frac{1}{\omega C_4} = \frac{1}{100 \cdot 500 \cdot 10^{-6}} = 20 \Omega$$



Elimination of coupling

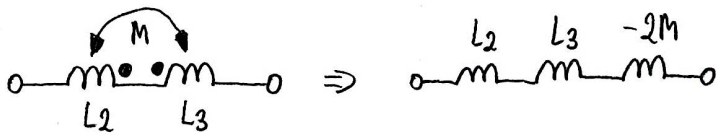

$$Z = R_1 + R_2 + jX_{L2} + jX_{L3} - j2X_M + R_3 - jX_{C4} + jX_{L4} = 15 + 30 + j10 + j40 - j20 + 15 - j20 + j30 = (60 + j40) \Omega$$

$$\underline{I} = \frac{U}{Z} = \frac{j100}{60 + j40} = (0.7682 + j1.1538) \text{ A} \quad I_A = |\underline{I}| = \sqrt{0.7682^2 + 1.1538^2} = \boxed{1.39 \text{ A}}$$