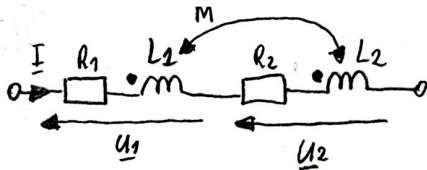



INDUCTORS IN SERIES WITH MUTUAL COUPLING



$$\begin{aligned} \underline{U}_1 &= R_1 \underline{I} + j\omega L_1 \underline{I} + j\omega M \underline{I} \\ \underline{U}_2 &= R_2 \underline{I} + j\omega L_2 \underline{I} + j\omega M \underline{I} \end{aligned}$$

→ +jωM when current enters the dots in the both inductors
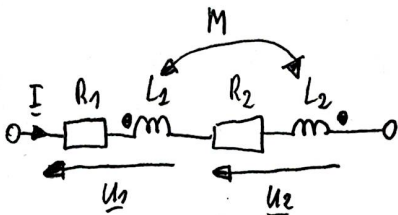
$$\underline{U} = \underline{U}_1 + \underline{U}_2 = (R_1 + R_2 + j\omega L_1 + j\omega L_2 + j2\omega M) \underline{I}$$




$$\begin{aligned} \underline{U}_1 &= R_1 \underline{I} + j\omega L_1 \underline{I} - j\omega M \underline{I} \\ \underline{U}_2 &= R_2 \underline{I} + j\omega L_2 \underline{I} - j\omega M \underline{I} \end{aligned}$$

→ -jωM when current enters a dot in one inductor and leaves a dot in other inductor


$$\underline{U} = \underline{U}_1 + \underline{U}_2 = (R_1 + R_2 + j\omega L_1 + j\omega L_2 - j2\omega M) \underline{I}$$

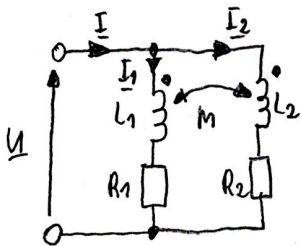INDUCTORS IN PARALLEL WITH MUTUAL COUPLING



$$\begin{cases} \underline{I} = \underline{I}_1 + \underline{I}_2 \\ \underline{U} = R_1 \underline{I}_1 + j\omega L_1 \underline{I}_1 + j\omega M \underline{I}_2 \\ \underline{U} = R_2 \underline{I}_2 + j\omega L_2 \underline{I}_2 + j\omega M \underline{I}_1 \end{cases}$$

→ +jωM when both currents enter the dots

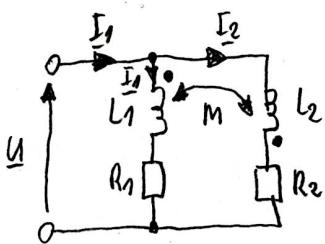


$$\begin{cases} \underline{I} = \underline{I}_1 + \underline{I}_2 \\ \underline{U} = R_1 \underline{I}_1 + j\omega L_1 \underline{I}_1 - j\omega M \underline{I}_2 \\ \underline{U} = R_2 \underline{I}_2 + j\omega L_2 \underline{I}_2 - j\omega M \underline{I}_1 \end{cases}$$

→ -jωM when one current enters a dot and the other current leaves a dot

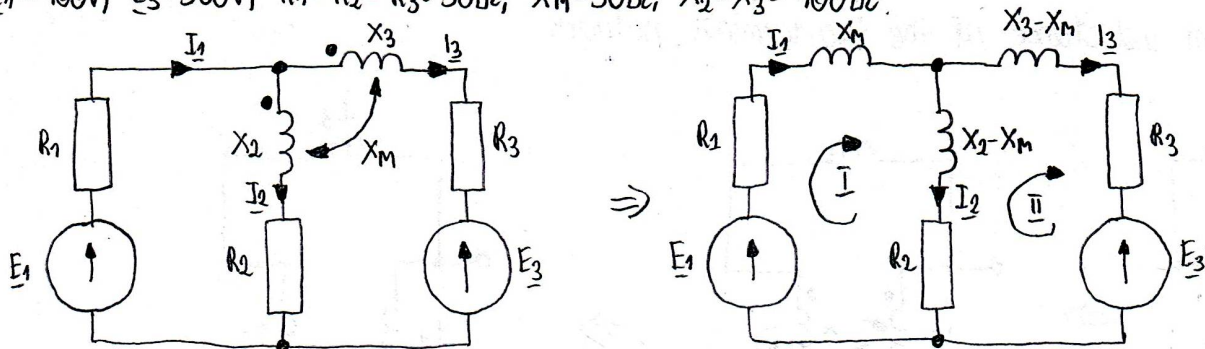PROBLEM #1

Calculate the currents in all branches of the circuit presented in the figure.
 $E_1 = 100V$, $E_3 = 500V$, $R_1 = R_2 = R_3 = 50\Omega$, $X_M = 50\Omega$, $X_2 = X_3 = 100\Omega$.



Method 1 (Elimination of coupling)

$$\begin{cases} \underline{I}_I (R_1 + R_2 + jX_M + jX_2 - jX_M) - \underline{I}_{II} (R_2 + jX_2 - jX_M) = E_1 \\ -\underline{I}_I (R_2 + jX_2 - jX_M) + \underline{I}_{II} (R_2 + R_3 + jX_2 - jX_M + jX_3 - jX_M) = -E_3 \end{cases}$$

$$\underline{W} = \begin{vmatrix} 2+j2 & -1-j1 \\ -1-j1 & 2+j2 \end{vmatrix} = j6$$

$$\begin{cases} \underline{I}_I (50+50+j100) - \underline{I}_{II} (50+j100-j50) = 100 \\ -\underline{I}_I (50+j100-j50) + \underline{I}_{II} (50+50+j100-j50+j100-j50) = -500 \end{cases}$$

$$\underline{W}_I = \begin{vmatrix} 2 & -1-j1 \\ -10 & 2+j2 \end{vmatrix} = -6-j6$$

$$\underline{I}_I (100+j100) - \underline{I}_{II} (50+j50) = 100 \quad | :50$$

$$-\underline{I}_I (50+j50) + \underline{I}_{II} (100+j100) = -500 \quad | :50$$

$$\underline{W}_{II} = \begin{vmatrix} 2+j2 & 2 \\ -1-j1 & -10 \end{vmatrix} = -18-j18$$

$$\underline{I}_I (2+j2) - \underline{I}_{II} (1+j1) = 2$$

$$-\underline{I}_I (1+j1) + \underline{I}_{II} (2+j2) = -10$$

$$\underline{I}_I = \frac{\underline{W}_I}{\underline{W}} = \frac{-6-j6}{j6} = (-1+j1) \text{ A}$$


$$\underline{I}_1 = \underline{I}_I = \boxed{(-1+j1) \text{ A}}$$

$$\underline{I}_{II} = \frac{\underline{W}_{II}}{\underline{W}} = \frac{-18-j18}{j6} = (-3+j3) \text{ A}$$

$$\underline{I}_2 = \underline{I}_I - \underline{I}_{II} = -1+j1+3-j3 = \boxed{(2-j2) \text{ A}}$$

$$\underline{I}_3 = \underline{I}_{II} = \boxed{(-3+j3) \text{ A}}$$

Method 2 (KCL + KVL)

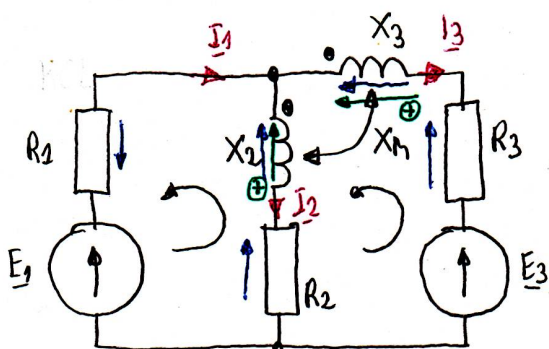

$$\text{KCL: } \underline{I}_1 - \underline{I}_2 - \underline{I}_3 = 0$$

$$\text{KVL: } R_1 \underline{I}_1 + jX_2 \underline{I}_2 + R_2 \underline{I}_2 + jX_M \underline{I}_3 - E_1 = 0$$


$$\text{KVL: } -R_2 \underline{I}_2 - jX_2 \underline{I}_2 + jX_3 \underline{I}_3 + R_3 \underline{I}_3 - jX_M \underline{I}_3 + jX_M \underline{I}_2 + E_3 = 0$$

PROBLEM #2

What should be the power of the Resistor R_1 so that it is not damaged during operation in the circuit shown in the figure.

$$\underline{U} = 10V, R_1 = 10\Omega, X_{L1} = 25\Omega, X_{L2} = 40\Omega, X_M = 10\Omega, X_{C3} = 20\Omega.$$

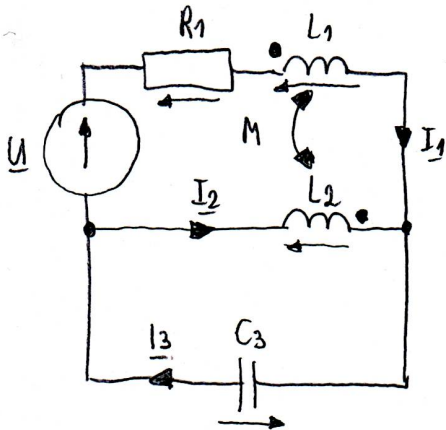Standard resistor power: 0.125W, 0.25W, 0.4W, 0.5W, 0.6W, 0.75W, 1W, 1.2W, 2W, 3W, 5W, 7W, 8W, 9W.



$$\begin{cases} \underline{I}_1 + \underline{I}_2 = \underline{I}_3 & \text{①} \quad \leftarrow \text{KCL} \\ \underline{U} = R_1 \underline{I}_1 + jX_{L1} \underline{I}_1 - jX_M \underline{I}_2 - jX_{L2} \underline{I}_2 - (-jX_M \underline{I}_1) & \leftarrow \text{KVL} \\ 0 = jX_{L2} \underline{I}_2 - jX_M \underline{I}_1 + (-jX_{C3} \underline{I}_3) & \leftarrow \text{KVL} \end{cases}$$

① $-jX_M$ when one current enters a dot and the other current leaves a dot

$+jX_M$ when both currents enter the dot (or both leave the dots)

$$10 \underline{I}_1 + j25 \underline{I}_1 - j10 \underline{I}_2 - j40 \underline{I}_2 + j10 \underline{I}_1 = 10$$

$$(10 + j35) \underline{I}_1 - j50 \underline{I}_2 = 10$$

$$j40 \underline{I}_2 - j10 \underline{I}_1 - j20 \underline{I}_3 = 0$$

$$\leftarrow \underline{I}_3 = \underline{I}_1 + \underline{I}_2$$

$$j40 \underline{I}_2 - j10 \underline{I}_1 - j20 \underline{I}_1 - j20 \underline{I}_2 = 0$$

$$-j30 \underline{I}_1 + j20 \underline{I}_2 = 0$$

$$j20 \underline{I}_2 = j30 \underline{I}_1 \quad / : j20$$

$$\underline{I}_2 = \frac{3}{2} \underline{I}_1$$

$$(10 + j35) \underline{I}_1 - j50 \cdot \frac{3}{2} \underline{I}_1 = 10$$

$$10 + j35 \underline{I}_1 - j75 \underline{I}_1 = 10$$

$$(10 - j40) \underline{I}_1 = 10$$

$$\underline{I}_1 = \frac{10}{10 - j40} = (0.0588 + j0.2353)A$$

$$\begin{aligned} \underline{U}_1 &= R_1 \underline{I}_1 = 10(0.0588 + j0.2353) = \\ &= (0.588 + j2.353)V \end{aligned}$$

$$\begin{aligned} \underline{S}_1 &= \underline{U}_1 \cdot \underline{I}_1^* = (0.588 + j2.353)(0.0588 - j0.2353) = \\ &= 0.5878 \text{ VA} \end{aligned}$$


$$P_n = \text{Re} \{ \underline{S}_1 \} = \boxed{0.5878 \text{ W}}$$

The power of resistor R_1 should be $\boxed{0.6 \text{ W}}$.

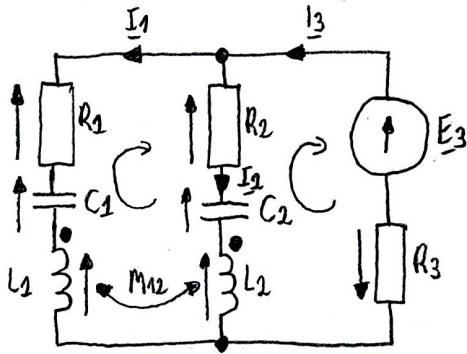PROBLEM #3

(this problem was not solved during the class)

Write equations according to KCL and KVL for the circuit presented in the figure.





$$\begin{aligned} \text{KCL} &\rightarrow \begin{cases} I_1 + I_2 = I_3 \end{cases} \\ \text{KVL} &\rightarrow \begin{cases} R_1 \cdot I_1 - jX_{C1} \cdot I_1 + jX_{L1} \cdot I_1 - R_2 \cdot I_2 + jX_{C2} \cdot I_2 - jX_{L2} \cdot I_2 \\ + jX_{M12} \cdot I_2 - jX_{M12} \cdot I_1 = 0 \end{cases} \\ \text{KVL} &\rightarrow \begin{cases} R_2 \cdot I_2 - jX_{C2} \cdot I_2 + jX_{L2} \cdot I_2 + R_3 \cdot I_3 + jX_{M12} \cdot I_1 - E_3 = 0 \end{cases} \end{aligned}$$

PROBLEM #4

(this problem was not solved during the class)

Calculate meter readings in the circuit shown in the figure.

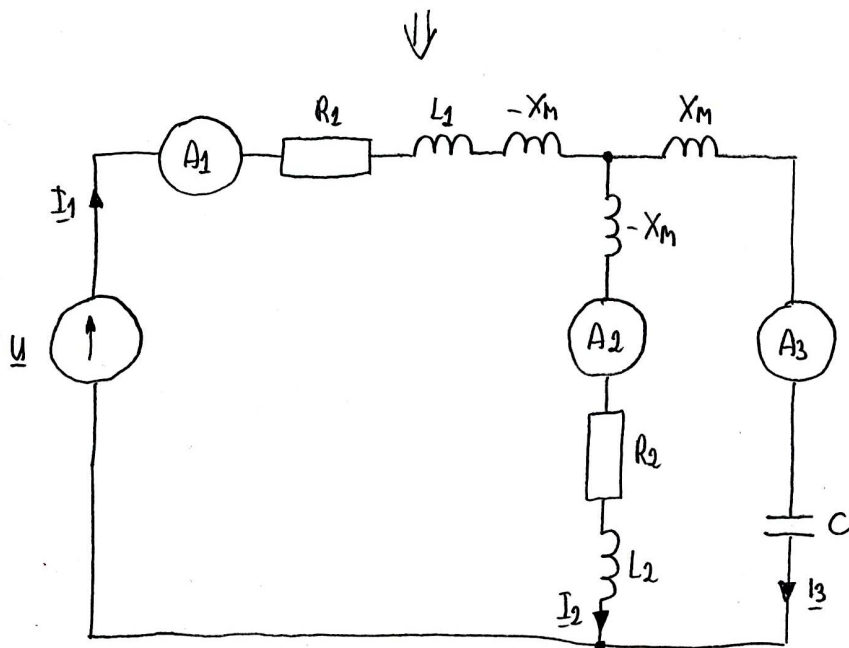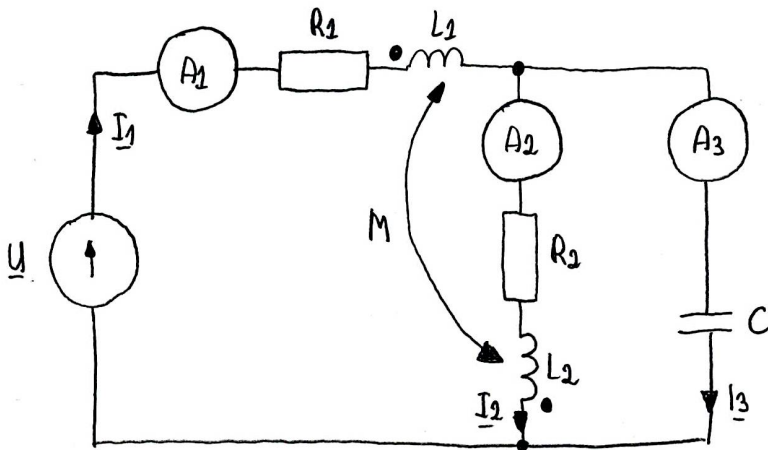$U = 100V, R_1 = R_2 = 15\Omega, X_{L1} = X_{L2} = 30\Omega, X_M = X_C = 10\Omega.$



$$\begin{aligned} Z_1 &= R_1 + jX_{L1} - jX_M = 15 + j30 - j10 = \\ &= (15 + j20)\Omega \end{aligned}$$

$$\begin{aligned} Z_2 &= R_2 + jX_{L2} - jX_M = 15 + j30 - j10 = \\ &= (15 + j20)\Omega \end{aligned}$$

$$Z_3 = jX_M - jX_C = j10 - j10 = 0\Omega$$

because $Z_3 = 0\Omega$ then $I_{A2} = 0A$ and $I_1 = I_3, I_{A1} = I_{A3} \quad Z_{eq} = Z_1 = (15 + j20)\Omega$

$$I_1 = \frac{U}{Z_{eq}} = \frac{100}{15 + j20} = (2.4 - j3.2)A = 4e^{-j53.1^\circ}A \quad \Rightarrow \quad I_{A1} = I_{A3} = |I_1| = 4A$$