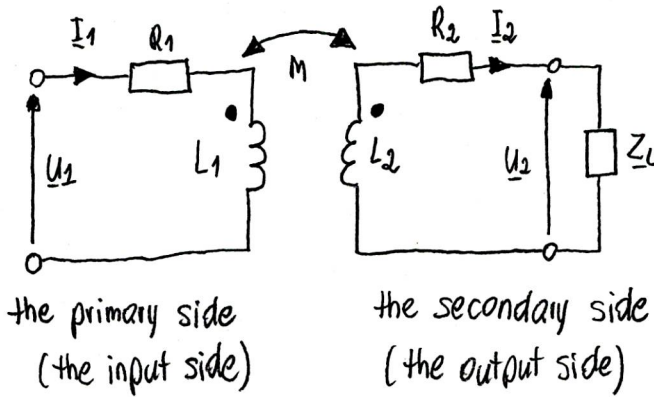


**AIR-CORE TRANSFORMER**

\* circuit diagram



$\underline{U}_1$  - primary voltage  
 $\underline{I}_1$  - primary current  
 $\underline{U}_2$  - secondary voltage  
 $\underline{I}_2$  - secondary current  
 $\underline{Z}_L$  - load impedance

\* equations

$$\begin{cases} R_1 \underline{I}_1 + j\omega L_1 \underline{I}_1 - j\omega M \underline{I}_2 = \underline{U}_1 \\ R_2 \underline{I}_2 + j\omega L_2 \underline{I}_2 - j\omega M \underline{I}_1 + \underline{Z}_L \underline{I}_2 = 0 \end{cases}$$

\* equations (open-circuited output),  $\underline{Z}_L \rightarrow \infty$ ,  $\underline{I}_2 = 0$


$$\begin{cases} R_1 \underline{I}_1 + j\omega L_1 \underline{I}_1 = \underline{U}_1 \\ -j\omega M \underline{I}_1 = \underline{U}_2 \end{cases}$$

\* equations (short-circuited output),  $\underline{Z}_L = 0$ ,  $\underline{U}_2 = 0$

$$\begin{cases} R_1 \underline{I}_1 + j\omega L_1 \underline{I}_1 - j\omega M \underline{I}_2 = \underline{U}_1 \\ R_2 \underline{I}_2 + j\omega L_2 \underline{I}_2 - j\omega M \underline{I}_1 = 0 \end{cases}$$
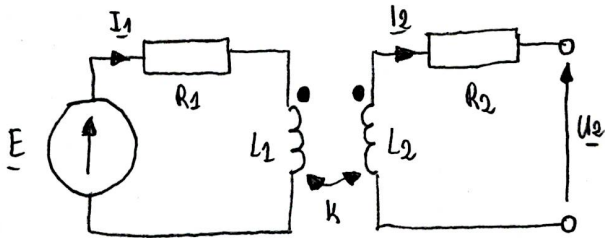
# PROBLEM #1

The air transformer was connected to the voltage source  $E$ . Calculate the readings of:  
 a) ammeter, b) voltmeter, connected to the terminals of the secondary winding.  
 $E = 200V$ ,  $k = 0.8$ ,  $R_1 = R_2 = 20\Omega$ ,  $X_{L1} = X_{L2} = 40\Omega$ .



$$M = k \sqrt{L_1 \cdot L_2} \quad X_m = k \sqrt{X_{L1} \cdot X_{L2}} = 0.8 \sqrt{40^2} = 0.8 \cdot 40 = 32\Omega$$

$$I_1 = \frac{W_I}{U} = \frac{4000 + j8000}{-176 + j1600} = (4.6685 - j30.135)A$$

$$I_2 = \frac{W_{II}}{U} = \frac{j6400}{-176 + j1600} = (3.9522 - j0.4347)A$$

a) ammeter - short circuit in the secondary winding


$$\begin{cases} R_1 I_1 + jX_{L1} I_1 - jX_m I_2 = E \\ -jX_m I_1 + R_2 I_2 + jX_{L2} I_2 = 0 \end{cases} \quad W = \begin{vmatrix} 20+j40 & -j32 \\ -j32 & 20+j40 \end{vmatrix} = -176 + j1600$$

$$\begin{cases} 20I_1 + j40I_1 - j32I_2 = 200 \\ -j32I_1 + 20I_2 + j40I_2 = 0 \end{cases} \quad W_I = \begin{vmatrix} 200 & -j32 \\ 0 & 20+j40 \end{vmatrix} = 4000 + j8000$$

$$\begin{cases} (20+j40)I_1 - j32I_2 = 200 \\ -j32I_1 + (20+j40)I_2 = 0 \end{cases} \quad W_{II} = \begin{vmatrix} 20+j40 & 200 \\ -j32 & 0 \end{vmatrix} = 0 + j6400$$

$$|I_2| = 3.976A$$

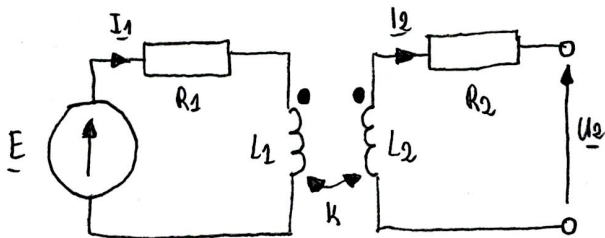b) voltmeter - open circuit in the secondary windings,  $I_2 = 0A$



$$R_1 I_1 + jX_{L1} I_1 = E$$


$$(R_1 + jX_{L1}) I_1 = E \rightarrow I_1 = \frac{E}{R_1 + jX_{L1}} = \frac{200}{20 + j40} = (2 - 4j)A$$

$$U_2 = -jX_m I_1 = j32(2 - 4j) = (128 + j64)V$$

$$|U_2| = 143.1084V$$
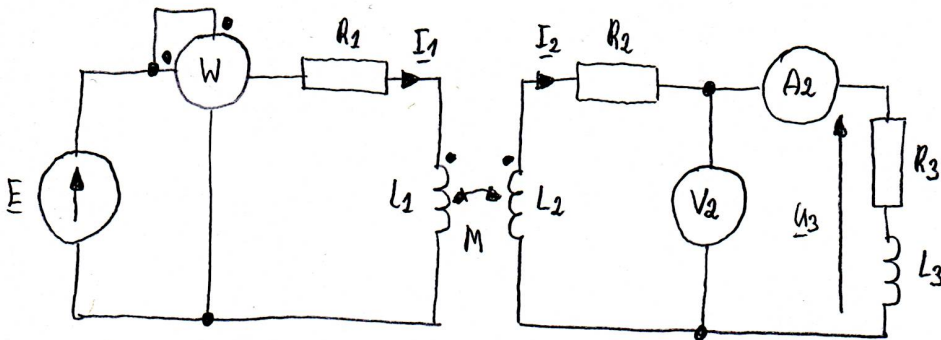
## PROBLEM #2

For the circuit below determine the results of measurements.  
 $E = 230V$ ,  $R_1 = X_{L2} = X_M = 10\Omega$ ,  $R_2 = 5\Omega$ ,  $R_3 = X_{L1} = X_{L3} = 20\Omega$ .



$$\begin{cases} R_1 \underline{I}_1 + jX_{L1} \underline{I}_1 - jX_M \underline{I}_2 = \underline{E} \\ R_2 \underline{I}_2 + jX_{L2} \underline{I}_2 - jX_M \underline{I}_1 + R_3 \underline{I}_2 + jX_{L3} \underline{I}_2 = 0 \end{cases}$$

$$W = \begin{vmatrix} 10+j20 & -j10 \\ -j10 & 25+j30 \end{vmatrix} = -250 + j800$$

$$\begin{cases} 10\underline{I}_1 + j20\underline{I}_1 - j10\underline{I}_2 = 230 \\ 5\underline{I}_2 + j10\underline{I}_2 - j10\underline{I}_1 + 20\underline{I}_2 + j20\underline{I}_2 = 0 \end{cases}$$

$$W_1 = \begin{vmatrix} 230 & -j10 \\ 0 & 25+j30 \end{vmatrix} = 5750 + j6800$$

$$\begin{cases} (10+j20) \underline{I}_1 + (-j10) \underline{I}_2 = 230 \\ (-j10) \underline{I}_1 + (25+j30) \underline{I}_2 = 0 \end{cases}$$

$$W_2 = \begin{vmatrix} 10+j20 & 230 \\ -j10 & 0 \end{vmatrix} = j2300$$

$$\underline{I}_1 = \frac{W_1}{W} = \frac{5750 + j6800}{-250 + j800} = (5.81 - j9.00) A$$

$$\underline{I}_2 = \frac{W_2}{W} = \frac{j2300}{-250 + j800} = (2.62 - j0.82) A$$

$$P_W = \operatorname{Re}[\underline{E} \cdot \underline{I}_1^*] = \operatorname{Re}[230 \cdot (5.81 + j9.00)] = \operatorname{Re}[1336.3 + j2070] = \boxed{1336.3 \text{ W}}$$


$$I_{A2} = |\underline{I}_2| = \sqrt{2.62^2 + 0.82^2} = \boxed{2.75 \text{ A}}$$

$$U_{V2} = |\underline{U}_3| = |(R_3 + jX_{L3}) \cdot \underline{I}_2| = |(20 + j20) \cdot (2.62 - j0.82)| = |68.8 + j36| = \boxed{77.65 \text{ V}}$$
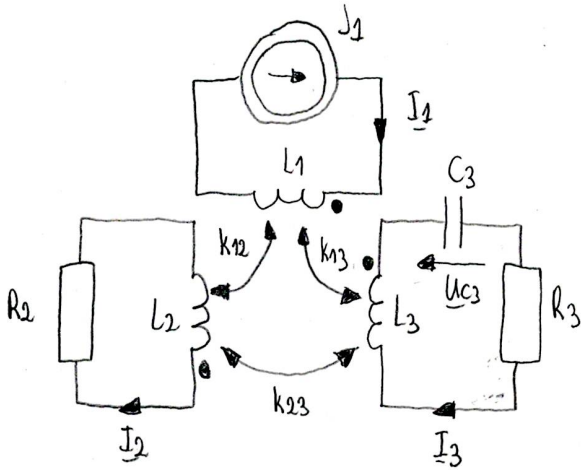
### PROBLEM #3

The maximum voltage across capacitor  $C_3$  must not exceed 75 V. Check whether this condition is met in the circuit shown in the diagram.

$X_{L1} = 80 \Omega$ ,  $R_2 = 10 \Omega$ ,  $X_{L2} = 20 \Omega$ ,  $R_3 = 10 \Omega$ ,  $X_{L3} = 20 \Omega$ ,  $X_{C3} = 10 \Omega$ ,  $k_{12} = 0.5$ ,  $k_{13} = 0.75$ ,  $k_{23} = 0.5$ ,  $I_1 = 3 \text{ A}$



$$M = k \cdot \sqrt{L_1 \cdot L_2} \cdot \omega$$

$$\omega M = k \cdot \sqrt{\omega L_1 \cdot \omega L_2}$$

$$X_M = k \cdot \sqrt{X_{L1} \cdot X_{L2}}$$

$$X_{M12} = k_{12} \cdot \sqrt{X_{L1} \cdot X_{L2}} = 0.5 \cdot \sqrt{80 \cdot 20} = 20 \Omega$$

$$X_{M13} = k_{13} \cdot \sqrt{X_{L1} \cdot X_{L3}} = 0.75 \cdot \sqrt{80 \cdot 20} = 30 \Omega$$

$$X_{M23} = k_{23} \cdot \sqrt{X_{L2} \cdot X_{L3}} = 0.5 \cdot \sqrt{20 \cdot 20} = 10 \Omega$$

$$\begin{cases} \underline{I}_1 = 3 \text{ A} \\ R_2 \cdot \underline{I}_2 + jX_{L2} \cdot \underline{I}_2 - \underline{I}_1 jX_{M12} + \underline{I}_3 jX_{M23} = 0 \\ R_3 \cdot \underline{I}_3 + jX_{L3} \cdot \underline{I}_3 - jX_{C3} \cdot \underline{I}_3 - \underline{I}_1 jX_{M13} + \underline{I}_2 jX_{M23} = 0 \end{cases}$$

$$\begin{cases} 10 \underline{I}_2 + j20 \underline{I}_2 - j20 \cdot 3 + j10 \cdot \underline{I}_3 = 0 \\ 10 \underline{I}_3 + j20 \underline{I}_3 - j10 \underline{I}_3 - j30 \cdot 3 + j10 \underline{I}_2 = 0 \end{cases}$$

$$\begin{cases} (10 + j20) \underline{I}_2 + (j10) \underline{I}_3 = j60 \quad | : 10 \\ (j10) \underline{I}_2 + (10 + j10) \underline{I}_3 = j80 \quad | : 10 \end{cases}$$

$$\begin{cases} (1 + j2) \underline{I}_2 + (j1) \underline{I}_3 = j6 \\ (j1) \underline{I}_2 + (1 + j1) \underline{I}_3 = j8 \end{cases}$$

$$D = \begin{vmatrix} 1+j2 & j1 \\ j1 & 1+j1 \end{vmatrix} = j3$$

$$D_2 = \begin{vmatrix} j6 & j1 \\ j8 & 1+j1 \end{vmatrix} = 3 + j6$$

$$D_3 = \begin{vmatrix} 1+j2 & j6 \\ j1 & j8 \end{vmatrix} = -12 + j8$$

$$\underline{I}_2 = \frac{D_2}{D} = \frac{3 + j6}{j3} = (2 - j1) \text{ A}$$

$$\underline{I}_3 = \frac{D_3}{D} = \frac{-12 + j8}{j3} = (3 + 4j) \text{ A}$$

$$\underline{U}_{C3} = -jX_{C3} \cdot \underline{I}_3 = -j10 \cdot (3 + 4j) = (40 - 30j) \text{ V}$$

$$|U_{C3}| = \sqrt{50} \text{ V} < 75 \text{ V}$$

The condition is met - the voltage across capacitor  $C_3$  is less than 75 V.