
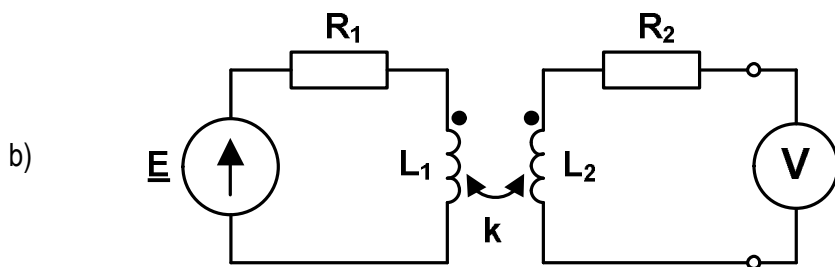


Module name: **Electrical Circuits 2**
 Module ID: **IS-FEE-10085S**
 Module type: **Class**
 Semester: **summer 2024/2025**
 Instructor: **Jarosław Forenc, j.forenc@pb.edu.pl**

Class 4 (25.03.2025)

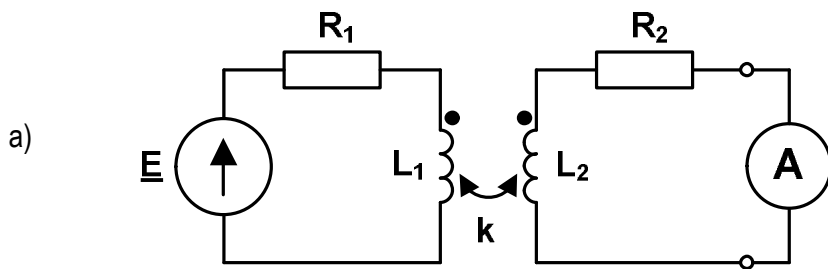
1. The air transformer was connected to the voltage source \underline{E} . Calculate the **readings** of:
 a) **ammeter**, b) **voltmeter**,
 connected to the terminals of the secondary winding.

$\underline{E} = 200 \text{ V}$, $k = 0.8$, $R_1 = R_2 = 20 \ \Omega$, $X_{L1} = X_{L2} = 40 \ \Omega$.



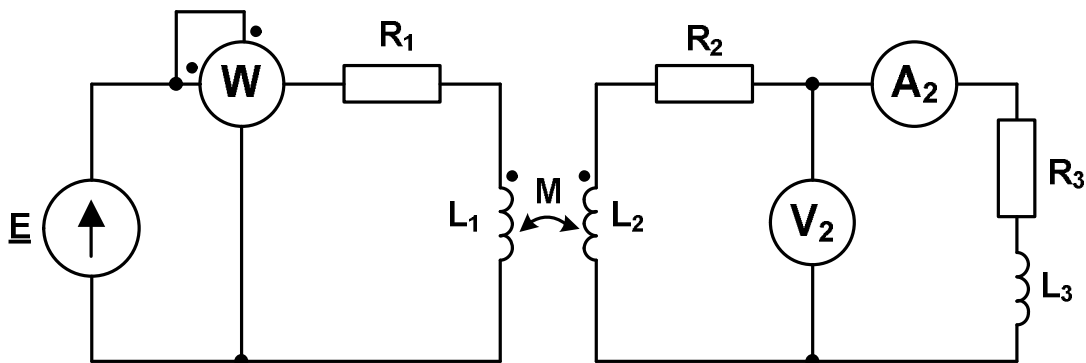
2. For the circuit below determine the results of measurements.

$\underline{E} = 230 \text{ V}$, $R_1 = X_{L2} = X_M = 10 \ \Omega$, $R_2 = 5 \ \Omega$, $R_3 = X_{L1} = X_{L3} = 20 \ \Omega$.



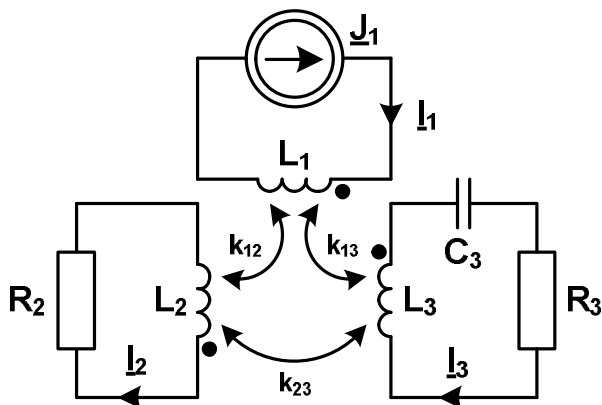3. The maximum voltage across capacitor C_3 must not exceed **75 V**. Check whether this condition is met in the circuit shown in the diagram.

$X_{L1} = 80 \Omega$, $R_2 = 10 \Omega$, $X_{L2} = 20 \Omega$, $R_3 = 10 \Omega$, $X_{L3} = 20 \Omega$, $X_{C3} = 10 \Omega$,
 $k_{12} = 0.5$, $k_{13} = 0.75$, $k_{23} = 0.5$, $\underline{J}_1 = 3 \text{ A}$



25.03.2025

Jarosław Forenc, PhD

j.forenc@pb.edu.pl