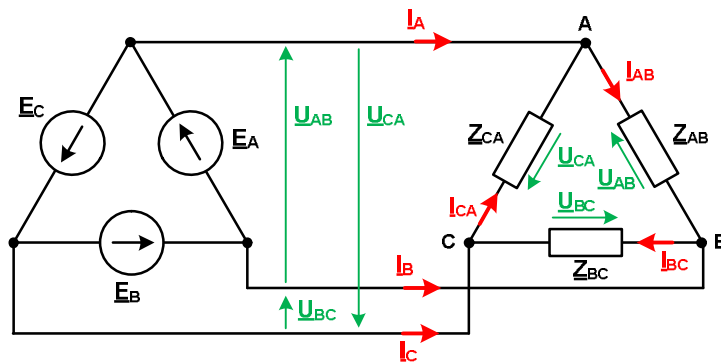


ELECTRICAL CIRCUITS 2 - CLASS 7 (15.04.2025)

Balanced Delta-Delta (Δ - Δ) connection



- Symbols in the circuit:

$\underline{E}_A, \underline{E}_B, \underline{E}_C$ - phase voltages of the generator

$\underline{U}_{AB}, \underline{U}_{BC}, \underline{U}_{CA}$ - phase voltages of the load

$\underline{I}_A, \underline{I}_B, \underline{I}_C$ - the line currents

$\underline{I}_{AB}, \underline{I}_{BC}, \underline{I}_{CA}$ - the phase currents

$\underline{Z}_{AB}, \underline{Z}_{BC}, \underline{Z}_{CA}$ - the load impedances

- Balanced load:

$$\underline{Z}_A = \underline{Z}_B = \underline{Z}_C = \underline{Z}$$

- Phase voltages of the load are equal to phase voltages of the generator:

$$\underline{U}_{AB} = \underline{E}_A, \quad \underline{U}_{BC} = \underline{E}_B, \quad \underline{U}_{CA} = \underline{E}_C$$

the complex values (phasors): $\underline{U}_{AB} + \underline{U}_{BC} + \underline{U}_{CA} = 0$

the rms (effective) values: $U_{AB} = U_{BC} = U_{CA}$

- The phase currents:

$$\underline{I}_{AB} = \frac{\underline{U}_{AB}}{\underline{Z}_{AB}}, \quad \underline{I}_{BC} = \frac{\underline{U}_{BC}}{\underline{Z}_{BC}}, \quad \underline{I}_{CA} = \frac{\underline{U}_{CA}}{\underline{Z}_{CA}}$$

the complex values (phasors): $\underline{I}_{AB} + \underline{I}_{BC} + \underline{I}_{CA} = 0$

the rms (effective) values: $I_{AB} = I_{BC} = I_{CA}$

- The line currents:

$$\underline{I}_A = \underline{I}_{AB} - \underline{I}_{CA}$$


$$\underline{I}_B = \underline{I}_{BC} - \underline{I}_{AB}$$

$$\underline{I}_C = \underline{I}_{CA} - \underline{I}_{BC}$$

the complex values (phasors): $\underline{I}_A + \underline{I}_B + \underline{I}_C = 0$

the rms (effective) values: $I_A = I_B = I_C$

- Phasor diagram of currents:

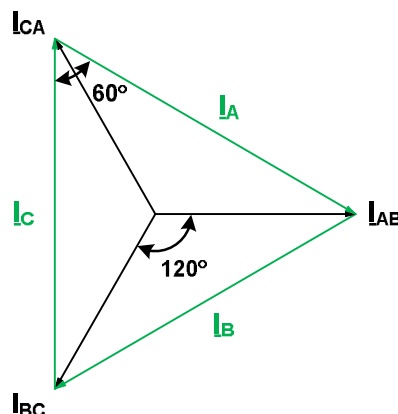

- Active, reactive and apparent power:

$$P = U_{AB} \cdot I_{AB} \cdot \cos \varphi_{AB} + U_{BC} \cdot I_{BC} \cdot \cos \varphi_{BC} + U_{CA} \cdot I_{CA} \cdot \cos \varphi_{CA}$$

$$Q = U_{AB} \cdot I_{AB} \cdot \sin \varphi_{AB} + U_{BC} \cdot I_{BC} \cdot \sin \varphi_{BC} + U_{CA} \cdot I_{CA} \cdot \sin \varphi_{CA}$$

$$S = U_{AB} \cdot I_{AB} + U_{BC} \cdot I_{BC} + U_{CA} \cdot I_{CA}$$

Complex power:

$$\underline{S} = \underline{U}_{AB} \cdot \underline{I}_{AB}^* + \underline{U}_{BC} \cdot \underline{I}_{BC}^* + \underline{U}_{CA} \cdot \underline{I}_{CA}^*$$

$$\underline{S} = P + jQ$$

$$P = \operatorname{Re}\{\underline{S}\}, \quad Q = \operatorname{Im}\{\underline{S}\}, \quad S = \|\underline{S}\|$$

in the case of balanced load:

$$U_{AB} = U_{BC} = U_{CA} = U_{ph}, \quad I_{AB} = I_{BC} = I_{CA} = I_{ph}, \quad \cos \varphi_{AB} = \cos \varphi_{BC} = \cos \varphi_{CA} = \cos \varphi_{ph}$$

then:


$$P = 3 \cdot U_{ph} \cdot I_{ph} \cdot \cos \varphi_{ph}, \quad Q = 3 \cdot U_{ph} \cdot I_{ph} \cdot \sin \varphi_{ph}, \quad S = 3 \cdot U_{ph} \cdot I_{ph}$$

ELECTRICAL CIRCUITS 2 - CLASS NO. 7 (15.04.2025)**PROBLEM #1**

The line-to-line voltage of a balanced 3-phase distribution line is $U_{LL} = 380 \text{ V rms}$.

The load impedance per phase is $Z_L = (30 + j20) \Omega$. Calculate the line currents and the active power of the load for the following configurations of load impedance:

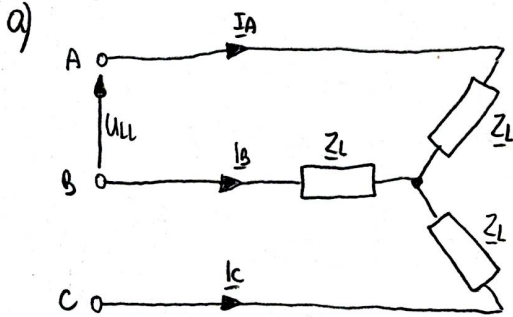a) a wye-connected system, b) a delta-connected system




$$U_{ph} = \frac{U_{LL}}{\sqrt{3}} = \frac{380}{\sqrt{3}} = 218.3831 \text{ V}$$

$$I_{ph} = \frac{U_{ph}}{Z_L} = \frac{218.3831}{30 + j20} = (5.0628 - j3.3753) \text{ A} = 6.08 e^{-j33.7^\circ} \text{ A}$$

$$I_A = I_B = I_C = I_{ph} = \boxed{6.08 \text{ A}}$$

$$S = 3 \cdot U_{ph} \cdot I_{ph}^* = 3 \cdot 218.3831 \cdot (5.0628 + j3.3753) = (3332.3 + j2221.5) \text{ VA}$$
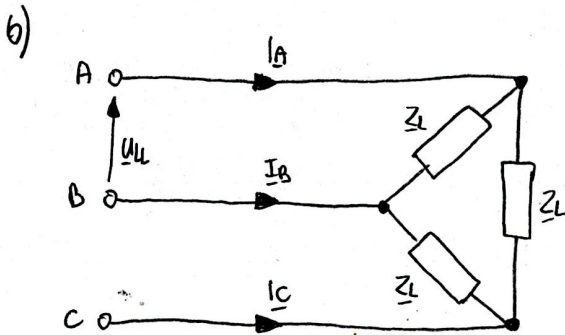
$$P = \operatorname{Re}\{S\} = \boxed{3332.3 \text{ W}}$$



$$U_{ph} = U_{LL} = 380 \text{ V}$$

$$I_{ph} = \frac{U_{ph}}{Z_L} = \frac{380}{30 + j20} = (8.7682 - j5.8462) \text{ A} = 10.5383 e^{-j33.7^\circ}$$


$$S = 3 U_{ph} \cdot I_{ph}^* = 3 \cdot 380 \cdot (8.7682 + j5.8462) = 9996.8 + j6664.6 \text{ VA}$$

$$P = \operatorname{Re}\{S\} = \boxed{9996.8 \text{ W}}$$

$$I_A = I_B = I_C = \sqrt{3} \cdot I_{ph} = \boxed{18.25 \text{ A}}$$

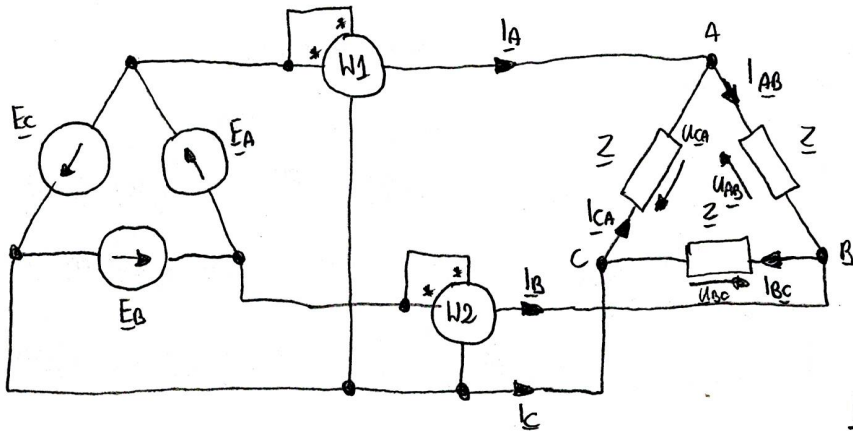PROBLEM #2

In a 3-phase balanced $\Delta-\Delta$ system the source voltage $E_{ph} = 230\text{ V rms}$. The impedance per phase is $Z = (8+j6)\Omega$. Find the line currents, active power of the load and wattmeters readings.



$$E_A = 230e^{j0^\circ} \text{ V} = 230 \text{ V}$$

$$E_B = 230e^{j120^\circ} \text{ V} = -115 - j199.19 \text{ V}$$

$$E_C = 230e^{j240^\circ} \text{ V} = -115 + j199.19 \text{ V}$$

$$U_{AB} = E_A$$

$$U_{BC} = E_B$$

$$U_{CA} = E_C$$

Note: for I_B current, the calculated angle is positive. After changing the angle to negative ($173.13^\circ - 360^\circ = -186.87^\circ$), we can see that the angle between the phase and line current is 30° .

$$I_{AB} = \frac{E_A}{Z} = \frac{230}{8+j6} = (18.4 - j13.8) \text{ A} = 23e^{-j36.87^\circ} \text{ A}$$

$$I_{BC} = \frac{E_B}{Z} = \frac{-115 - j199.19}{8+j6} = (-21.15 - j9.03) \text{ A} = 23e^{-j156.87^\circ} \text{ A}$$

$$I_{CA} = \frac{E_C}{Z} = \frac{-115 + j199.19}{8+j6} = (2.75 + j22.83) \text{ A} = 23e^{j83.13^\circ} \text{ A}$$

$$I_A = I_{AB} - I_{CA} = 18.4 - j13.8 - 2.75 - j22.83 = (15.65 - j36.63) \text{ A} = 39.84e^{-j66.87^\circ} \text{ A}$$

$$I_B = I_{BC} - I_{AB} = -21.15 - j9.03 - 18.4 + j13.8 = (-39.55 + j4.77) \text{ A} = 39.84e^{j173.13^\circ} \text{ A} = 39.84e^{-j186.87^\circ} \text{ A}$$

$$I_C = I_{CA} - I_{BC} = 2.75 + j22.83 + 21.15 + j9.03 = (23.9 + j31.87) \text{ A} = 39.84e^{j53.13^\circ} \text{ A} = 39.84e^{-j306.87^\circ} \text{ A}$$

$$S_1 = (-E_C) \cdot I_A^* = (115 - j199.19) \cdot (15.65 + j36.63) = \underbrace{(8086.76 + j1095.98)}_{P_{W1}} \text{ VA} \rightarrow P_{W1} = 8086.76 \text{ W}$$

$$S_2 = E_B \cdot I_B^* = (-115 - j199.19) \cdot (-39.55 - j4.77) = \underbrace{(3589.23 + j8426.02)}_{P_{W2}} \text{ VA} \rightarrow P_{W2} = 3589.23 \text{ W}$$

$$S = E_A \cdot I_A^* + E_B \cdot I_B^* + E_C \cdot I_C^* = 230 \cdot (18.4 - j13.8) + (-115 - j199.19) \cdot (-21.15 - j9.03) + (-115 + j199.19) \cdot (2.75 + j22.83)$$


$$P_{\text{load}} = P_{W1} + P_{W2} = 4232 + j3174 + 4232 + j3174 + 4232 + j3174 = \underbrace{(12686 + j9522)}_{P_{\text{load}}} \text{ VA}$$

$$P_{\text{load}} = \boxed{12686 \text{ W}} \quad P_{W1} + P_{W2} = 8086.76 + 3589.23 = \boxed{12685.99 \text{ W}}$$

PROBLEM #3

The three-phase electric heater consists of three heating coils Y-connected. The nominal power of the heater is $P_n = 3 \text{ kW}$, and the nominal voltage $U_n = 230 \text{ V rms}$. The heater has been damaged. After its repair the length of the first coil decreased by 5% and the length of the second coil by 10%.

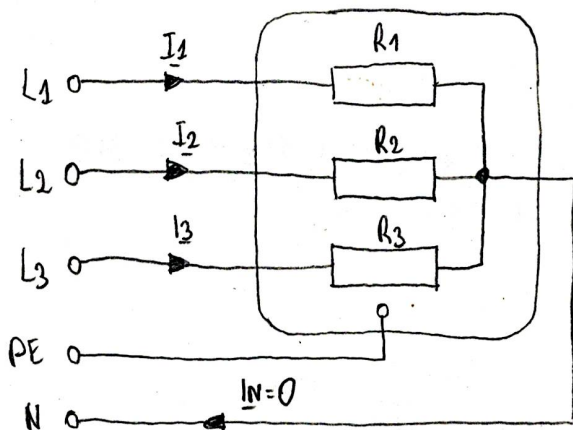a) calculate the line currents before repairing the heater,



$$P = \frac{P_n}{3} = \frac{3000}{3} = 1000 \text{ W}$$

$$R_1 = R_2 = R_3 = R \quad R = \frac{U_n^2}{P} = \frac{230^2}{1000} = 52.8 \, \Omega$$

$$\underline{E}_1 = 230 e^{j0^\circ} = 230 \text{ V}$$

$$\underline{E}_2 = 230 e^{j120^\circ} = (-115 - j119.18) \text{ V}$$

$$\underline{E}_3 = 230 e^{j240^\circ} = (-115 + j119.18) \text{ V}$$

$$\underline{I}_1 = \frac{\underline{E}_1}{R} = \frac{230}{52.8} = 4.3478 = 4.3478 e^{j0^\circ} \text{ A}$$


$$\underline{I}_1 + \underline{I}_2 + \underline{I}_3 = 0$$

$$\underline{I}_2 = \frac{\underline{E}_2}{R} = \frac{-115 - j119.18}{52.8} = (-2.1738 - j3.7653) = 4.3478 e^{-j120^\circ} \text{ A}$$

$$\underline{I}_1 = \underline{I}_2 = \underline{I}_3$$

$$\underline{I}_3 = \frac{\underline{E}_3}{R} = \frac{-115 + j119.18}{52.8} = (-2.1738 + j3.7653) = 4.3478 e^{j120^\circ} \text{ A}$$

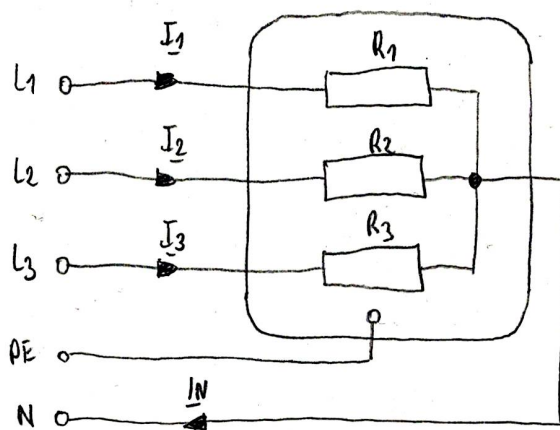b) calculate line currents, the current in the neutral line and the power of the repaired heater



$$R_1 = 0.95 R = 0.95 \cdot 52.8 = 50.255 \, \Omega$$

$$R_2 = 0.9 R = 0.9 \cdot 52.8 = 47.61 \, \Omega$$

$$R_3 = R = 52.8 \, \Omega$$

$$\underline{I}_1 = \frac{\underline{E}_1}{R_1} = \frac{230}{50.255} = 4.5769 = 4.5769 e^{j0^\circ} \text{ A}$$

$$\underline{I}_2 = \frac{\underline{E}_2}{R_2} = \frac{-115 - j119.18}{47.61} = (-2.4155 - j4.1839) = 4.8308 e^{-j120^\circ} \text{ A}$$


$$\underline{I}_3 = \frac{\underline{E}_3}{R_3} = \frac{-115 + j119.18}{52.8} = (-2.1738 + j3.7653) = 4.3478 e^{j120^\circ} \text{ A}$$

$$\underline{I}_N = \underline{I}_1 + \underline{I}_2 + \underline{I}_3 = 4.5769 - 2.4155 - j4.1839 - 2.1738 + j3.7653 = (-0.0127 - j0.4184) = 0.4186 e^{-j81.74^\circ} \text{ A}$$

$$P_n = \frac{U_n^2}{R_1} + \frac{U_n^2}{R_2} + \frac{U_n^2}{R_3} = \frac{230^2}{50.255} + \frac{230^2}{47.61} + \frac{230^2}{52.8} = 3163.7 \text{ W}$$

$$P_n = \operatorname{Re} \{ \underline{S} \} = \operatorname{Re} \{ \underline{E}_1 \underline{I}_1^* + \underline{E}_2 \underline{I}_2^* + \underline{E}_3 \underline{I}_3^* \} = \operatorname{Re} \{ 230 \cdot (4.5769) + (-115 - j119.18)(-2.4155 + j4.1839) + (-115 + j119.18)(-2.1738 - j3.7653) \} = 3163.7 \text{ W}$$

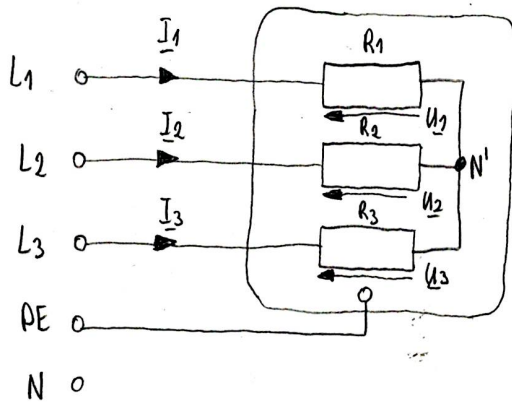c) calculate line currents and the power of the repaired heater, when the neutral line is not connected



$$Y_1 = \frac{1}{Z_1} = \frac{1}{R_1} = \frac{1}{50.255} = 0.0198 \text{ } \Omega^{-1}$$

$$Y_2 = \frac{1}{Z_2} = \frac{1}{R_2} = \frac{1}{47.61} = 0.021 \text{ } \Omega^{-1}$$

$$Y_3 = \frac{1}{Z_3} = \frac{1}{R_3} = \frac{1}{52.8} = 0.0189 \text{ } \Omega^{-1}$$

$$U_{NN'} = \frac{E_1 \cdot Y_1 + E_2 \cdot Y_2 + E_3 \cdot Y_3}{Y_1 + Y_2 + Y_3} = \frac{230 \cdot 0.0198 + (-115 - j188.18) \cdot 0.021 + (-115 + j188.18) \cdot 0.0189}{0.0198 + 0.021 + 0.0189} =$$

$$= (-0.2126 - j6.8954) \text{ V}$$

$$U_1 = E_1 - U_{NN'} = 230 - (-0.2126 - j6.8954) = (230.2126 + j6.8954) \text{ V} = 230.3188 e^{j1.74^\circ} \text{ V}$$

$$U_2 = E_2 - U_{NN'} = (-115 - j188.18) - (-0.2126 - j6.8954) = (-114.7874 - j182.1804) \text{ V} = 223.86 e^{-j120.85^\circ} \text{ V}$$

$$U_3 = E_3 - U_{NN'} = (-115 + j188.18) - (-0.2126 - j6.8954) = (-114.7874 + j206.1813) \text{ V} = 235.9807 e^{j119.11^\circ} \text{ V}$$

$$I_1 = \frac{U_1}{R_1} = \frac{230.2126 + j6.8954}{50.255} = (4.5808 + j0.1382) \text{ A} = 4.583 e^{j1.74^\circ} \text{ A}$$

$$I_2 = \frac{U_2}{R_2} = \frac{-114.7874 - j182.1804}{47.61} = (-2.411 - j4.0368) \text{ A} = 4.701 e^{-j120.85^\circ} \text{ A}$$

$$I_3 = \frac{U_3}{R_3} = \frac{-114.7874 + j206.1813}{52.8} = (-2.1688 + j3.8876) \text{ A} = 4.4608 e^{j119.11^\circ} \text{ A}$$

$$P_n = \frac{|U_1|^2}{R_1} + \frac{|U_2|^2}{R_2} + \frac{|U_3|^2}{R_3} = \frac{230.3188^2}{50.255} + \frac{223.86^2}{47.61} + \frac{235.9807^2}{52.8} = 3160.8 \text{ W}$$

$$P_n = R_1 \cdot |I_1|^2 + R_2 \cdot |I_2|^2 + R_3 \cdot |I_3|^2 = 50.255 \cdot 4.583^2 + 47.61 \cdot 4.701^2 + 52.8 \cdot 4.4608^2 = 3160.8 \text{ W}$$

$$P_n = \operatorname{Re} \{ S \} = \operatorname{Re} \{ U_1 \cdot I_1^* + U_2 \cdot I_2^* + U_3 \cdot I_3^* \} = 3160.8 \text{ W}$$