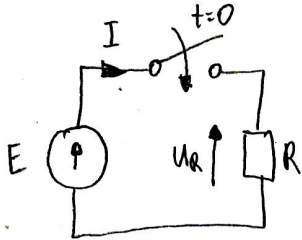




ELECTRICAL CIRCUITS 2 - CLASS NO. 10 (20.05.2025)

TRANSIENT AND STEADY STATE

* R CIRCUIT




$t < 0$	$t \gg 0$
$I = 0$	$I = \frac{E}{R}$
$U_R = 0$	$U_R = E$

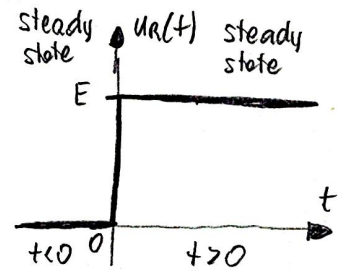
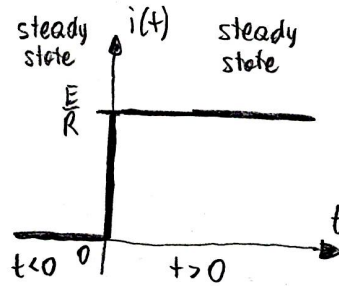


E - DC voltage source


* RC CIRCUIT

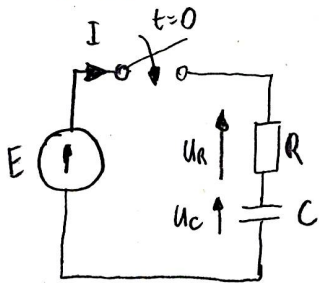




$t < 0$	$t \gg 0$
$I = 0$	$I = 0$
$U_R = 0$	$U_R = 0$
$U_L = 0$	$U_L = E$

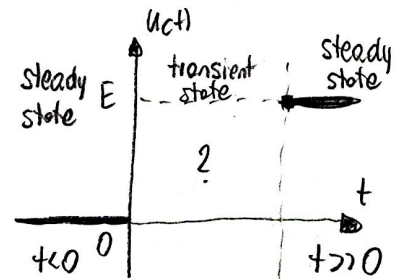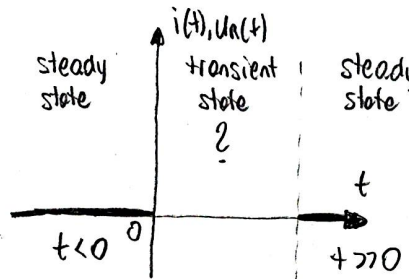

* RL CIRCUIT

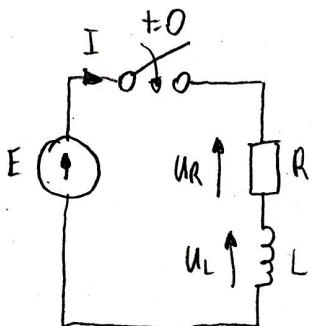

$t < 0$	$t \gg 0$
$I = 0$	$I = \frac{E}{R}$
$U_R = 0$	$U_R = E$
$U_L = 0$	$U_L = 0$

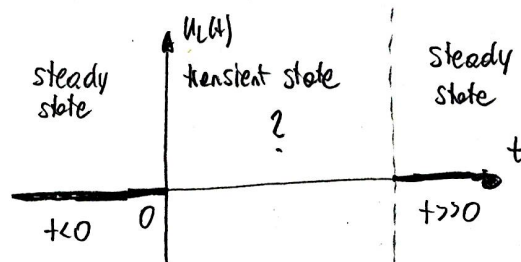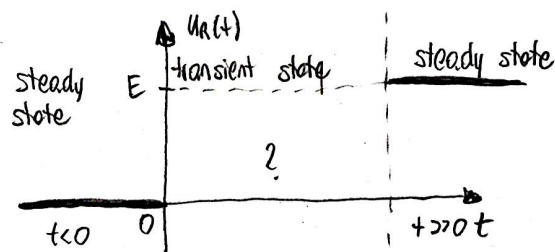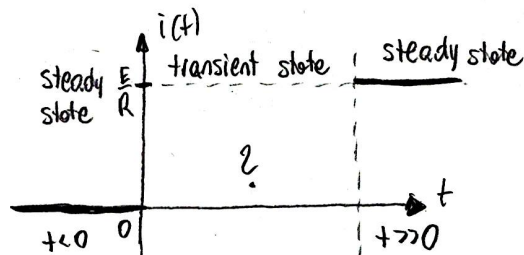


INITIAL AND STEADY STATE VALUES

* initial conditions

for $C \rightarrow U_C$ at $t=0$
for $L \rightarrow I_L$ at $t=0$

* example 1

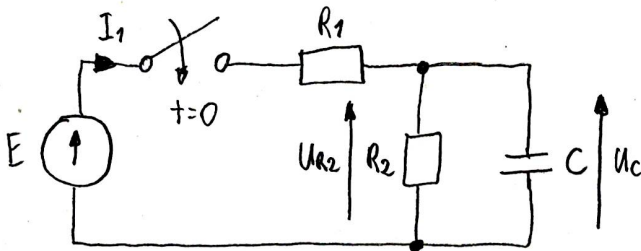

$$t < 0$$

$$U_C = 0$$

$$t \gg 0$$


$$U_C = U_{R2}$$

$$I_1 = \frac{E}{R_1 + R_2}$$

$$U_{R2} = U_C = I_1 \cdot R_2 = \frac{R_2 \cdot E}{R_1 + R_2}$$

$$U_C = \frac{R_2 \cdot E}{R_1 + R_2}$$

* example 2

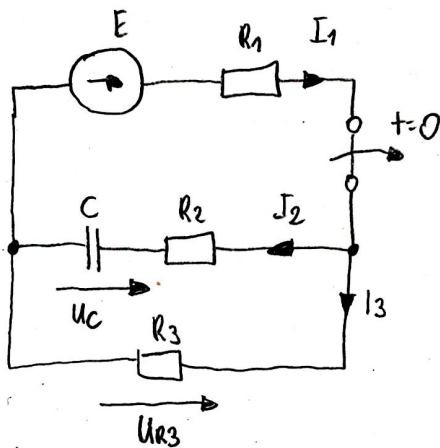

$$t < 0$$

$$U_C = U_{R3}$$

$I_2 = 0$, $C \rightarrow$ open circuit for DC


$$I_1 = I_3$$

$$I_1 = \frac{E}{R_1 + R_3}$$

$$U_{R3} = I_1 \cdot R_3 = \frac{R_3 E}{R_1 + R_3}$$


$$U_C = \frac{R_3 \cdot E}{R_1 + R_3}$$

$$t \gg 0$$

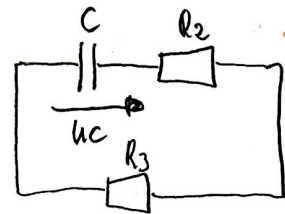

no source $\rightarrow U_C = 0$

* example 3

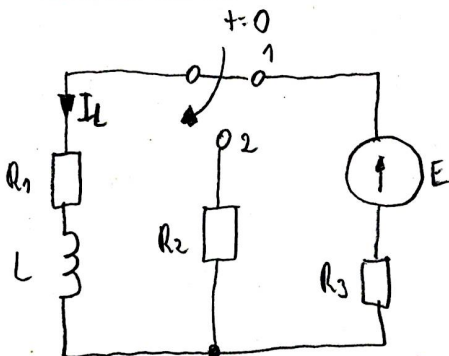


$$t < 0$$

$L \rightarrow$ short circuit for DC

$$I_L = \frac{E}{R_1 + R_3}$$


$$t \gg 0$$

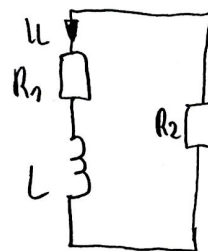

no source $\rightarrow I_L = 0$

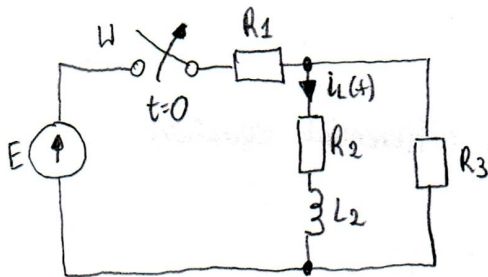PROBLEM #1

The circuit shown in the figure has been in a steady-state. The switch was open at $t=0$. Find $i_L(t)$. $E=80V$, $R_1=120\Omega$, $R_2=50\Omega$, $R_3=200\Omega$, $L_2=0.75H$.




* INITIAL VALUES ($t < 0$), steady-state before opening the switch

Notes:

- We consider circuit as a DC circuit
- in the case of a DC circuit, we replace inductor with a short-circuit and capacitor with an open-circuit
- We use classical methods: Ohm's Law, KCL, KVL

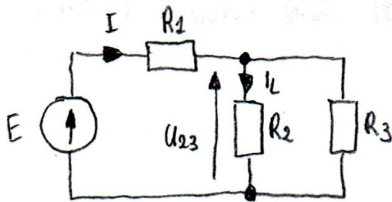our circuit before opening the switch (DC circuit), $I_L = ?$



$$I = \frac{E}{R_1 + \frac{R_2 \cdot R_3}{R_2 + R_3}} = \frac{80}{120 + \frac{50 \cdot 200}{50 + 200}} = \frac{80}{120 + 40} = \frac{80}{160} = 0.5 \text{ A}$$

$$U_{23} = I \cdot \frac{R_2 \cdot R_3}{R_2 + R_3} = 0.5 \cdot \frac{50 \cdot 200}{50 + 200} = 0.5 \cdot 40 = 20 \text{ V}$$

$$I_L = \frac{U_{23}}{R_2} = \frac{20}{50} = 0.4 \text{ A}$$

* TRANSIENT ANALYSIS ($t > 0$), circuit after opening the switch

Notes:

- We write differential equation with the use of KVL or KCL
- note that: $u_L = L \frac{di_L(t)}{dt}$ $i_C(t) = C \frac{du_C(t)}{dt}$
- general form of differential equation:

$$a_n \frac{d^n x(t)}{dt^n} + a_{n-1} \frac{d^{n-1} x(t)}{dt^{n-1}} + \dots + a_1 \frac{dx(t)}{dt} + a_0 x(t) = f(t) \quad (1)$$

where:


$x(t)$ - searched quantity (current (voltage))

$a_n, a_{n-1}, \dots, a_1, a_0$ - constant coefficients (R, L, C, M in the circuit)

$f(t)$ - voltage and current sources

n - the order of differential equation (the number of inductors/capacitors in the circuit)

our circuit after opening the switch

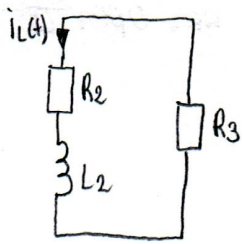

using KVL:

$$u_{R2}(t) + u_{L2}(t) + u_{R3}(t) = 0$$

$$R_2 \cdot i_L(t) + L_2 \frac{di_L(t)}{dt} + R_3 \cdot i_L(t) = 0$$

$$\boxed{L_2 \frac{di_L(t)}{dt} + (R_2 + R_3) i_L(t) = 0} \quad \text{— a first-order differential equation}$$

Notes:

- the solution of equation (1) has a form

$$x(t) = x_p(t) + x_c(t) \quad (2)$$

where:

$x_p(t)$ — the particular integral solution (forced response)


$x_c(t)$ — the complementary solution (natural response)

in our case: $i_L(t) = i_{LP}(t) + i_{LC}(t)$

Notes:

- the particular integral solution we obtain by solving the steady state circuit ($t \rightarrow \infty$)

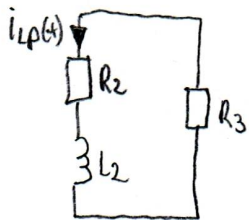in steady state ($t \rightarrow \infty$) $i_{LP}(t) = ?$



$i_{LP}(t) = 0$ ← because there is no voltage source in the circuit

Notes:

- we obtain the complementary solution by solving the homogeneous equation (1)

$$a_n \frac{d^n x_c(t)}{dt^n} + a_{n-1} \frac{d^{n-1} x_c(t)}{dt^{n-1}} + \dots + a_1 \frac{dx_c(t)}{dt} + a_0 x_c(t) = 0 \quad (3)$$

- the solution of (3) has a form:

$$x_c(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + \dots + A_n e^{s_n t}$$

where:

$s_1, s_2, \dots, s_n$ — roots of characteristic equation: $a_n s^n + a_{n-1} s^{n-1} + \dots + a_1 s + a_0 = 0$

$A_1, A_2, \dots, A_n$ — integration constants determined with the use of initial values

$i_{Lc}(t)$ - the complementary solution
a first-order differential equation:

$$L_2 \frac{di_{Lc}(t)}{dt} + (R_2 + R_3) i_{Lc}(t) = 0$$

has a solution in the form:

$$i_{Lc}(t) = A_1 \cdot e^{s_1 t}$$

s_1 is determined from the characteristic equation:

$$L_2 \cdot s_1 + (R_2 + R_3) = 0 \Rightarrow s_1 = -\frac{R_2 + R_3}{L_2} = -\frac{50 + 100}{0.75} = -333.33$$

A_1 is determined with the use of initial conditions

$$\text{at } t=0: i_L(0^-) = i_L(0^+) \quad i_L(0^-) = i_L(0^+) = I_L = 0.4 \text{ A}$$

$$i_L(t) = i_{Lp}(t) + i_{Lc}(t)$$

$$i_L(t) = 0 + A_1 e^{s_1 t}$$


$$i_L(t) = A_1 e^{-\frac{R_2 + R_3}{L_2} \cdot t}$$

$$t=0 \Rightarrow 0.4 = A_1 e^{-\frac{R_2 + R_3}{L_2} \cdot 0} = 1$$

$$A_1 = 0.4$$

finally:
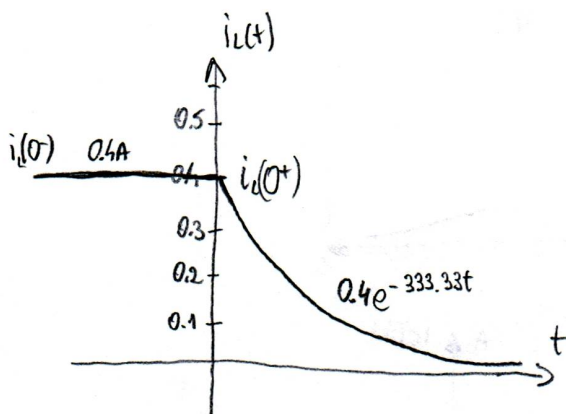
$$i_L(t) = i_{Lp}(t) + i_{Lc}(t) = 0 + 0.4 e^{-333.3t} = 0.4 e^{-333.3t} \text{ A}$$



$$u_{L2}(t) = L_2 \frac{di_L(t)}{dt} = 0.75 \frac{d}{dt} (0.4 e^{-333.3t}) = 0.75 \cdot 0.4 \cdot (-333.3) e^{-333.3t} = -100 e^{-333.3t}$$

