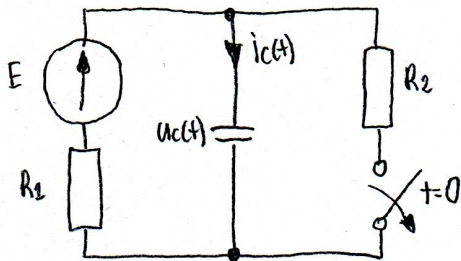



ELECTRICAL CIRCUITS 2 - CLASS NO. 11 (27.05.2025)

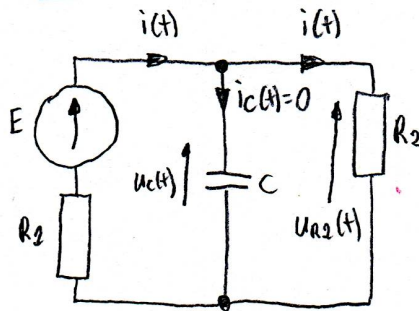PROBLEM #1

The circuit shown in the figure has been in a steady-state. The switch was open at $t=0$. Calculate and plot $i_c(t)$ and $u_c(t)$ for $t<0$, $t=0$ and $t>0$. $E=100V$, $R_1=20\Omega$, $R_2=40\Omega$, $C=10mF$.



steady-state before opening the switch ($t<0$)



$$i_c(t) = 0 A$$


$$u_c(t) = u_{R2}(t)$$

$$i(t) = \frac{E}{R_1 + R_2}$$

$$u_{R2}(t) = R_2 \cdot i(t) = \frac{R_2}{R_1 + R_2} \cdot E$$

$$u_{R2}(t) = \frac{40}{20+40} \cdot 100 = 66,67 V$$

circuit after opening the switch ($t>0$)

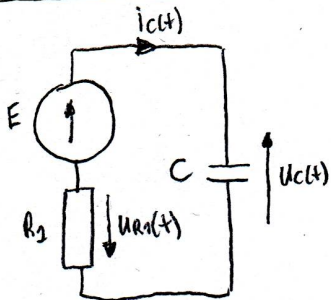

$$u_{R2}(t) + u_c(t) = E$$

$$R_2 \cdot i_c(t) + u_c(t) = E$$


$$i_c(t) = C \frac{du_c(t)}{dt}$$

$$R_2 C \frac{du_c(t)}{dt} + u_c(t) = E$$

$$u_c(t=0) = 66,67 V$$

$$u_c(t=0) = 66,67 V$$

$$u_c(t \rightarrow \infty) = 100 V$$

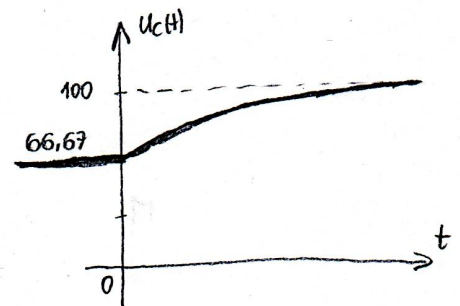

$$u_c(t) = u_{cp}(t) + u_{cc}(t)$$

$u_{cp}(t)$ - the particular solution ($t \gg 0$)

$$u_{cp}(t) = E = 100 V$$

$u_{cc}(t)$ - the complementary solution

$$R_2 C \frac{du_{cc}(t)}{dt} + u_{cc}(t) = 0 \quad u_{cc}(t) = A_1 e^{s_1 t}$$

$$R_2 C s_1 + 1 = 0 \Rightarrow s_1 = -\frac{1}{R_2 C} = -\frac{1}{20 \cdot 0,01} = -\frac{1}{0,2} = -5 s$$

at $t=0$

$$u_c(t) = u_{cp}(t) + u_{cc}(t)$$

$$66,67 = 100 + A_1 e^0 \Rightarrow A_1 = 66,67 - 100 = -33,33 V$$

$$u_{cc}(t) = -33,33 e^{-5t} V$$


$$u_c(t) = u_{cp}(t) + u_{cc}(t) = 100 - 33,33 e^{-5t} V$$

$$i_c(t) = C \frac{du_c(t)}{dt} = 0,01 \frac{d}{dt} (100 - 33,33 e^{-5t}) = 0,01 \cdot 33,33 \cdot 5 e^{-5t} = 1,67 e^{-5t} A$$

$$i_c(t<0) = 0 A$$


$$i_c(t=0) = 1,67 A$$

$$i_c(t \rightarrow \infty) = 0 A$$

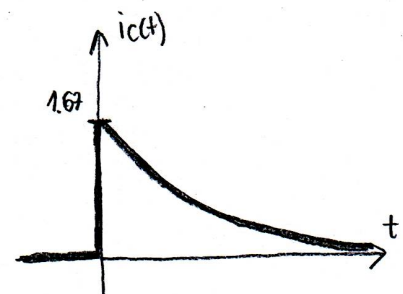


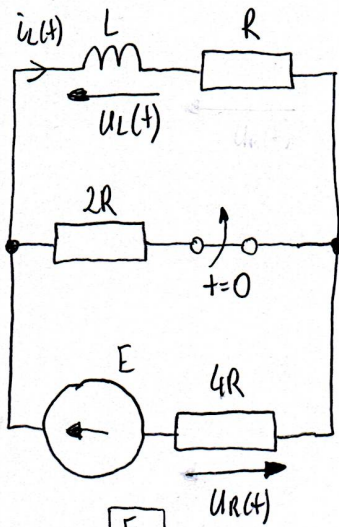PROBLEM #2

The circuit shown in the figure has been in a steady-state. At $t=0$ the switch was open. Find and plot $i_L(t)$, $u_L(t)$, and $u_R(t)$ for $t < 0$, $t = 0$, and $t > 0$.



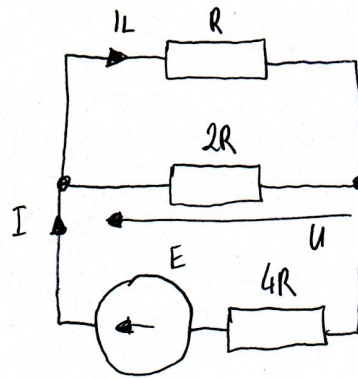steady-state before opening the switch ($t < 0$)



$$R_{eq1} = \frac{R \cdot 2R}{R + 2R} = \frac{2R^2}{3R} = \frac{2}{3}R$$

$$R_{eq} = \frac{2R}{3} + 4R = \frac{2R}{3} + \frac{12R}{3} = \frac{14}{3}R$$

$$I = \frac{E}{R_{eq}} = \frac{E}{\frac{14R}{3}} = \frac{3E}{14R}$$

$$u = R_{eq1} \cdot I = \frac{2R}{3} \cdot \frac{3E}{14R} = \frac{E}{7}$$


$$I_L = \frac{u}{R} = \frac{E}{7R}$$

$$I_L(0^-) = \frac{E}{7R}$$

$$u_L(0^-) = 0$$

$$u_R(0^-) = 4R \cdot I = \frac{4R \cdot 3E}{14R} = \frac{6}{7}E$$

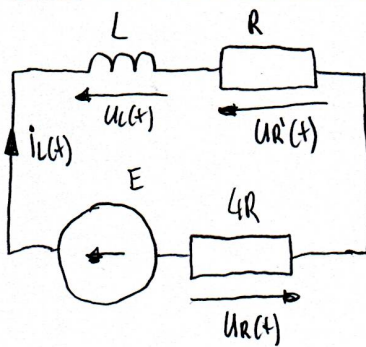circuit after opening the switch ($t > 0$)



KVL

$$u_L(t) + R \cdot i_L(t) + 4R \cdot i_L(t) = E$$

$$L \frac{di_L(t)}{dt} + 5R \cdot i_L(t) = E$$

$$i_L(t) = i_{lp}(t) + i_{lc}(t)$$

$i_{lp}(t)$ - the particular solution ($t \gg 0$)

$$i_{lp}(t) = \frac{E}{5R}$$

$i_{lc}(t)$ - the complementary solution

$$L \frac{di_{lc}(t)}{dt} + 5R i_{lc}(t) = 0$$

$$i_{lc}(t) = A_2 e^{s_2 t}$$

$$i_{lc} = -\frac{2E}{35R} e^{-\frac{5R}{L}t}$$

$$(s_2) \quad L s_2 + 5R = 0$$

$$s_2 = -\frac{5R}{L}$$

(A₂)

$$i_L(0^-) = i_L(0^+)$$

$$i_L(t) = i_{lp}(t) + i_{lc}(t) \quad \text{for } t = 0$$

$$\frac{E}{7R} = \frac{E}{5R} + A_2 e^{s_2 t} \quad \leftarrow t=0$$

$$A_2 = \frac{E}{7R} - \frac{E}{5R} = \frac{5E - 7E}{35R} = -\frac{2E}{35R}$$

$$\dot{i}_L(t) = \dot{i}_{LP}(t) + \dot{i}_{LC}(t)$$

$$\dot{i}_L(t) = \frac{E}{5R} - \frac{2E}{35R} e^{-\frac{5R}{L}t}$$


$$u_L(t) = L \frac{di_L(t)}{dt} = L \frac{d}{dt} \left(\frac{E}{5R} - \frac{2E}{35R} e^{-\frac{5R}{L}t} \right) = -\frac{2EL}{35R} \cdot \left(-\frac{5R}{L} \right) e^{-\frac{5R}{L}t} = \frac{2E}{7} e^{-\frac{5R}{L}t}$$

$$u_R(t) = 4R \cdot i_L(t) = \frac{4RE}{5R} - \frac{2 \cdot 4RE}{35R} e^{-\frac{5R}{L}t} = \frac{4E}{5} - \frac{8E}{35} e^{-\frac{5R}{L}t}$$

$$\dot{i}_L(t < 0) = \frac{E}{7R}$$

$$\dot{i}_L(t = 0) = \frac{E}{5R} - \frac{2E}{35R} = \frac{7E - 2E}{35R} = \frac{E}{7R}$$


$$\dot{i}_L(t > 0) = \frac{E}{5R}$$

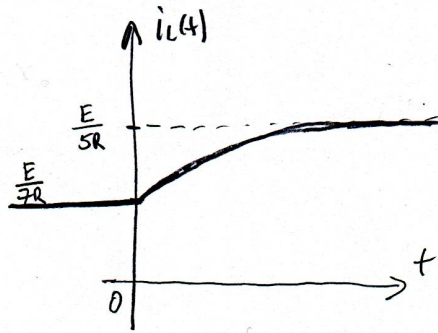

$$u_L(t < 0) = 0$$

$$u_L(t = 0) = \frac{2E}{7}$$


$$u_L(t > 0) = 0$$

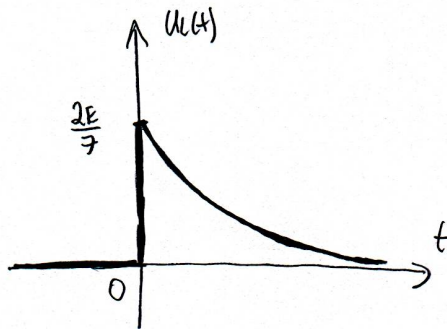

$$u_R(t < 0) = \frac{6E}{7}$$


$$u_R(t > 0) = \frac{4E}{5}$$
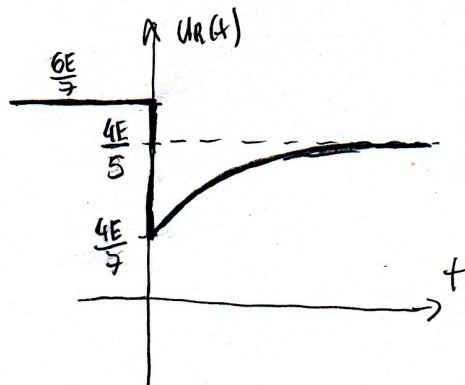
$$u_R(t = 0) = \frac{4E}{5} - \frac{8E}{35} = \frac{(28-8)E}{35} = \frac{20E}{35} = \frac{4E}{7}$$



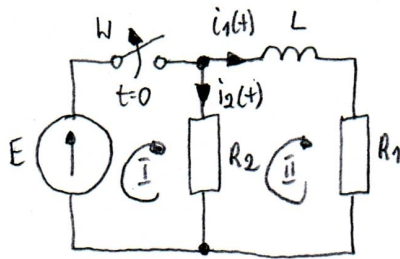PROBLEM #3

The circuit shown in the figure has been in a steady-state. The switch was open at $t=0$. Plot $i_1(t)$ and $i_2(t)$ for $t < 0$, $t=0$ and $t > 0$. Use the classical method. $E=100V$, $L=0.1H$, $R_1=25\Omega$, $R_2=75\Omega$,



steady-state before opening switch ($t < 0$)

$$\begin{cases} I_1 R_2 - I_2 R_2 = E \\ -I_1 R_2 + I_2 (R_1 + R_2) = 0 \end{cases}$$

$$\begin{cases} 75 I_1 - 75 I_2 = 100 \\ -75 I_1 + 100 I_2 = 0 \end{cases} +$$

$$25 I_2 = 100$$

$$I_2 = 4 A$$


$$I_1 R_2 = E + I_2 R_2$$

$$I_1 = \frac{E + I_2 R_2}{R_2} = \frac{100 + 4 \cdot 75}{75} = \frac{400}{75} = 5.33 A$$

$$i_1 = I_1 = \boxed{4 A}$$

$$i_2 = I_1 - I_2 = 5.33 - 4 = \boxed{1.33 A}$$

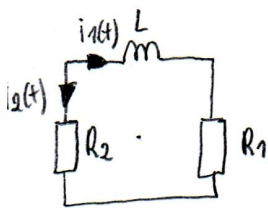circuit after opening the switch ($t > 0$)



using KVL:

$$i_2(t) \cdot R_1 + i_1(t) \cdot R_2 + L \frac{di_1(t)}{dt} = 0$$

$$L \frac{di_1(t)}{dt} + (R_1 + R_2) i_1(t) = 0$$

$$i_1(t) = i_{1p}(t) + i_{1c}(t)$$

$i_{1p}(t)$ - the particular solution

$$i_{1p}(t) = 0$$

$i_{1c}(t)$ - the complementary solution

$$L \frac{di_{1c}(t)}{dt} + (R_1 + R_2) i_{1c}(t) = 0$$

$$L s_1 + R_1 + R_2 = 0 \quad s_1 = -\frac{R_1 + R_2}{L}$$

$$i_{1c} = A_1 e^{s_1 t}$$

$$\text{at } t=0: i_1(t) = i_{1p}(t) + i_{1c}(t)$$

$$4 = 0 + A_1 e^0 \rightarrow A_1 = 4$$

$$i_1(t) = 4e^{-1000t} A$$

$$i_2(t) = -i_1(t) = -4e^{-1000t} A$$

