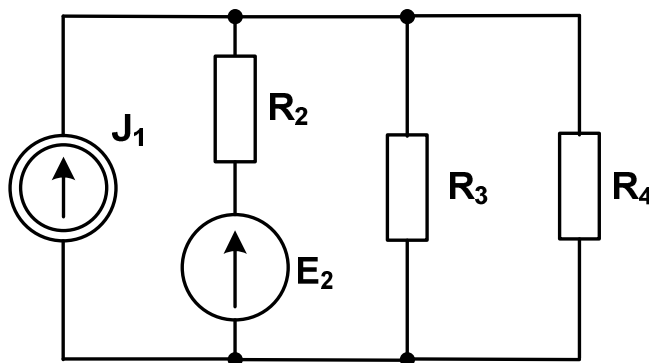


Module name: **Electrical Circuits 1**
 Module ID: **IS-FEE-10070W**
 Module type: **Class**
 Semester: **winter 2024/2025**
 Instructor: **Jarosław Forenc, j.forenc@pb.edu.pl**


Class 03 (21.10.2024)

1. What should be the minimum power rating of the resistor R_4 in the circuit shown in the figure?

$J_1 = 1 \text{ A}$, $E_2 = 10 \text{ V}$, $R_2 = R_3 = R_4 = 2 \Omega$




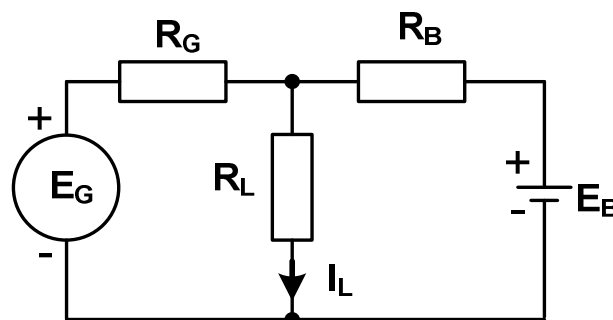2. An automobile generator with an internal resistance of $R_G = 0.2 \Omega$ develops an open-circuit voltage of $E_G = 16 \text{ V}$. The storage battery has an internal resistance of $R_B = 0.1 \Omega$ and an open-circuit voltage of $E_B = 12.8 \text{ V}$. Both sources are connected in parallel to a load $R_L = 1 \Omega$. Determine the load current I_L .



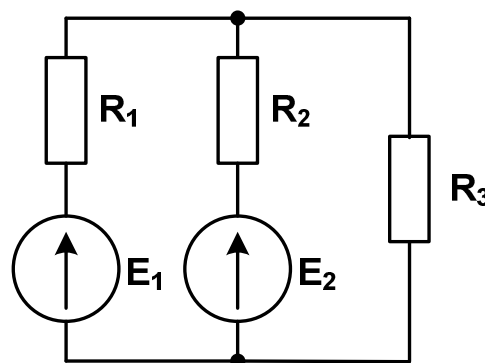3. Make a power balance for the circuit shown in the figure (i.e., the power provided by the batteries equals the sum of the power dissipated by the resistances).


$E_1 = 10 \text{ V}$, $R_1 = 4 \Omega$, $E_2 = 12 \text{ V}$, $R_2 = 2 \Omega$,
 $R_3 = 10 \Omega$



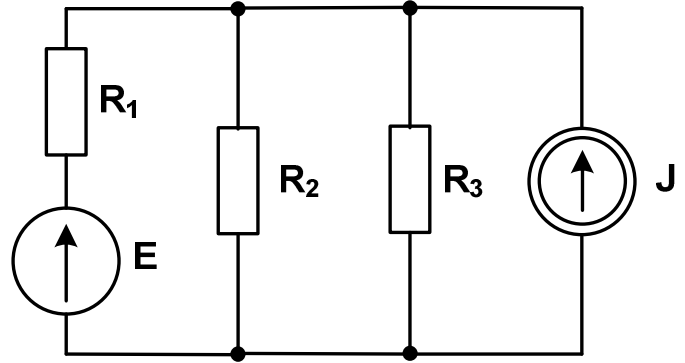4. Calculate the currents in all branches of the circuit shown in the figure using the **superposition principle**.

$$E = 4 \text{ V}, J = 1 \text{ A},$$

$$R_1 = 1 \ \Omega, R_2 = 2 \ \Omega, R_3 = 2 \ \Omega$$



5. An automobile generator with an internal resistance of $R_G = 0.2 \ \Omega$ develops an open-circuit voltage of $E_G = 16 \text{ V}$. The storage battery has an internal resistance of $R_B = 0.1 \ \Omega$ and an open-circuit voltage of $E_B = 12.8 \text{ V}$. Both sources are connected in parallel to a load $R_L = 1 \ \Omega$. Determine the load current I_L using the **superposition principle**.

