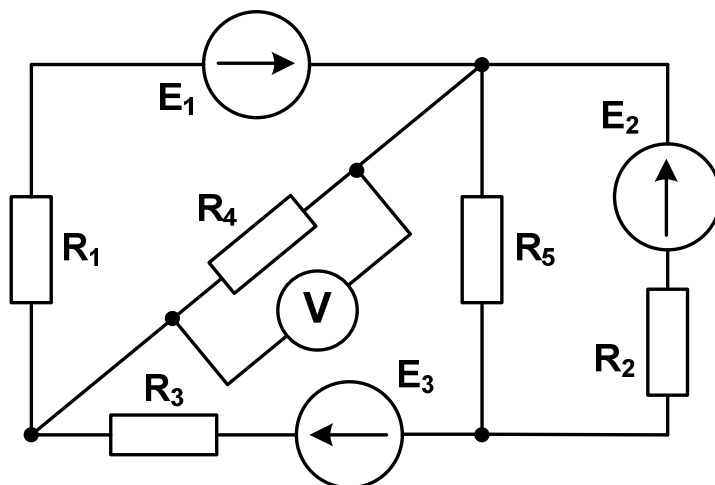




Module name: **Electrical Circuits 1**
 Module ID: **IS-FEE-10070W**
 Module type: **Class**
 Semester: **winter 2024/2025**
 Instructor: **Jarosław Forenc, j.forenc@pb.edu.pl**

Class 05 (04.11.2024)

1. Calculate the reading on the voltmeter reading in the circuit shown in the figure, using the **Node-Voltage Method**. $E_1 = 12\text{ V}$, $E_2 = E_3 = 6\text{ V}$, $R_1 = 100\ \Omega$, $R_2 = 390\ \Omega$, $R_3 = 330\ \Omega$, $R_4 = 150\ \Omega$, $R_5 = 120\ \Omega$, $R_V = \infty$.



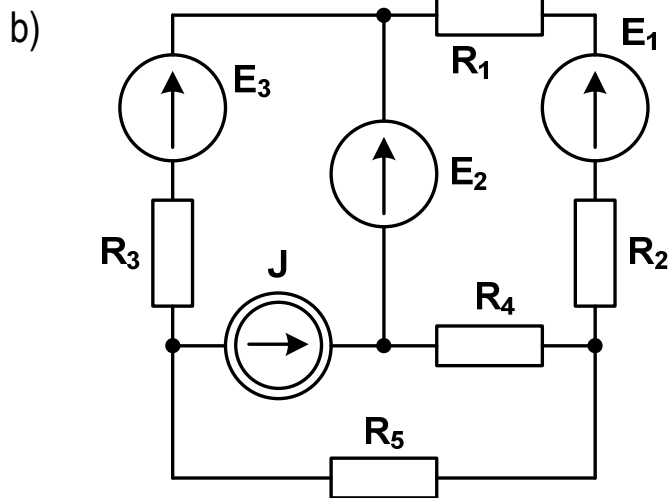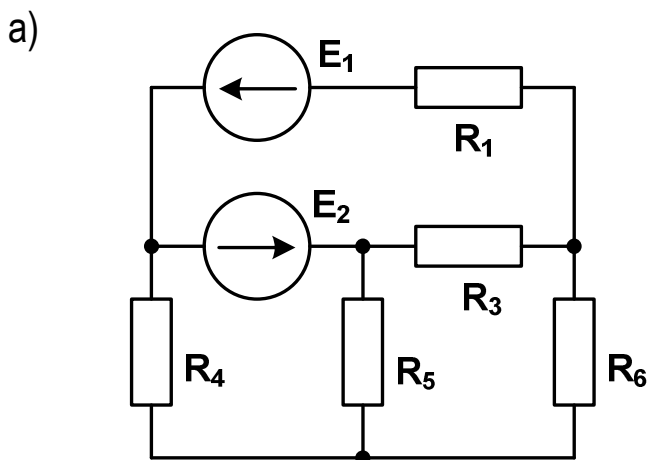2. Write the equations according to the **Node-Voltage Method** for the circuits shown in the figures.



3. Measure the internal resistance of a **9V** battery using the following method:

- **Step 1:** Use a multimeter to measure the battery's voltage, **E**.
- **Step 2:** Measure the actual resistance of a **R = 220 Ω** resistor with a multimeter. Connect this resistor in series with the battery and then measure the voltage **U** across the resistor.
- **Step 3:** Calculate the battery's internal resistance, **R_{int}**, using the following formula:

$$R_{int} = R \cdot \frac{E - U}{U}$$

4. Measure the actual resistances of the resistors:

$$R_1 = 220 \Omega, R_2 = 100 \Omega, R_3 = 470 \Omega, R_4 = 470 \Omega.$$

Using these measured values and **9V** battery, calculate the potential **V_A** with the **Node-Voltage Method**. Consider two cases: a) **R_{int} = 0 Ω**, and b) **R_{int}** as the value calculated in problem no. 3.

Build the circuit shown in the figure. Using a multimeter, measure the voltage between points **V_A** and **V_B**, and compare the measured results with the calculated values.

