

LOOP-CURRENT METHOD IN AC CIRCUITS


* the analysis is performed with the following sequence of steps.

- ① identify the loops
- ② assign a loop current to each loop
- ③ write KVL equation around each loop
- ④ solve the resulting system of equations for all loop currents
- ⑤ the branch current depends on the loop currents flowing in the branch

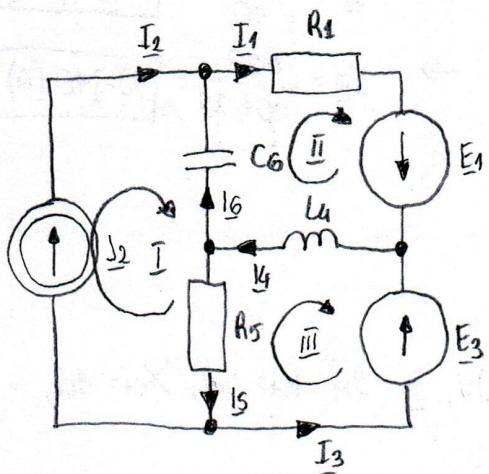PROBLEM #1

Calculate the currents in all branches of the circuit shown in the figure using the Loop-Current Method.

$$R_1 = 20\Omega, X_{L4} = 20\Omega, R_5 = 10\Omega, X_{C6} = 20\Omega, E_1 = j20V, E_3 = 20V, J_2 = 10A.$$



$$\begin{cases} \underline{I_I} = \underline{J_2} = 10A \\ \underline{I_{II}}(R_1 + jX_{L4} - jX_{C6}) - (-jX_{C6}) \cdot \underline{I_I} - (jX_{L4}) \cdot \underline{I_{III}} = E_1 \\ \underline{I_{III}}(R_5 + jX_{L4}) - \underline{I_I}(R_5) - \underline{I_{II}}(jX_{L4}) = -E_3 \end{cases}$$

$$\begin{cases} 10 \cdot j20 + \underline{I_{II}}(20 + j20 - j20) - \underline{I_{III}}(j20) = j20 \\ -10 \cdot 10 - \underline{I_{II}}(j20) + \underline{I_{III}}(10 + j20) = -20 \end{cases}$$

$$\begin{cases} \underline{I_{II}} \cdot 20 - \underline{I_{III}} \cdot j20 = -j180 \\ -\underline{I_{II}} \cdot j20 + \underline{I_{III}}(10 + j20) = 80 \end{cases}$$

Cramer's rule

$$W = \begin{vmatrix} 20 & -j20 \\ -j20 & 10+j20 \end{vmatrix} = 200 + j400 + 400 = 600 + j400$$

$$W_{II} = \begin{vmatrix} -j180 & -j20 \\ 80 & 10+j20 \end{vmatrix} = -j1800 + 3600 + j1600 = 3600 - j200$$

$$W_{III} = \begin{vmatrix} 20 & -j180 \\ -j20 & 80 \end{vmatrix} = 1600 + 3600 = 5200$$

$$I_{II} = \frac{W_{II}}{W} = \frac{3600 - j200}{600 + j400} = 4 - j3 \text{ (A)}$$

$$I_{III} = \frac{W_{III}}{W} = \frac{5200}{600 + j400} = 6 - j4 \text{ (A)}$$

$$\underline{I_I} = \underline{I_{II}} = 4 - j3 \text{ (A)}$$

$$\underline{I_2} = \underline{J_2} = 10 \text{ (A)}$$

$$\underline{I_3} = -\underline{I_{III}} = -6 + j4 \text{ (A)}$$

$$\underline{I_4} = \underline{I_{II}} - \underline{I_{III}} = 4 - j3 - 6 + j4 = -2 + 1j \text{ (A)}$$


$$\underline{I_5} = \underline{I_I} - \underline{I_{III}} = 10 - 6 + j4 = 4 + j4 \text{ (A)}$$

$$\underline{I_6} = \underline{I_{II}} - \underline{I_I} = 4 - j3 - 10 = -6 - j3 \text{ (A)}$$

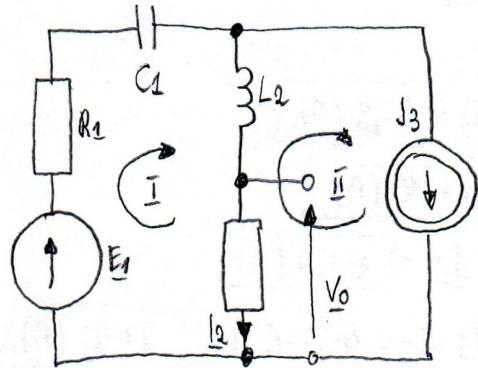PROBLEM #2

Determine the voltage V_o using the Loop-Current Method.

$$R_1 = 2\Omega, X_{C1} = 1\Omega, X_{L2} = 2\Omega, R_2 = 4\Omega, E_1 = 12V, J_3 = 2A.$$



$$V_o = R_2 \cdot I_2$$

$$I_{II} = J_3 = 2A$$

$$I_I (R_1 - jX_{C1} + jX_{L2} + R_2) - I_{II} (R_2 + jX_{L2}) = E_1$$

$$I_I (2 - j1 + j2 + 4) - 2(4 + j2) = 12$$

$$(6+j) I_I = 12 + 2(4+j2)$$

$$(6+j) I_I = 12 + 8 + j4$$

$$(6+j) I_I = 20 + j4$$

$$I_I = \frac{20+j4}{6+j} = (3.3514 + j 0.1081) A$$

$$I_2 = I_I - I_{II}$$

$$I_2 = 3.3514 + j 0.1081 - 2$$


$$I_2 = (1.3514 + j 0.1081) A$$

$$V_o = R_2 \cdot I_2 = 4 \cdot (1.3514 + j 0.1081) = (5.4054 + j 0.4324) V$$

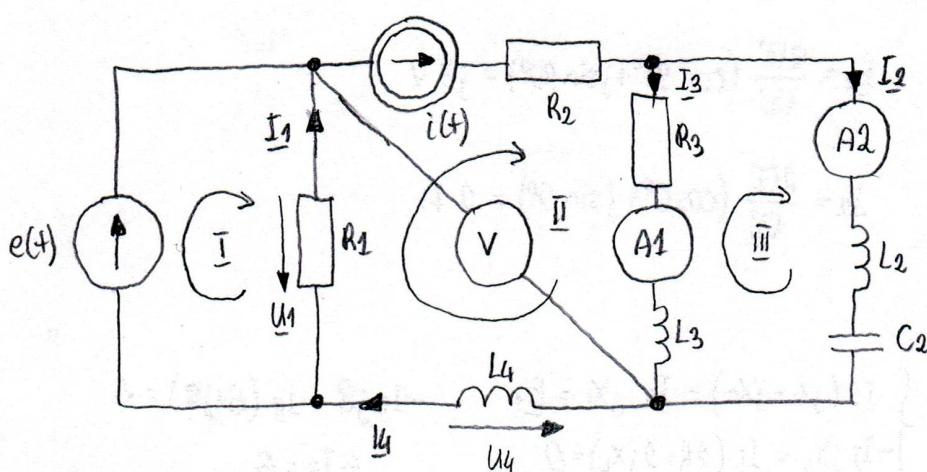PROBLEM #3

Calculate the meter readings in the circuit shown below using the Loop-Current Method.

$$e(t) = 100\sqrt{2} \sin(\omega t) V, i(t) = 5\sqrt{2} \cos(\omega t) A, R_1 = R_2 = R_3 = X_{L2} = X_{L3} = X_{L4} = X_{C2} = 10\Omega.$$



$$E = \frac{100\sqrt{2}}{\sqrt{2}} (\cos 0^\circ + j \sin 0^\circ) = 100 V$$

$$i(t) = 5\sqrt{2} \sin(\omega t + 90^\circ)$$

$$I = \frac{5\sqrt{2}}{\sqrt{2}} (\cos 90^\circ + j \sin 90^\circ) = j5 A$$

$$\begin{cases} I_{II} R_1 - I_{III} R_1 = E \\ I_{II} = j5 A \end{cases}$$

$$-I_{II} (R_3 + jX_{L3}) + I_{III} (R_3 + jX_{L3} + jX_{L2} - jX_{C2}) = 0$$

$$\begin{cases} 10 I_I - 10 I_{II} = 100 \\ -I_{II} (10 + j10) + I_{III} (10 + j10 + j10 - j10) = 0 \end{cases}$$

$$-I_{II} (10 + j10) + I_{III} (10 + j10 + j10 - j10) = 0$$

$$10 \underline{I}_I - 10 \cdot j5 = 100$$

$$-j5(10+j10) + \underline{I}_{\bar{III}}(10+j10) = 0$$

$$10 \underline{I}_I = 100 + j50 \quad | : 10$$

$$\underline{I}_{\bar{III}}(10+j10) = -50 + j50$$

$$\underline{I}_I = [10+j5] A$$

$$\underline{I}_{\bar{III}} = \frac{-50+j50}{10+j10} = [j5] A$$

$$\underline{I}_{\bar{II}} = [j5] A$$

$$\underline{I}_{A1} = \underline{I}_{\bar{II}} - \underline{I}_{\bar{III}} = j5 - j5 = 0 \text{ A} \rightarrow \boxed{\underline{I}_{A1} = 0 \text{ A}}$$

$$\underline{I}_{A2} = \underline{I}_{\bar{III}} = j5 \text{ A} = 5e^{j90^\circ} \text{ A} \rightarrow \boxed{\underline{I}_{A2} = 5 \text{ A}}$$

$$\underline{U}_V = \underline{U}_1 + \underline{U}_4 = (\underline{I}_{\bar{II}} - \underline{I}_I) \cdot R_1 + \underline{I}_{\bar{II}} \cdot jX_{L4} = (j5 - 10 - j5) \cdot 10 + j5 \cdot j10 = -100 - 50 = -150 \text{ V}$$

$$\underline{U}_V = 150e^{j180^\circ} \rightarrow \boxed{\underline{U}_V = 150 \text{ V}}$$