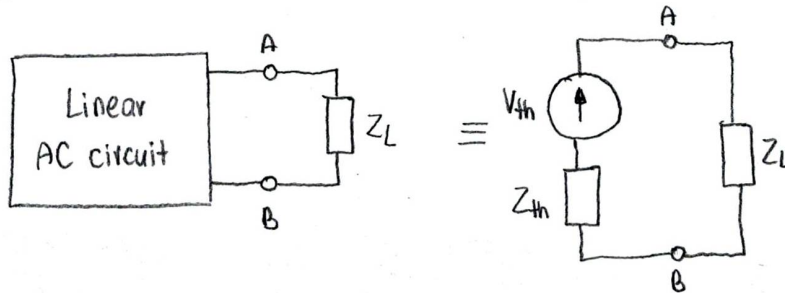


ELECTRICAL CIRCUITS 1 - CLASS NO. 13 (20.01.2025)

THEVENIN'S THEOREM

* any linear AC circuit containing voltage sources, current sources, resistors, inductors and capacitors can be replaced at terminals A-B by an equivalent AC voltage source V_{th} in series with an equivalent impedance Z_{th}




V_{th} - the equivalent voltage obtained at terminals A-B of the circuit with terminals A-B open circuited


Z_{th} - the equivalent impedance between terminals A-B with all sources replaced by their internal impedances (all the voltage sources are replaced by a short, all the current sources are replaced by an open)

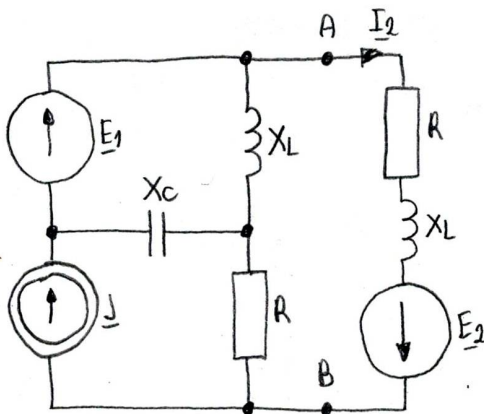PROBLEM #1


Determine the current I_2 using Thevenin's Theorem. $E_1 = 3V$, $E_2 = j8V$, $J = 2A$, $R = 3\Omega$, $X_L = 4\Omega$, $X_C = 2\Omega$.



Z_{th}

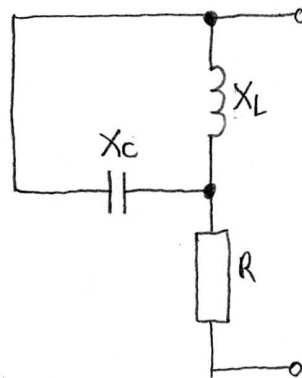
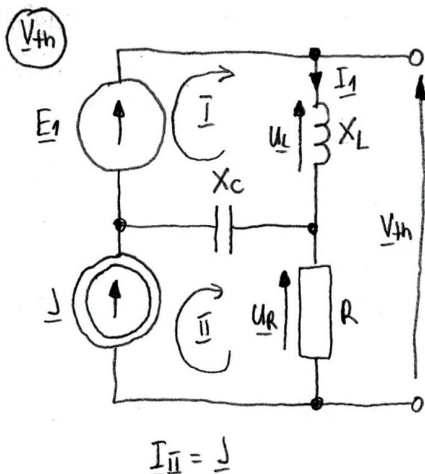
$$\begin{aligned} Z_{th} &= R + \frac{jX_L \cdot (-jX_C)}{jX_L - jX_C} \\ &= 3 + \frac{j4 \cdot (-j2)}{j4 - j2} \\ &= 3 + \frac{8}{j2} = \boxed{(3 - j4)\Omega} \end{aligned}$$




$$I_1(jX_L - jX_C) - J(-jX_C) = E_1$$

$$I_1 = \frac{E_1 - jX_C \cdot J}{jX_L - jX_C} = \frac{3 - j2 \cdot 2}{j4 - j2} = \frac{3 - j4}{j2} = (-2 - j1.5)A$$

$$V_{th} = U_R + U_L = J \cdot R + I_1 \cdot jX_L = 2 \cdot 3 + (-2 - j1.5) \cdot j4 = \boxed{(12 - j8)V}$$




$$I_{II} = J$$

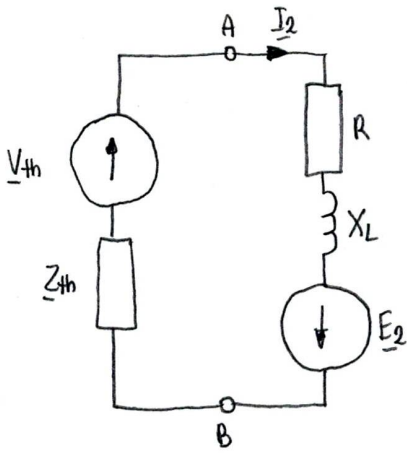


$$\underline{I}_2 = \frac{V_{th} + E_2}{R + jX_L + Z_{th}} = \frac{12 - j8 + j8}{3 + j4 + 3 - j4} = \frac{12}{6} = \boxed{2 \text{ A}}$$

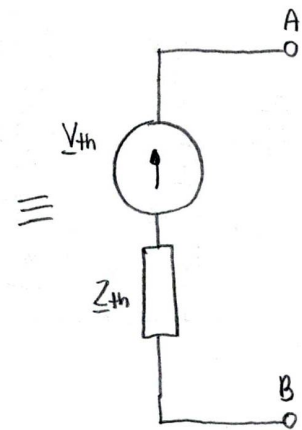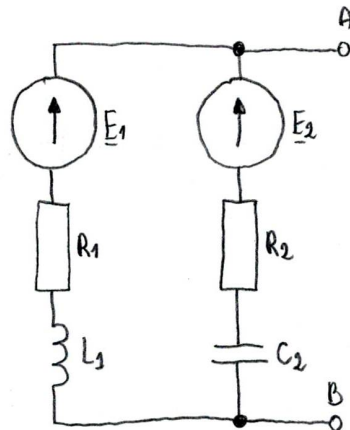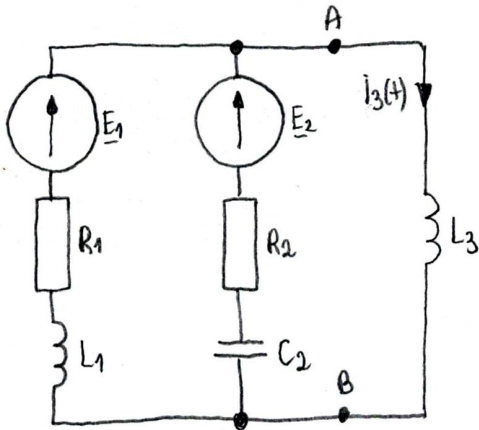PROBLEM #2

Determine the current $i_3(t)$ using Thevenin's Theorem. $e_1(t) = 200 \sin(\omega t + 45^\circ) \text{ V}$, $e_2(t) = 100\sqrt{2} \cos(\omega t) \text{ V}$,
 $R_1 = 20 \Omega$, $X_{L1} = 80 \Omega$, $R_2 = 40 \Omega$, $X_{C2} = 40 \Omega$, $X_{L3} = 20 \Omega$. $e_2(t) = 100\sqrt{2} \sin(\omega t + 90^\circ)$



Z_{th}

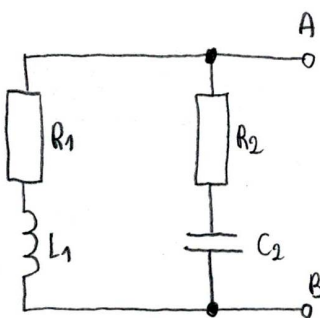


$$Z_{th} = \frac{(R_1 + jX_{L1})(R_2 - jX_{C2})}{R_1 + jX_{L1} + R_2 - jX_{C2}} = \frac{(20 + j80)(40 - j40)}{20 + j80 + 40 - j40} =$$

$$= \frac{4000 + j2400}{60 + j40} = \boxed{(64.62 - j3.08) \Omega}$$

$$\underline{E}_1 = \frac{200}{\sqrt{2}} (\cos 45^\circ + j \sin 45^\circ) = \frac{200}{\sqrt{2}} \left(\frac{\sqrt{2}}{2} + j \frac{\sqrt{2}}{2} \right) = (100 + j100) \text{ V}$$


$$\underline{E}_2 = \frac{100\sqrt{2}}{\sqrt{2}} (\cos 90^\circ + j \sin 90^\circ) = 100 (0 + j1) = j100 \text{ V}$$

V_{th}

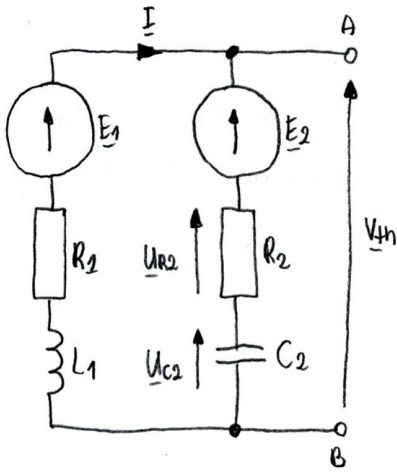

$$\underline{I} = \frac{E_1 - E_2}{R_1 + jX_{L1} + R_2 - jX_{C2}} = \frac{100 + j100 - j100}{20 + j80 + 40 - j40} = \frac{100}{60 + j40} = (1.15 - j0.77) \text{ A}$$
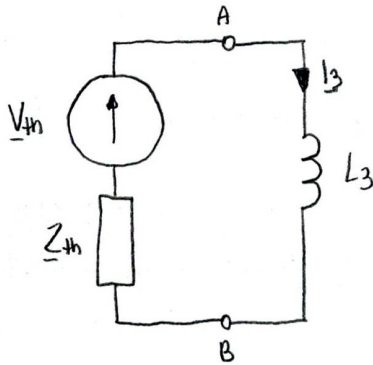
$$V_{th} = E_2 + U_{R2} + U_{C2} = E_2 + R_2 \cdot \underline{I} - jX_{C2} \cdot \underline{I} = j100 + 40(1.15 - j0.77) - j40(1.15 - j0.77) = \boxed{(15.38 + j23.08) \text{ V}}$$



$$\underline{I}_3 = \frac{V_{th}}{Z_{th} + jX_{L3}} = \frac{15.38 + j23.08}{64.62 - j3.08 + j30} = \frac{15.38 + j23.08}{64.62 + j26.92} =$$


$$= \boxed{(0.31 + j0.28) \text{ A}} = \boxed{0.42 e^{j41.63^\circ} \text{ A}}$$

$$i_3(t) = 0.42 \sqrt{2} \sin(\omega t + 41.63^\circ) \text{ A}$$

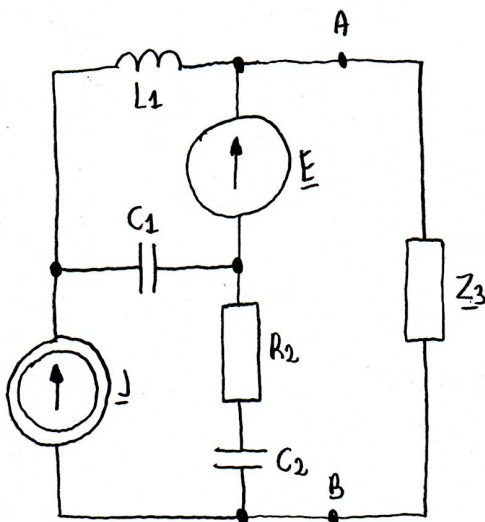
PROBLEM #3

Calculate an active power on Z_3 . Use Thevenin's Theorem.


$$E = (10 + j10) \text{ V}, \quad \underline{J} = (2 + j2) \text{ A}, \quad X_{L1} = 20 \Omega, \quad X_{C1} = 10 \Omega, \quad R_2 = 10 \Omega, \quad X_{C2} = 10 \Omega, \quad Z_3 = (10 + j10) \Omega$$



Z_{TH}

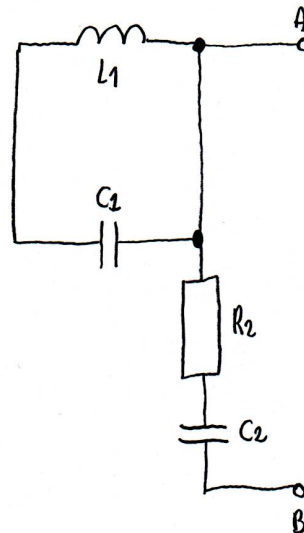
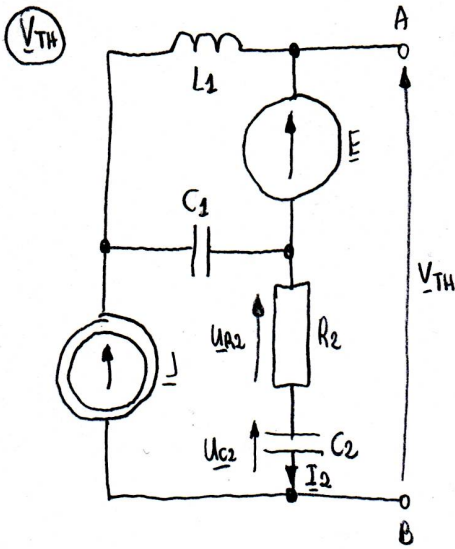
$$Z_{TH} = R_2 - jX_{C2} = \boxed{(10 - j10) \Omega}$$




$$\underline{I}_2 = \underline{I}$$

$$\underline{V}_{TH} = \underline{E} + \underline{U}_{R2} + \underline{U}_{C2}$$

$$\underline{V}_{TH} = \underline{E} + (\underline{R}_2 - jX_{C2}) \cdot \underline{I}_2$$

$$\underline{V}_{TH} = \underline{E} + (\underline{R}_2 - jX_{C2}) \underline{I}$$
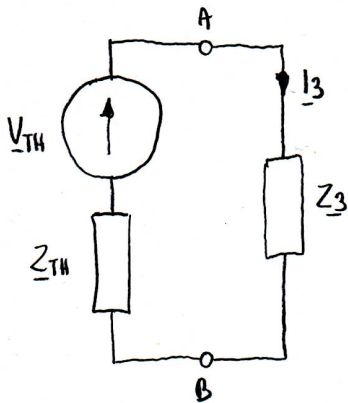
$$\underline{V}_{TH} = (10 + j10) + (10 - j10)(2 + j2) = 10 + j10 + 20 + j20 - j20 + 20 = \boxed{(50 + j10) \text{ V}}$$



$$\underline{I}_3 = \frac{\underline{V}_{TH}}{\underline{Z}_{TH} + \underline{Z}_3} = \frac{50 + j10}{10 - j10 + 10 + j10} = \frac{50 + j10}{20} = (2.5 + j0.5) \text{ A}$$

Method 1

$$|\underline{I}_3| = \sqrt{2.5^2 + 0.5^2} = \sqrt{6.25 + 0.25} = \sqrt{6.5}$$

$$P = \text{Re} \{ \underline{Z}_3 \} \cdot |\underline{I}_3|^2 = 10 \cdot (\sqrt{6.5})^2 = 10 \cdot 6.5 = \boxed{65 \text{ W}}$$

Method 2

$$\underline{U}_3 = \underline{Z}_3 \cdot \underline{I}_3 = (10 + j10) \cdot (2.5 + j0.5) = 25 + j5 + j25 - 5 = (20 + j30) \text{ V}$$

$$\underline{S}_3 = \underline{U}_3 \cdot \underline{I}_3^* = (20 + j30)(2.5 - j0.5) = 50 - j10 + j75 + 15 = (65 + j65) \text{ VA}$$

$$P_3 = \text{Re} \{ \underline{S}_3 \} = \boxed{65 \text{ W}}$$