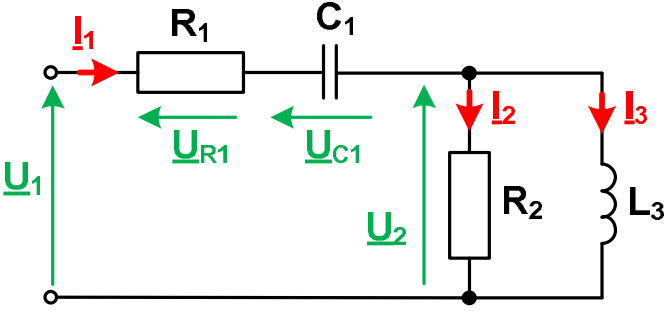
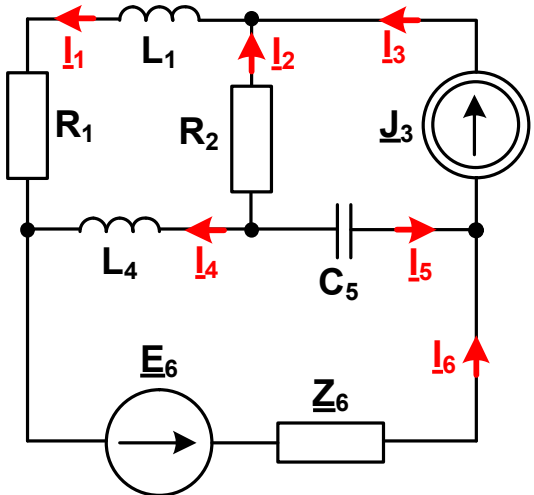
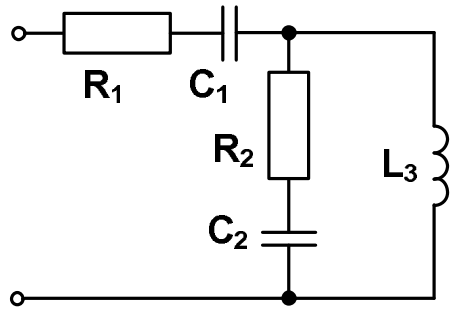


ELECTRICAL CIRCUITS 1 (IS-FEE-10070W) - TEST 2 (EXAMPLE)

PROBLEM TO BE SOLVED IN A GROUP		Points
<p>1. Draw a phasor diagram for the circuit shown in the figure.</p> 	10	
<p>2. Determine the current I_6 using Thevenin's Theorem. Calculate the active, reactive, and apparent power for Z_6.</p> <p>$J_3 = j5 \text{ A}$, $E_6 = 50 \text{ V}$, $R_1 = 10 \Omega$, $X_{L1} = 5 \Omega$, $R_2 = 15 \Omega$, $X_{L4} = 20 \Omega$, $X_{C5} = 5 \Omega$, $Z_6 = (10-j5) \Omega$</p> 	25	
PROBLEMS TO BE SOLVED INDIVIDUALLY		Points
<p>3. Calculate the equivalent impedance of the circuit shown in the figure.</p> <p>$\omega = 100 \text{ rad/s}$, $R_1 = 10 \Omega$, $R_2 = 5 \Omega$, $L_3 = 200 \text{ mH}$, $C_1 = 500 \mu\text{F}$, $C_2 = 1 \text{ mF}$</p> 	5	
<p>4. In the circuit from problem no 2, calculate the currents in all branches using any method.</p>	20	

Note: 31 points are required to pass the test.