

* SELF INDUCTANCE

L
inductance - L

X_L - inductive reactance $Z = jX_L = j\omega L$


the unit of inductance: henry

$X_L = \omega L$, $\omega = 2\pi f$ ω - angular velocity

the unit symbol: H


the unit of inductive reactance: ohm [Ω]

* INDUCTORS IN SERIES

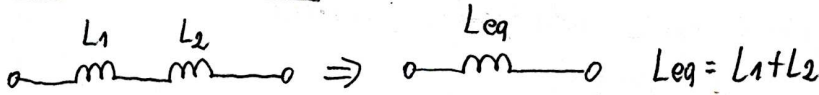

when there is no mutual coupling between inductors in series, the total inductance is the sum of the individual inductances

* INDUCTORS IN PARALLEL

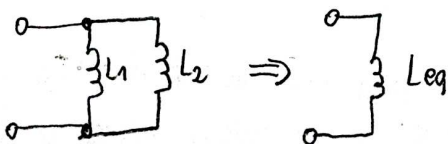

$$Leq = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2}} = \frac{L_1 \cdot L_2}{L_1 + L_2}$$

* MUTUAL INDUCTANCE



mutual inductance occurs when inductors are placed in close proximity to one another and share a common magnetic flux

X_M - mutual reactance

the letter symbol of mutual inductance: M

$$X_M = \omega M \quad \omega = 2\pi f$$

the unit of mutual inductance: henry

the unit of mutual reactance: ohm [Ω]


the unit symbol: H

$$Z = jX_M = j\omega M$$

$$M = k \cdot \sqrt{L_1 \cdot L_2} \quad k - \text{coefficient of coupling } (0 \leq k \leq 1)$$

* the coefficient k is an indication of how much flux in one coil is linked with the other coil

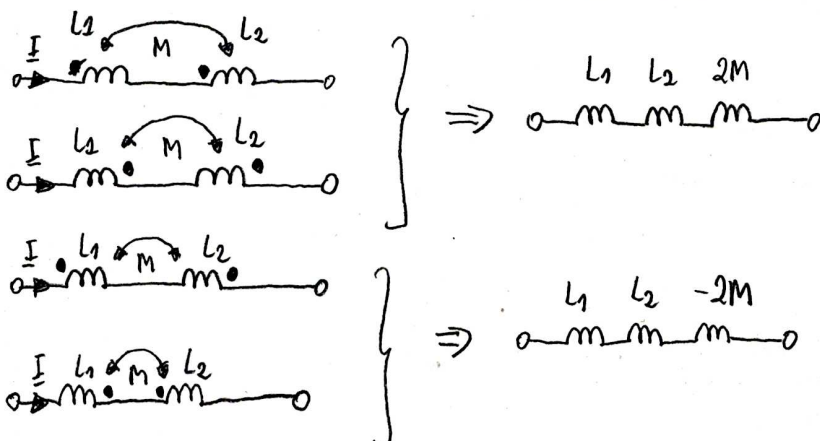
* INDUCTORS IN SERIES WITH MUTUAL COUPLING



* if all the flux in one coil reaches the other coil, then we have 100% coupling and $k=1$

* if there is no coupling $k=0$

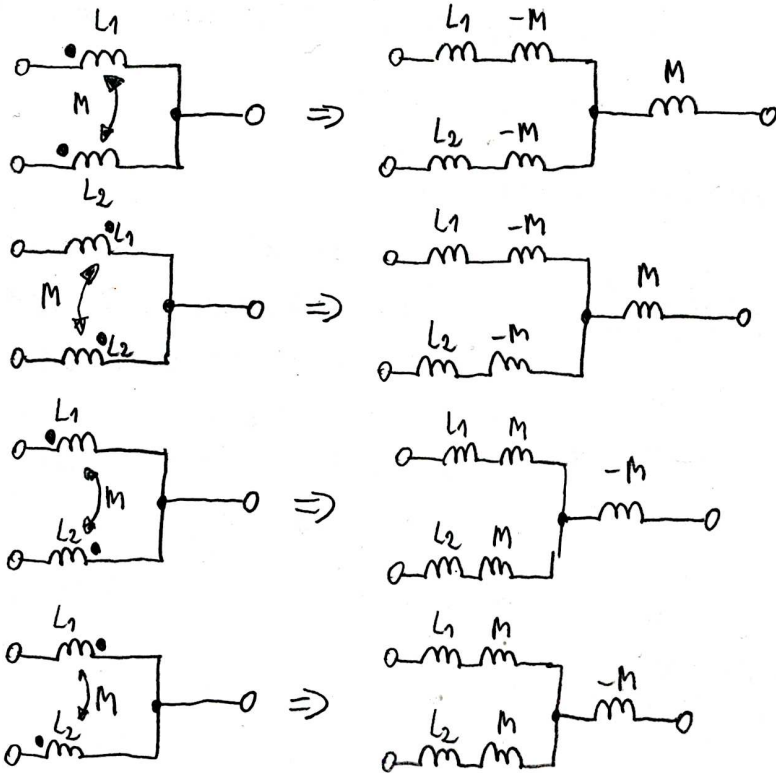
* ELIMINATION OF COUPLING IN ELEMENTS HAVING A COMMON NODE



PROBLEM #1


Eliminate couplings and calculate the equivalent inductance of the circuits shown in the figures. $L_1=0.1\text{H}$, $L_2=0.2\text{H}$, $L_3=0.4\text{H}$, $M_{12}=0.1\text{H}$, $M_{23}=0.25\text{H}$, $M_{13}=0.2\text{H}$.

a)


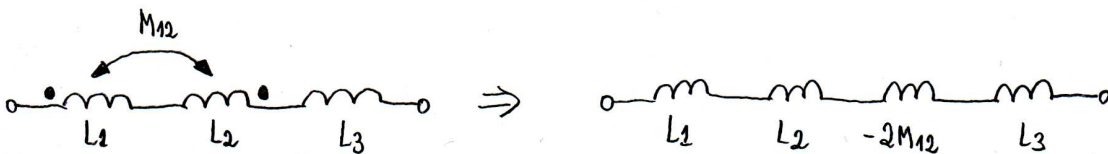


$$L_{eq} = L_1 + L_2 - 2M_{12} + L_3 = 0.1 + 0.2 - 2 \cdot 0.1 + 0.4 = \boxed{0.5\text{H}}$$

b)

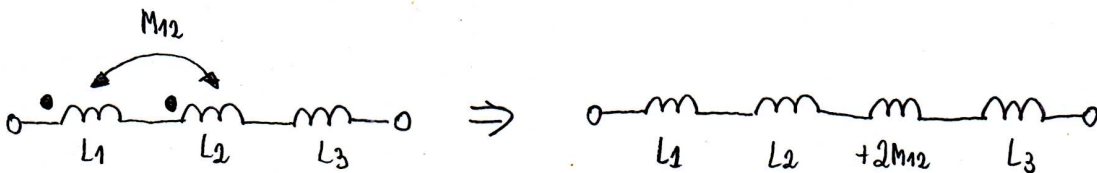

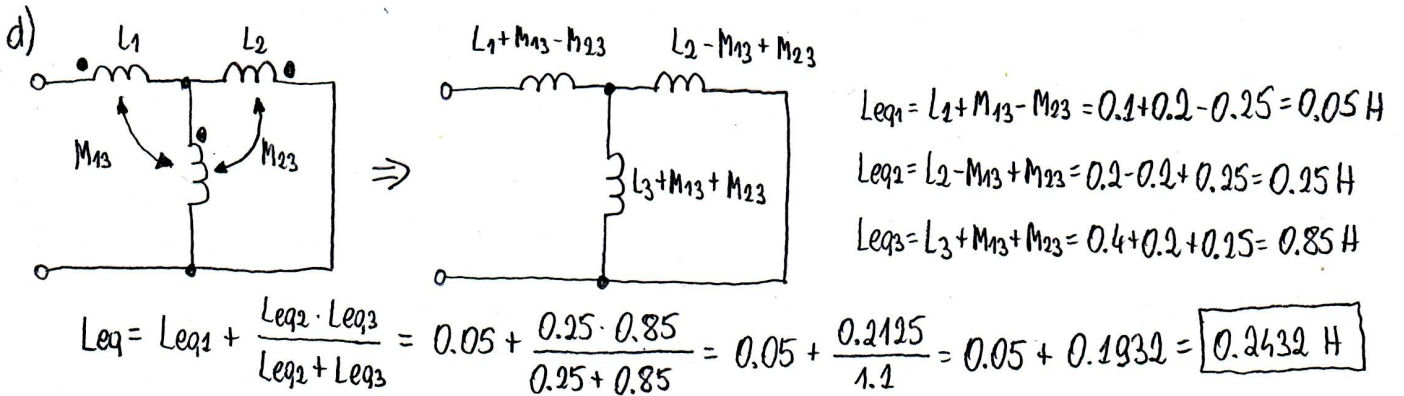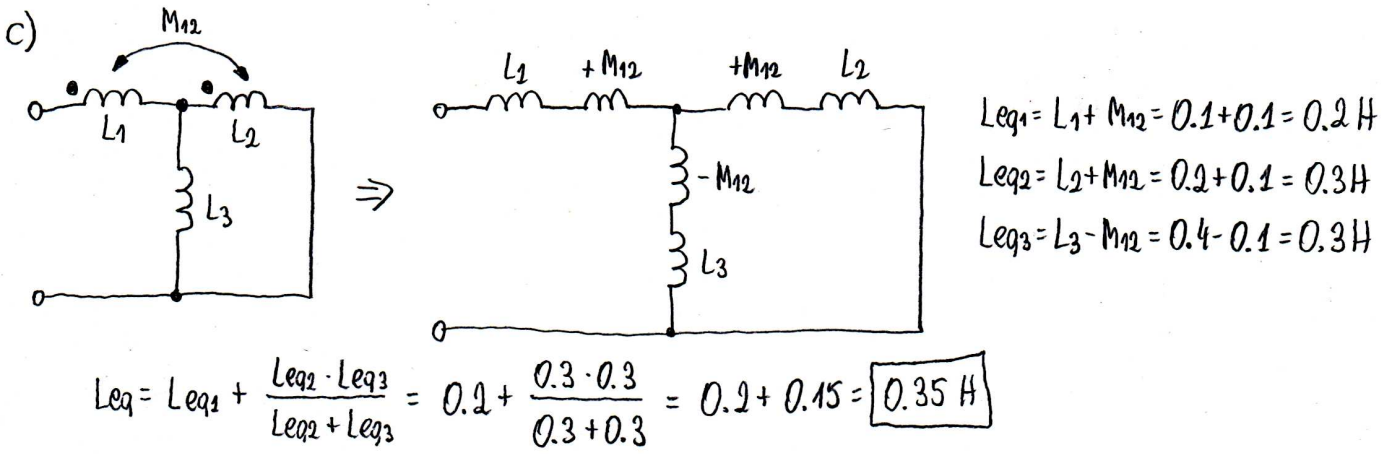
$$L_{eq} = L_1 + L_2 + 2M_{12} + L_3 = 0.1 + 0.2 + 2 \cdot 0.1 + 0.4 = \boxed{0.9\text{H}}$$




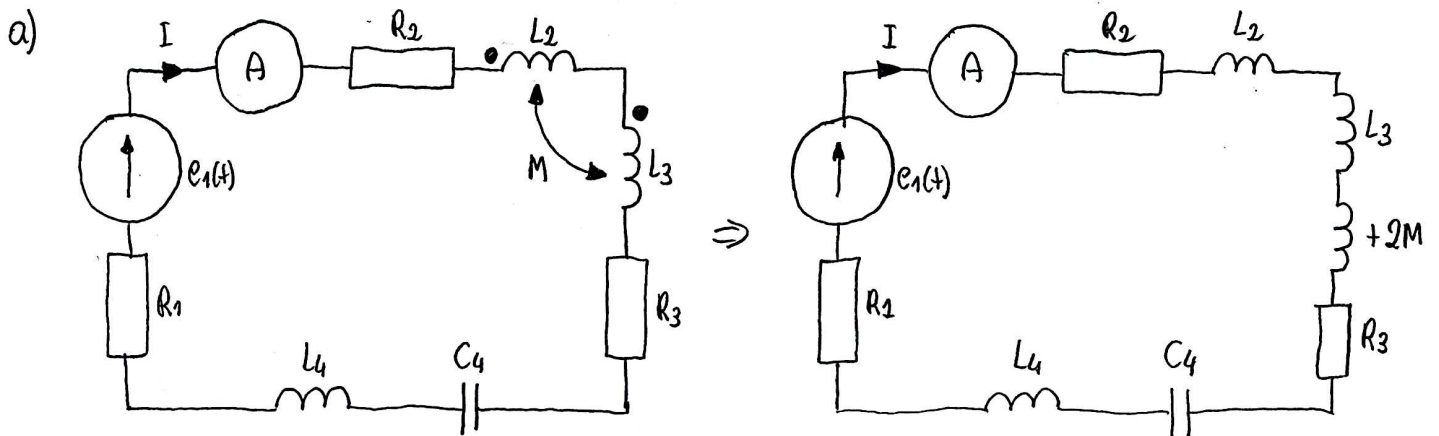PROBLEM #2

Calculate ammeter readings in the circuits shown in the figures. $M = 0.1 \text{ H}$
 $e_1(t) = 100\sqrt{2} \sin(100t + 90^\circ) \text{ V}$, $R_1 = 15 \Omega$, $R_2 = 30 \Omega$, $L_2 = 0.1 \text{ H}$, $L_3 = 0.4 \text{ H}$, $R_3 = 15 \Omega$, $C_4 = 500 \mu\text{F}$, $L_4 = 0.3 \text{ H}$.




Elimination of coupling

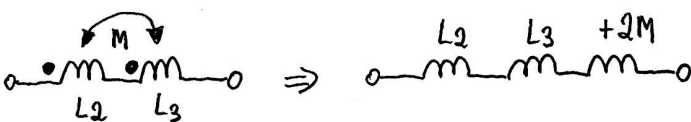


$Z = R_1 + jX_{L2} + jX_{L3} + 2jX_M + R_3 + jX_{L4} - jX_{C4} + R_2$
 $Z = 30 + j10 + j40 + j20 + 15 + j30 - j20 + 15 = (60 + j80) \Omega$
 $I = \frac{U}{Z} = \frac{j100}{60 + j80} = (0.8 + j0.6) \text{ A}$
 $I_A = |I| = \sqrt{0.8^2 + 0.6^2} = \boxed{1 \text{ A}}$

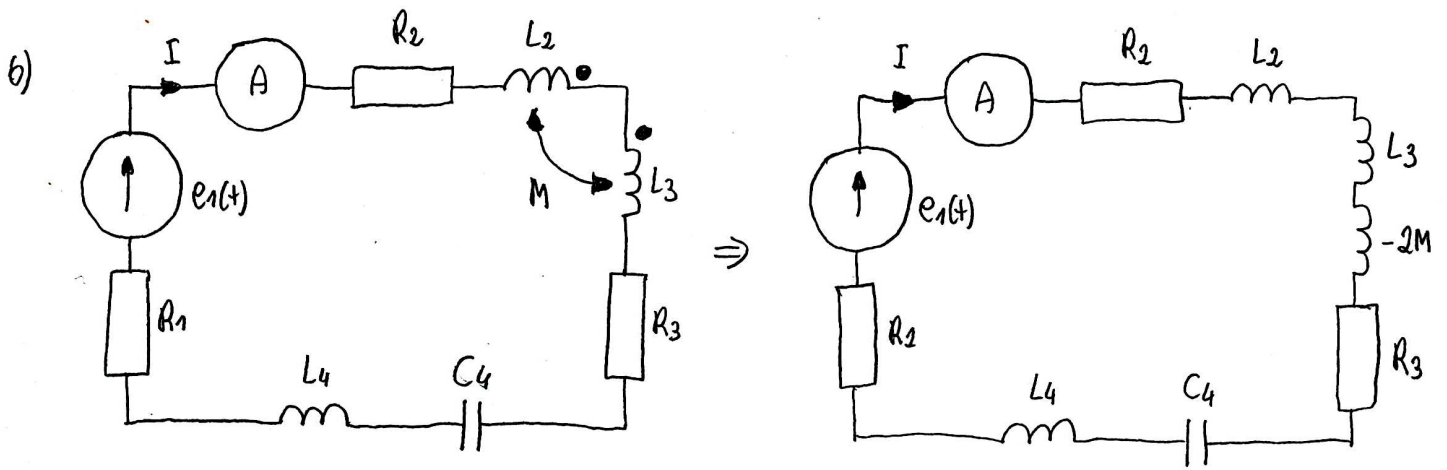$E_1 = 100 (\cos 90^\circ + j \sin 90^\circ) = j100 \text{ V}$
 $X_{L2} = \omega L_2 = 100 \cdot 0.1 = 10 \Omega$
 $X_{L3} = \omega L_3 = 100 \cdot 0.4 = 40 \Omega$
 $X_M = \omega M = 100 \cdot 0.1 = 10 \Omega$
 $X_{L4} = \omega L_4 = 100 \cdot 0.3 = 30 \Omega$
 $X_{C4} = \frac{1}{\omega C_4} = \frac{1}{100 \cdot 500 \cdot 10^{-6}} = 20 \Omega$



Elimination of coupling

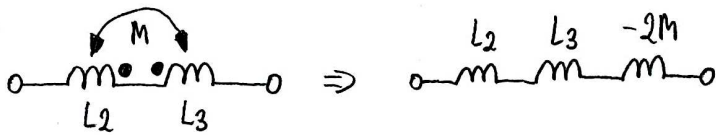

$$\underline{Z} = R_1 + R_2 + jX_{L2} + jX_{L3} - j2X_M + R_3 - jX_{C4} + jX_{L4} = 15 + 30 + j10 + j40 - j20 + 15 - j20 + j30 = (60 + j40) \Omega$$

$$\underline{I} = \frac{U}{\underline{Z}} = \frac{j100}{60 + j40} = (0.7692 + j1.1538) \text{ A} \quad I_A = |\underline{I}| = \sqrt{0.7692^2 + 1.1538^2} = \boxed{1.39 \text{ A}}$$