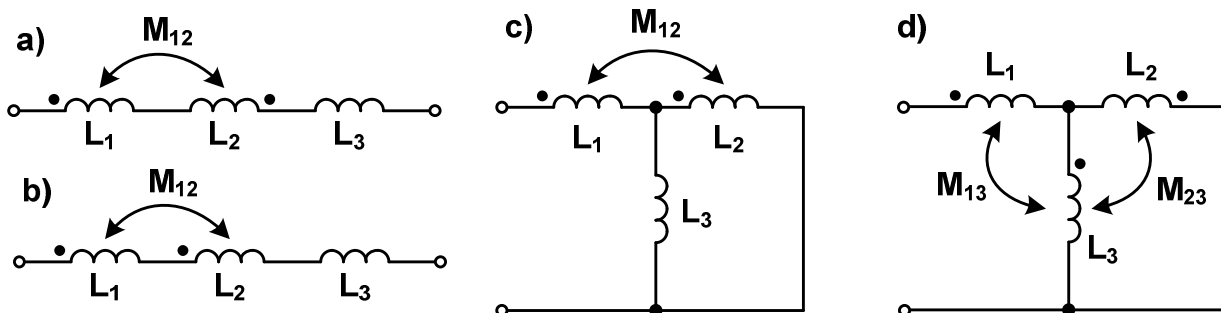


Module name: **Electrical Circuits 2**
 Module ID: **IS-FEE-10085S**
 Module type: **Class**
 Semester: **summer 2023/2024**
 Instructor: **Jarosław Forenc, j.forenc@pb.edu.pl**


Class 2 (05.03.2024)

1. Eliminate couplings and calculate the equivalent inductance of the circuits shown in the figures. $L_1 = 0.1 \text{ H}$, $L_2 = 0.2 \text{ H}$, $L_3 = 0.4 \text{ H}$, $M_{12} = 0.1 \text{ H}$, $M_{23} = 0.25 \text{ H}$, $M_{13} = 0.2 \text{ H}$.



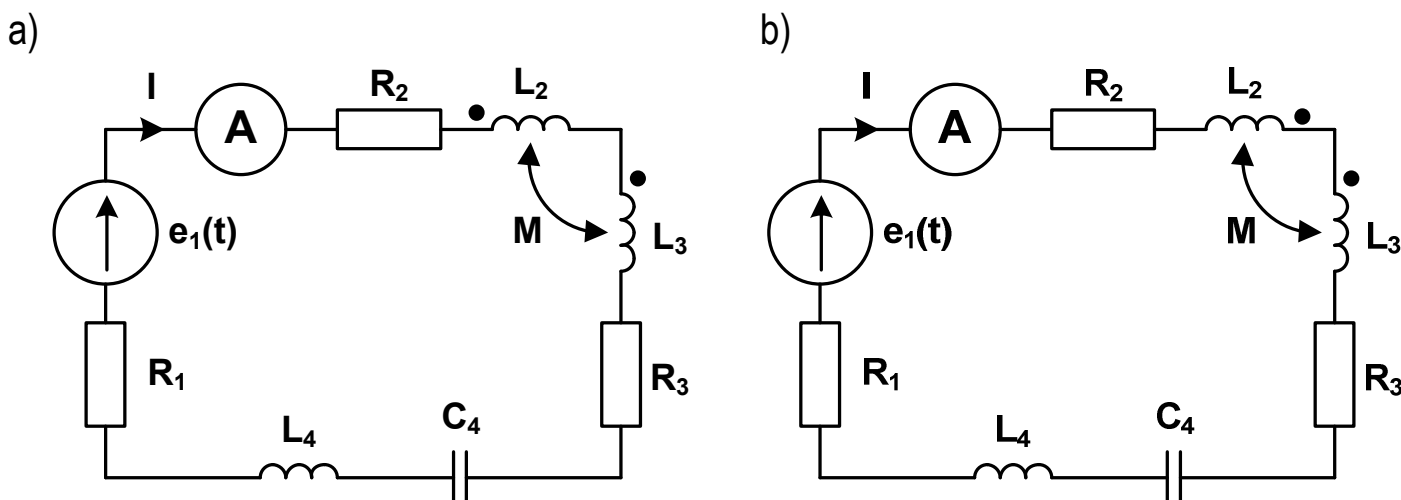2. Calculate **ammeter readings** in the circuits shown in the figures.


$e_1(t) = 100\sqrt{2}\sin(100t+90^\circ) \text{ V}$, $R_1 = 15 \ \Omega$, $R_2 = 30 \ \Omega$, $L_2 = 0.1 \text{ H}$, $L_3 = 0.4 \text{ H}$,
 $R_3 = 15 \ \Omega$, $C_4 = 500 \ \mu\text{F}$, $L_4 = 0.3 \text{ H}$, $M = 0.1 \text{ H}$.



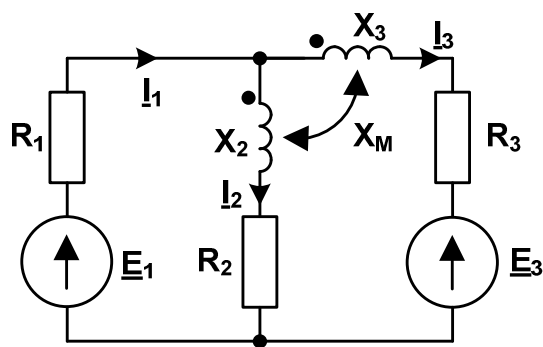3. Calculate the **currents** in all branches of the circuit presented in the figure.

$$\underline{E}_1 = 100 \text{ V}, \underline{E}_3 = 500 \text{ V}, R_1 = R_2 = R_3 = 50 \ \Omega,$$

$$X_M = 50 \ \Omega, X_2 = X_3 = 100 \ \Omega.$$




4. What should be the power of the resistor R_1 so that it is not damaged during operation in the circuit shown in the figure.

$$\underline{U} = 10 \text{ V}, R_1 = 10 \ \Omega, X_{L1} = 25 \ \Omega,$$

$$X_{L2} = 40 \ \Omega, X_M = 10 \ \Omega, X_{C3} = 20 \ \Omega.$$

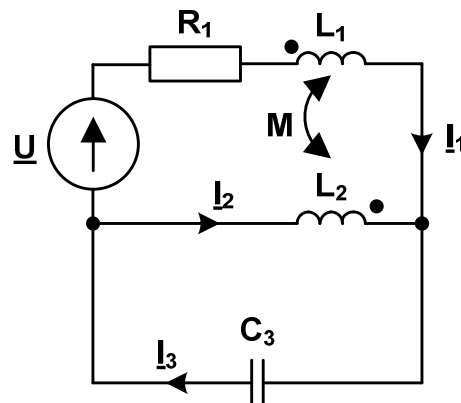Standard resistor power: 0.125 W, 0.25 W, 0.4 W, 0.5 W, 0.6 W, 0.75 W, 1 W, 1.2 W, 2 W, 3 W, 5 W, 7 W, 8 W, 9 W.



05.03.2024


Jarosław Forenc, PhD

j.forenc@pb.edu.pl

Module name: **Electrical Circuits 2**
 Module ID: **IS-FEE-10085S**
 Module type: **Class**
 Semester: **summer 2023/2024**
 Instructor: **Jarosław Forenc, j.forenc@pb.edu.pl**


Class 2 (05.03.2024)

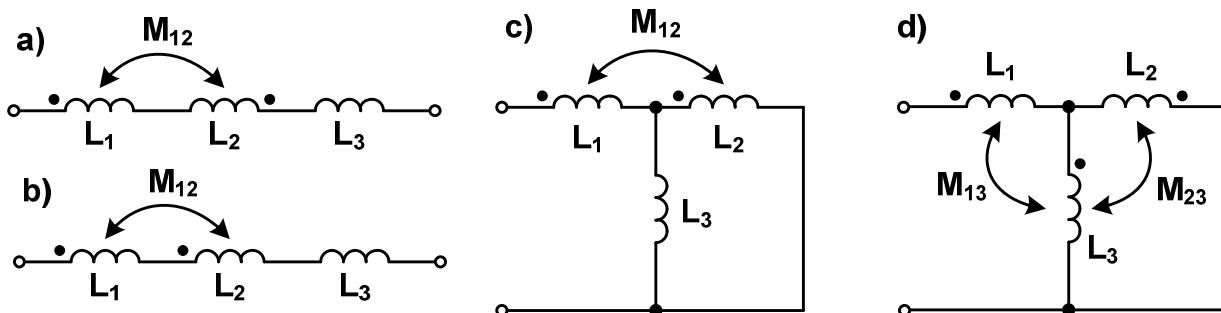1. Eliminate couplings and calculate the equivalent inductance of the circuits shown in the figures. $L_1 = 0.1 \text{ H}$, $L_2 = 0.2 \text{ H}$, $L_3 = 0.4 \text{ H}$, $M_{12} = 0.1 \text{ H}$, $M_{23} = 0.25 \text{ H}$, $M_{13} = 0.2 \text{ H}$.



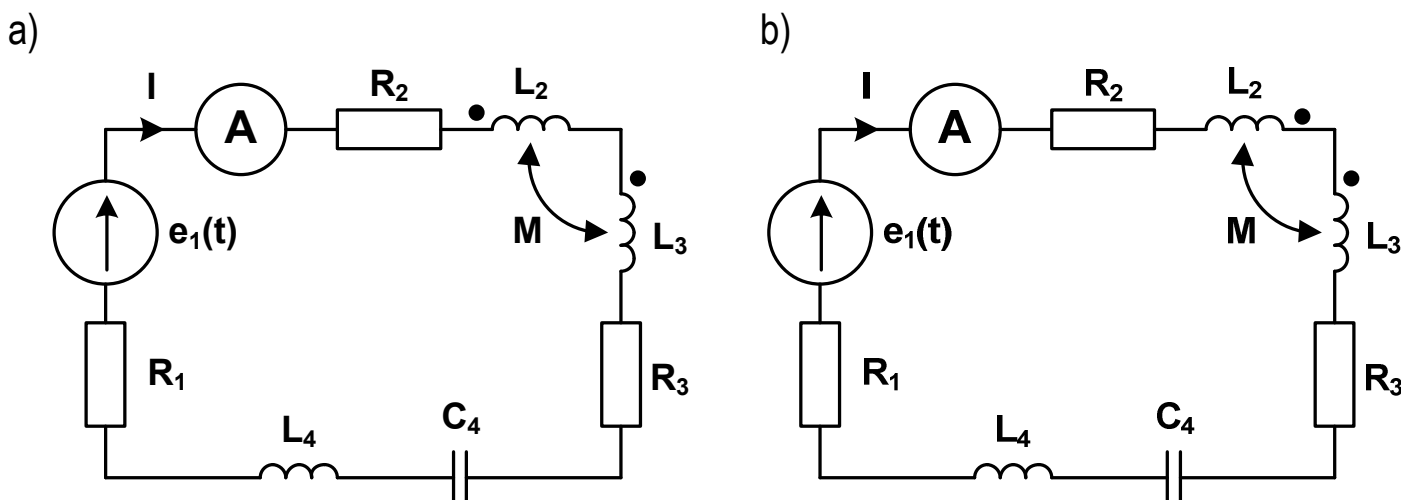2. Calculate **ammeter readings** in the circuits shown in the figures.


$e_1(t) = 100\sqrt{2}\sin(100t+90^\circ) \text{ V}$, $R_1 = 15 \ \Omega$, $R_2 = 30 \ \Omega$, $L_2 = 0.1 \text{ H}$, $L_3 = 0.4 \text{ H}$,
 $R_3 = 15 \ \Omega$, $C_4 = 500 \ \mu\text{F}$, $L_4 = 0.3 \text{ H}$, $M = 0.1 \text{ H}$.



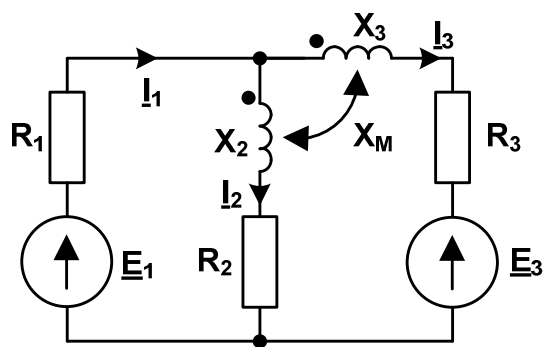3. Calculate the **currents** in all branches of the circuit presented in the figure.

$$\underline{E}_1 = 100 \text{ V}, \underline{E}_3 = 500 \text{ V}, R_1 = R_2 = R_3 = 50 \ \Omega,$$

$$X_M = 50 \ \Omega, X_2 = X_3 = 100 \ \Omega.$$




4. What should be the power of the resistor R_1 so that it is not damaged during operation in the circuit shown in the figure.

$$\underline{U} = 10 \text{ V}, R_1 = 10 \ \Omega, X_{L1} = 25 \ \Omega,$$

$$X_{L2} = 40 \ \Omega, X_M = 10 \ \Omega, X_{C3} = 20 \ \Omega.$$

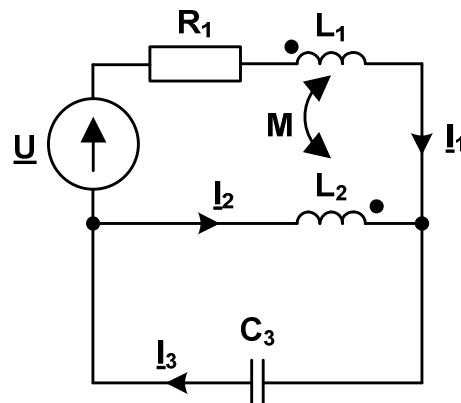Standard resistor power: 0.125 W, 0.25 W, 0.4 W, 0.5 W, 0.6 W, 0.75 W, 1 W, 1.2 W, 2 W, 3 W, 5 W, 7 W, 8 W, 9 W.



05.03.2024


Jarosław Forenc, PhD

j.forenc@pb.edu.pl

Module name: **Electrical Circuits 2**
 Module ID: **IS-FEE-10085S**
 Module type: **Class**
 Semester: **summer 2023/2024**
 Instructor: **Jarosław Forenc, j.forenc@pb.edu.pl**


Class 2 (05.03.2024)

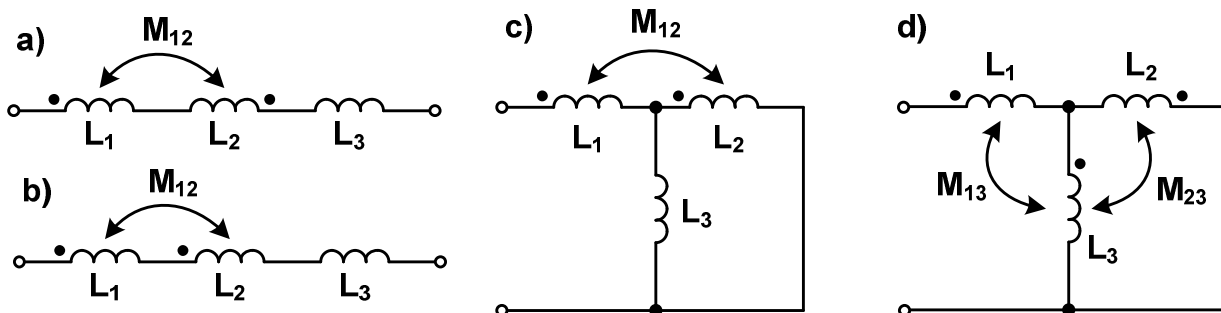1. Eliminate couplings and calculate the equivalent inductance of the circuits shown in the figures. $L_1 = 0.1 \text{ H}$, $L_2 = 0.2 \text{ H}$, $L_3 = 0.4 \text{ H}$, $M_{12} = 0.1 \text{ H}$, $M_{23} = 0.25 \text{ H}$, $M_{13} = 0.2 \text{ H}$.



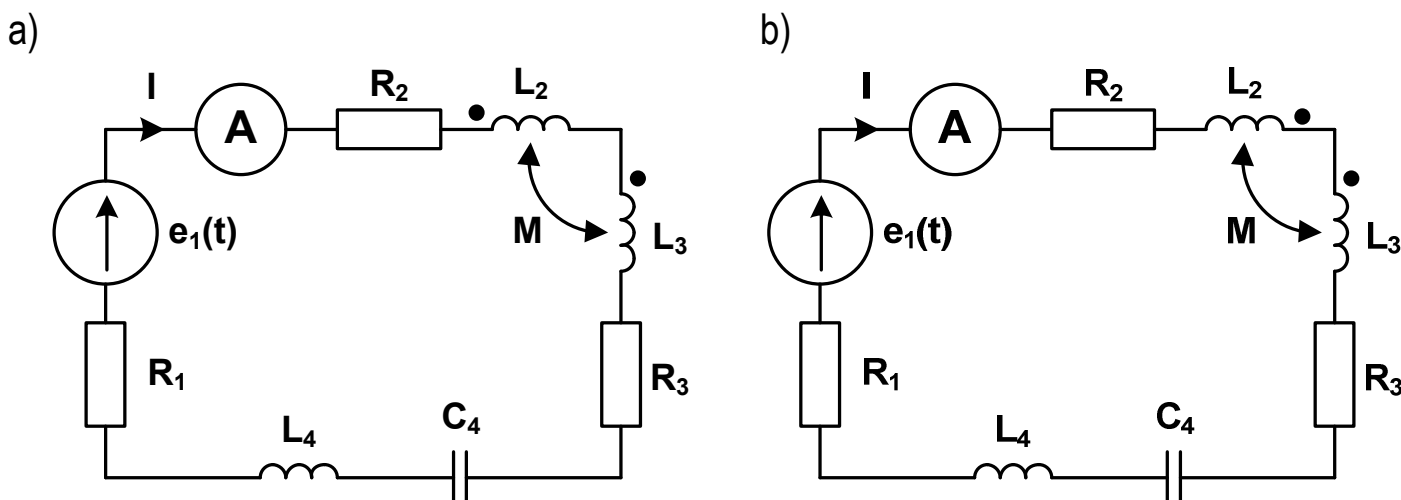2. Calculate **ammeter readings** in the circuits shown in the figures.


$e_1(t) = 100\sqrt{2}\sin(100t+90^\circ) \text{ V}$, $R_1 = 15 \ \Omega$, $R_2 = 30 \ \Omega$, $L_2 = 0.1 \text{ H}$, $L_3 = 0.4 \text{ H}$,
 $R_3 = 15 \ \Omega$, $C_4 = 500 \ \mu\text{F}$, $L_4 = 0.3 \text{ H}$, $M = 0.1 \text{ H}$.



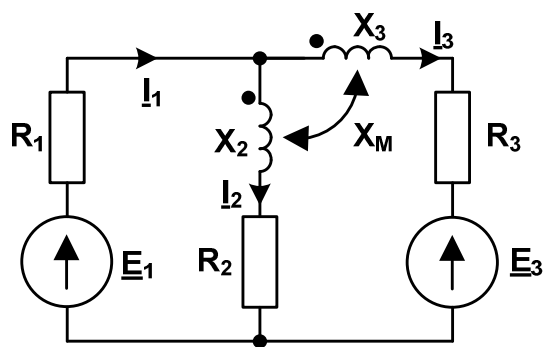3. Calculate the **currents** in all branches of the circuit presented in the figure.

$$\underline{E}_1 = 100 \text{ V}, \underline{E}_3 = 500 \text{ V}, R_1 = R_2 = R_3 = 50 \ \Omega,$$

$$X_M = 50 \ \Omega, X_2 = X_3 = 100 \ \Omega.$$




4. What should be the power of the resistor R_1 so that it is not damaged during operation in the circuit shown in the figure.

$$\underline{U} = 10 \text{ V}, R_1 = 10 \ \Omega, X_{L1} = 25 \ \Omega,$$

$$X_{L2} = 40 \ \Omega, X_M = 10 \ \Omega, X_{C3} = 20 \ \Omega.$$

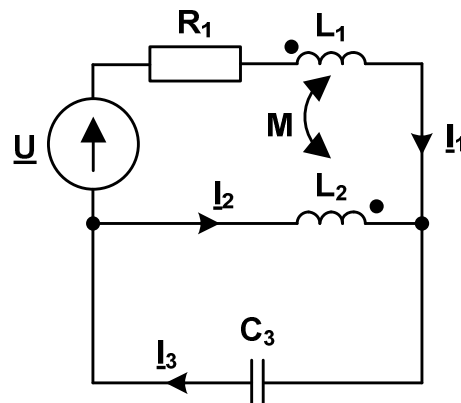Standard resistor power: 0.125 W, 0.25 W, 0.4 W, 0.5 W, 0.6 W, 0.75 W, 1 W, 1.2 W, 2 W, 3 W, 5 W, 7 W, 8 W, 9 W.



05.03.2024


Jarosław Forenc, PhD

j.forenc@pb.edu.pl

Module name: **Electrical Circuits 2**
 Module ID: **IS-FEE-10085S**
 Module type: **Class**
 Semester: **summer 2023/2024**
 Instructor: **Jarosław Forenc, j.forenc@pb.edu.pl**


Class 2 (05.03.2024)

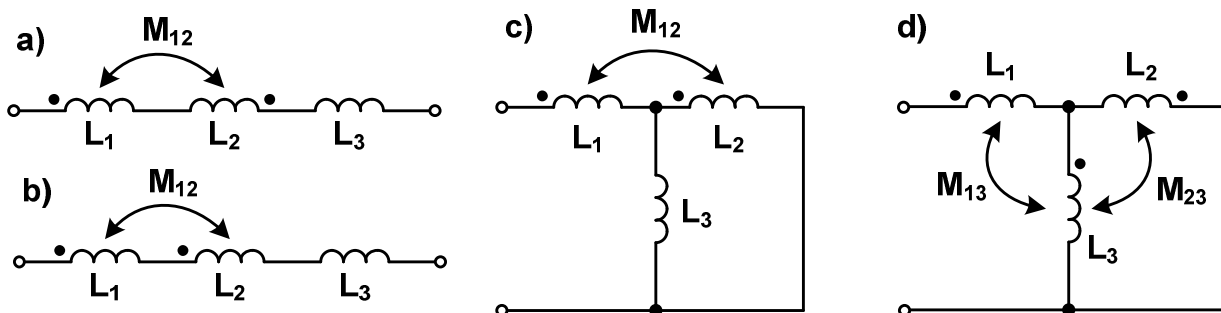1. Eliminate couplings and calculate the equivalent inductance of the circuits shown in the figures. $L_1 = 0.1 \text{ H}$, $L_2 = 0.2 \text{ H}$, $L_3 = 0.4 \text{ H}$, $M_{12} = 0.1 \text{ H}$, $M_{23} = 0.25 \text{ H}$, $M_{13} = 0.2 \text{ H}$.



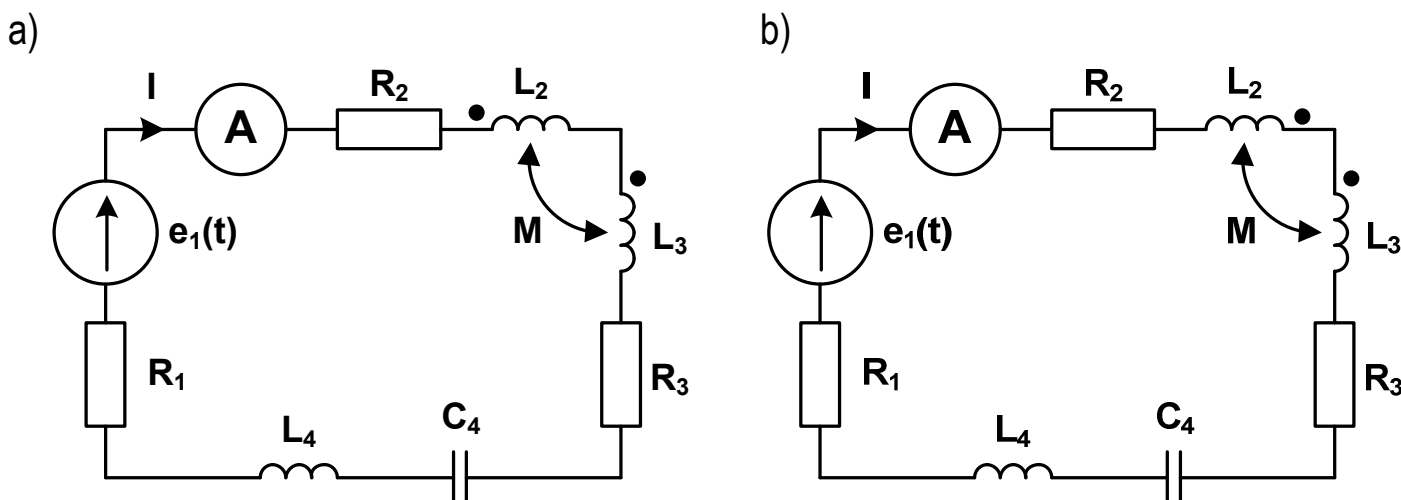2. Calculate **ammeter readings** in the circuits shown in the figures.


$e_1(t) = 100\sqrt{2}\sin(100t+90^\circ) \text{ V}$, $R_1 = 15 \ \Omega$, $R_2 = 30 \ \Omega$, $L_2 = 0.1 \text{ H}$, $L_3 = 0.4 \text{ H}$,
 $R_3 = 15 \ \Omega$, $C_4 = 500 \ \mu\text{F}$, $L_4 = 0.3 \text{ H}$, $M = 0.1 \text{ H}$.



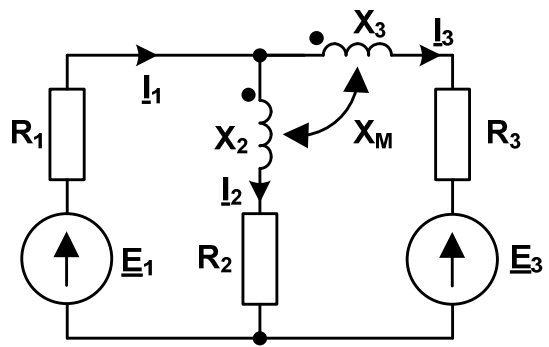3. Calculate the **currents** in all branches of the circuit presented in the figure.

$$\underline{E}_1 = 100 \text{ V}, \underline{E}_3 = 500 \text{ V}, R_1 = R_2 = R_3 = 50 \ \Omega,$$

$$X_M = 50 \ \Omega, X_2 = X_3 = 100 \ \Omega.$$




4. What should be the power of the resistor R_1 so that it is not damaged during operation in the circuit shown in the figure.

$$\underline{U} = 10 \text{ V}, R_1 = 10 \ \Omega, X_{L1} = 25 \ \Omega,$$

$$X_{L2} = 40 \ \Omega, X_M = 10 \ \Omega, X_{C3} = 20 \ \Omega.$$

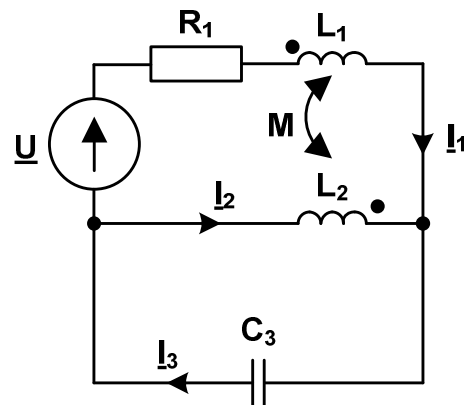Standard resistor power: 0.125 W, 0.25 W, 0.4 W, 0.5 W, 0.6 W, 0.75 W, 1 W, 1.2 W, 2 W, 3 W, 5 W, 7 W, 8 W, 9 W.



05.03.2024


Jarosław Forenc, PhD

j.forenc@pb.edu.pl

Module name: **Electrical Circuits 2**
 Module ID: **IS-FEE-10085S**
 Module type: **Class**
 Semester: **summer 2023/2024**
 Instructor: **Jarosław Forenc, j.forenc@pb.edu.pl**


Class 2 (05.03.2024)

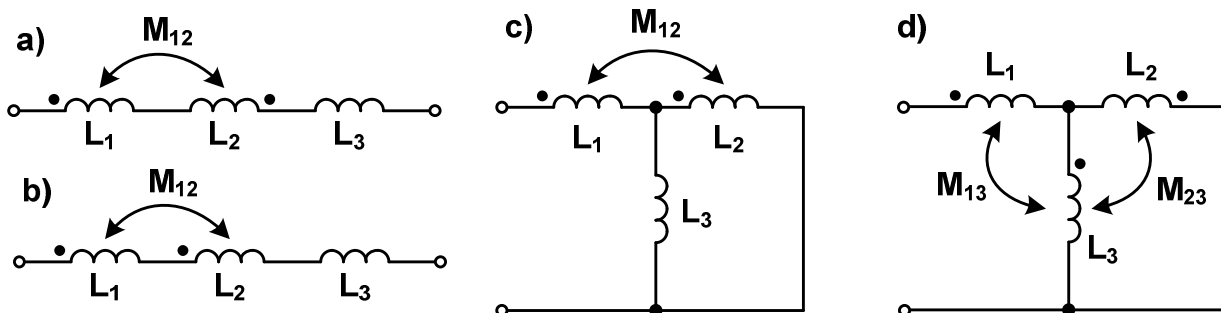1. Eliminate couplings and calculate the equivalent inductance of the circuits shown in the figures. $L_1 = 0.1 \text{ H}$, $L_2 = 0.2 \text{ H}$, $L_3 = 0.4 \text{ H}$, $M_{12} = 0.1 \text{ H}$, $M_{23} = 0.25 \text{ H}$, $M_{13} = 0.2 \text{ H}$.



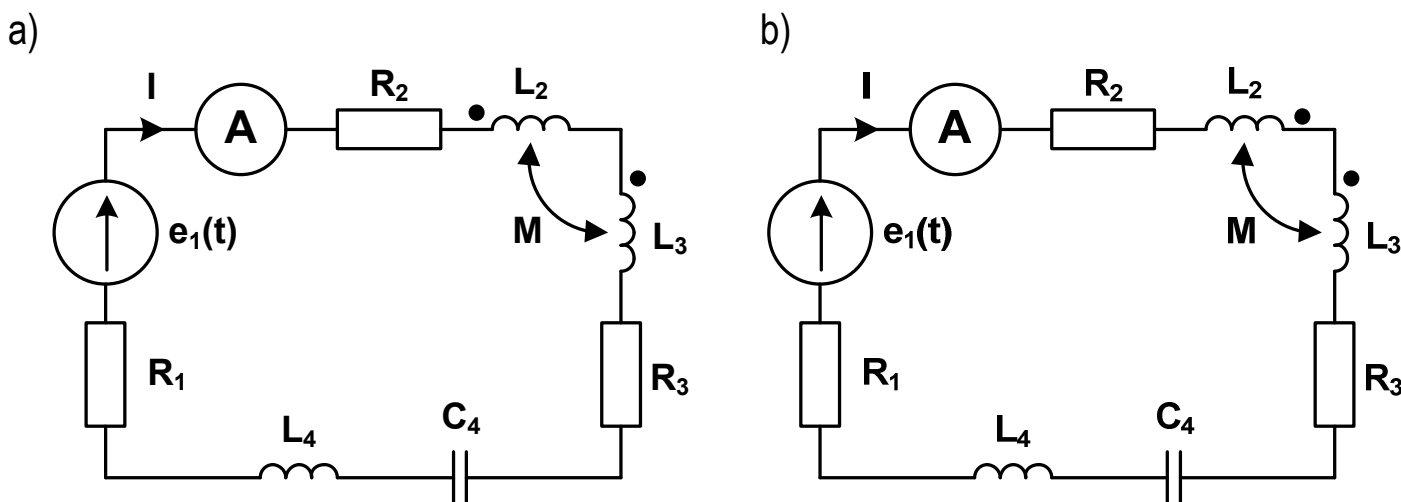2. Calculate **ammeter readings** in the circuits shown in the figures.


$e_1(t) = 100\sqrt{2}\sin(100t+90^\circ) \text{ V}$, $R_1 = 15 \ \Omega$, $R_2 = 30 \ \Omega$, $L_2 = 0.1 \text{ H}$, $L_3 = 0.4 \text{ H}$,
 $R_3 = 15 \ \Omega$, $C_4 = 500 \ \mu\text{F}$, $L_4 = 0.3 \text{ H}$, $M = 0.1 \text{ H}$.



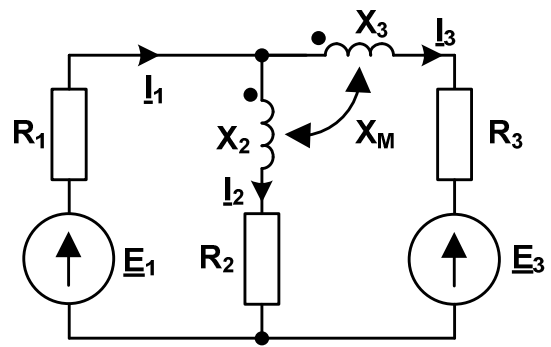3. Calculate the **currents** in all branches of the circuit presented in the figure.

$$\underline{E}_1 = 100 \text{ V}, \underline{E}_3 = 500 \text{ V}, R_1 = R_2 = R_3 = 50 \ \Omega,$$

$$X_M = 50 \ \Omega, X_2 = X_3 = 100 \ \Omega.$$




4. What should be the power of the resistor R_1 so that it is not damaged during operation in the circuit shown in the figure.

$$\underline{U} = 10 \text{ V}, R_1 = 10 \ \Omega, X_{L1} = 25 \ \Omega,$$

$$X_{L2} = 40 \ \Omega, X_M = 10 \ \Omega, X_{C3} = 20 \ \Omega.$$

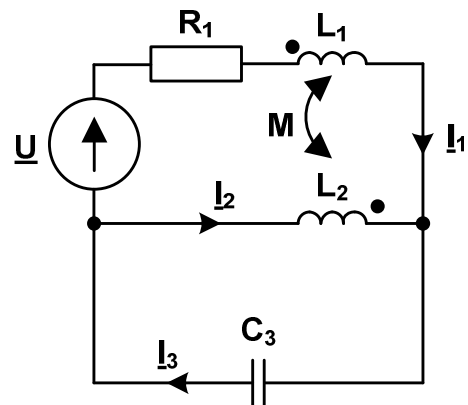Standard resistor power: 0.125 W, 0.25 W, 0.4 W, 0.5 W, 0.6 W, 0.75 W, 1 W, 1.2 W, 2 W, 3 W, 5 W, 7 W, 8 W, 9 W.



05.03.2024


Jarosław Forenc, PhD

j.forenc@pb.edu.pl

Module name: **Electrical Circuits 2**
 Module ID: **IS-FEE-10085S**
 Module type: **Class**
 Semester: **summer 2023/2024**
 Instructor: **Jarosław Forenc, j.forenc@pb.edu.pl**


Class 2 (05.03.2024)

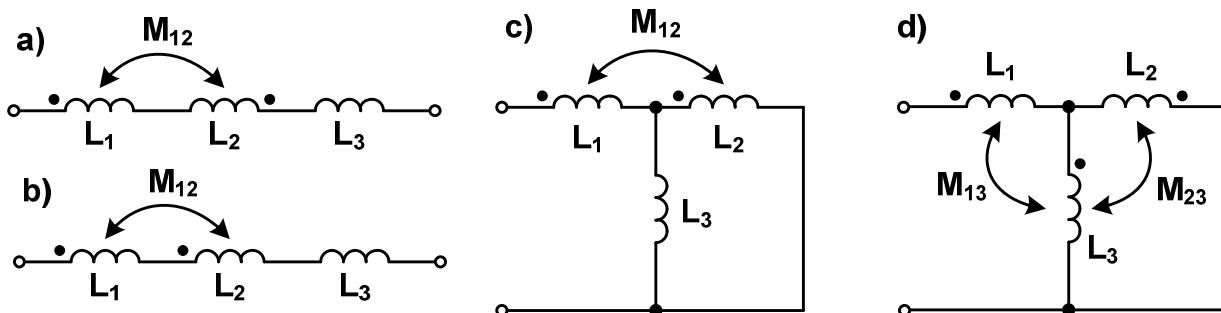1. Eliminate couplings and calculate the equivalent inductance of the circuits shown in the figures. $L_1 = 0.1 \text{ H}$, $L_2 = 0.2 \text{ H}$, $L_3 = 0.4 \text{ H}$, $M_{12} = 0.1 \text{ H}$, $M_{23} = 0.25 \text{ H}$, $M_{13} = 0.2 \text{ H}$.



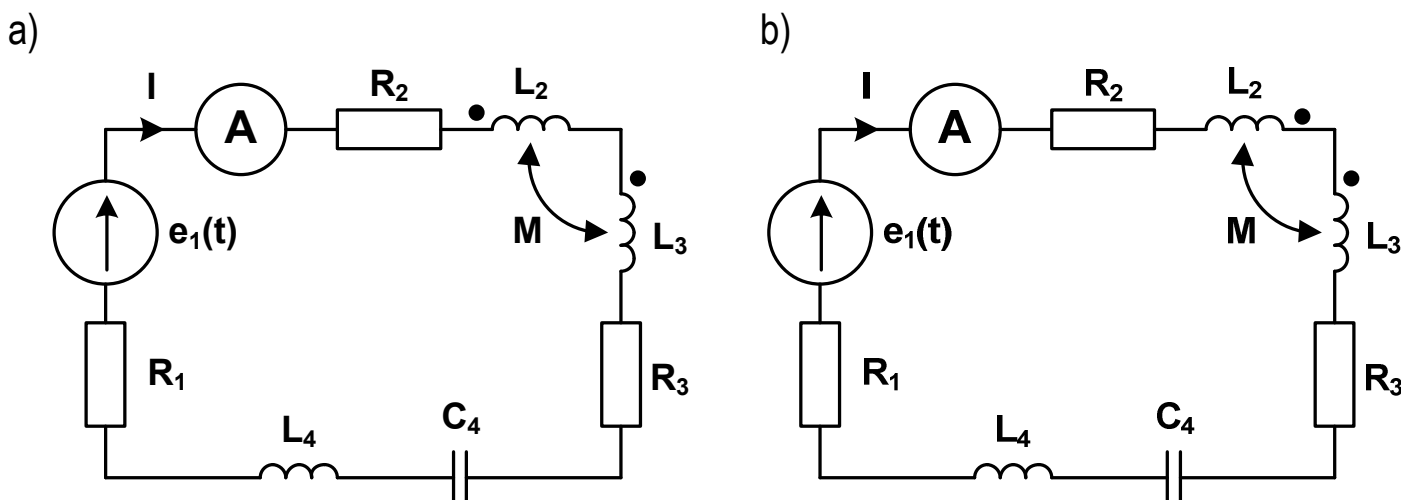2. Calculate **ammeter readings** in the circuits shown in the figures.


$e_1(t) = 100\sqrt{2}\sin(100t+90^\circ) \text{ V}$, $R_1 = 15 \ \Omega$, $R_2 = 30 \ \Omega$, $L_2 = 0.1 \text{ H}$, $L_3 = 0.4 \text{ H}$,
 $R_3 = 15 \ \Omega$, $C_4 = 500 \ \mu\text{F}$, $L_4 = 0.3 \text{ H}$, $M = 0.1 \text{ H}$.



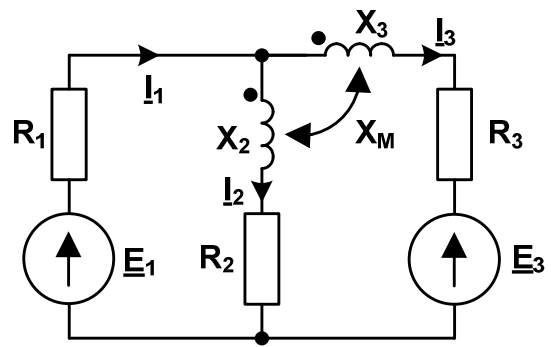3. Calculate the **currents** in all branches of the circuit presented in the figure.

$$\underline{E}_1 = 100 \text{ V}, \underline{E}_3 = 500 \text{ V}, R_1 = R_2 = R_3 = 50 \ \Omega,$$

$$X_M = 50 \ \Omega, X_2 = X_3 = 100 \ \Omega.$$




4. What should be the power of the resistor R_1 so that it is not damaged during operation in the circuit shown in the figure.

$$\underline{U} = 10 \text{ V}, R_1 = 10 \ \Omega, X_{L1} = 25 \ \Omega,$$

$$X_{L2} = 40 \ \Omega, X_M = 10 \ \Omega, X_{C3} = 20 \ \Omega.$$

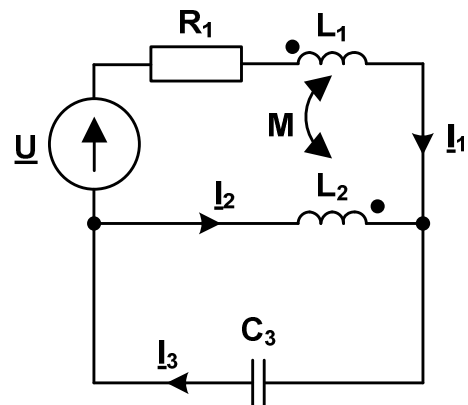Standard resistor power: 0.125 W, 0.25 W, 0.4 W, 0.5 W, 0.6 W, 0.75 W, 1 W, 1.2 W, 2 W, 3 W, 5 W, 7 W, 8 W, 9 W.



05.03.2024


Jarosław Forenc, PhD

j.forenc@pb.edu.pl

Module name: **Electrical Circuits 2**
 Module ID: **IS-FEE-10085S**
 Module type: **Class**
 Semester: **summer 2023/2024**
 Instructor: **Jarosław Forenc, j.forenc@pb.edu.pl**


Class 2 (05.03.2024)

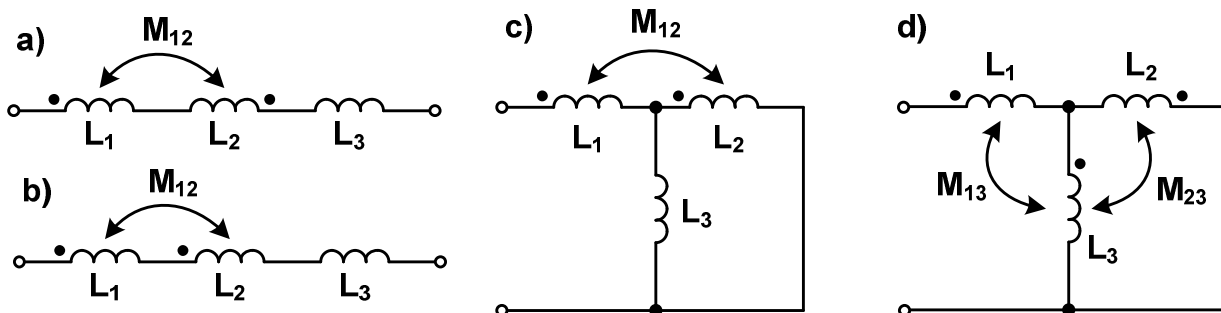1. Eliminate couplings and calculate the equivalent inductance of the circuits shown in the figures. $L_1 = 0.1 \text{ H}$, $L_2 = 0.2 \text{ H}$, $L_3 = 0.4 \text{ H}$, $M_{12} = 0.1 \text{ H}$, $M_{23} = 0.25 \text{ H}$, $M_{13} = 0.2 \text{ H}$.



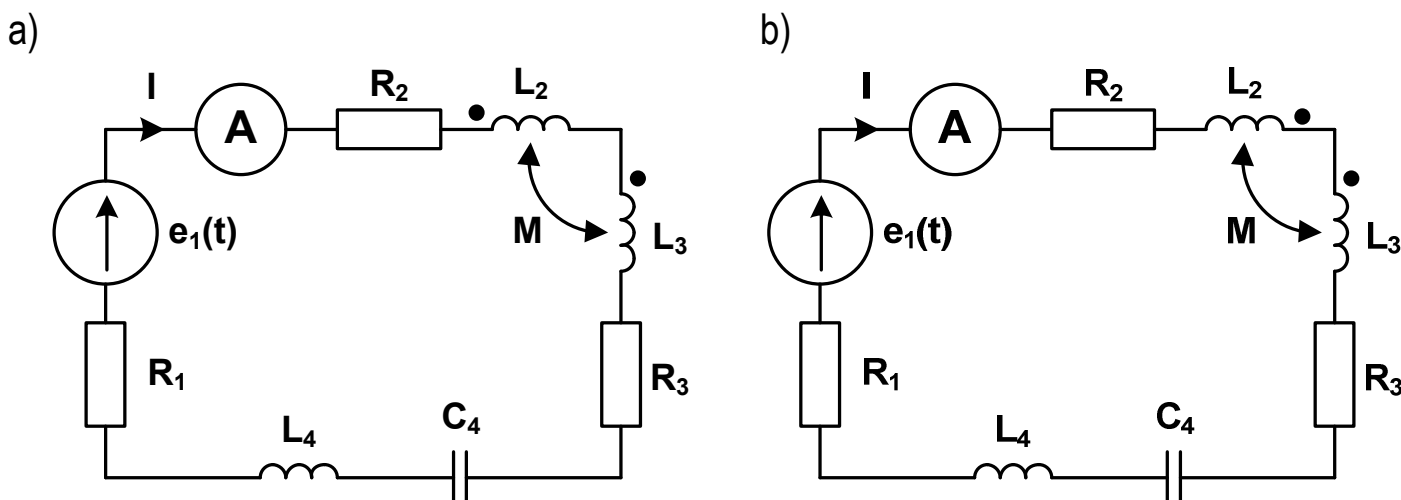2. Calculate **ammeter readings** in the circuits shown in the figures.


$e_1(t) = 100\sqrt{2}\sin(100t+90^\circ) \text{ V}$, $R_1 = 15 \ \Omega$, $R_2 = 30 \ \Omega$, $L_2 = 0.1 \text{ H}$, $L_3 = 0.4 \text{ H}$,
 $R_3 = 15 \ \Omega$, $C_4 = 500 \ \mu\text{F}$, $L_4 = 0.3 \text{ H}$, $M = 0.1 \text{ H}$.



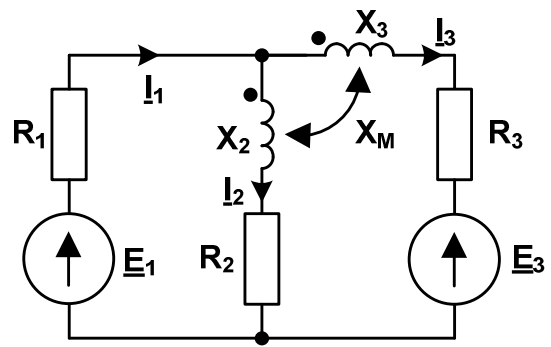3. Calculate the **currents** in all branches of the circuit presented in the figure.

$$\underline{E}_1 = 100 \text{ V}, \underline{E}_3 = 500 \text{ V}, R_1 = R_2 = R_3 = 50 \ \Omega,$$

$$X_M = 50 \ \Omega, X_2 = X_3 = 100 \ \Omega.$$




4. What should be the power of the resistor R_1 so that it is not damaged during operation in the circuit shown in the figure.

$$\underline{U} = 10 \text{ V}, R_1 = 10 \ \Omega, X_{L1} = 25 \ \Omega,$$

$$X_{L2} = 40 \ \Omega, X_M = 10 \ \Omega, X_{C3} = 20 \ \Omega.$$

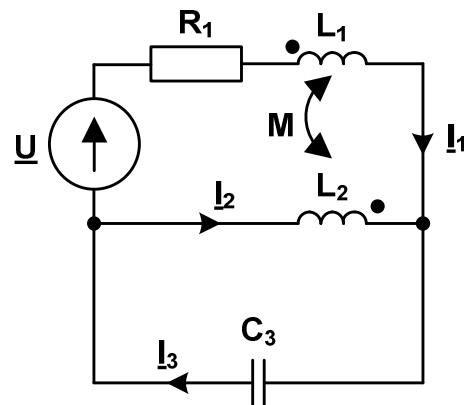Standard resistor power: 0.125 W, 0.25 W, 0.4 W, 0.5 W, 0.6 W, 0.75 W, 1 W, 1.2 W, 2 W, 3 W, 5 W, 7 W, 8 W, 9 W.



05.03.2024

Jarosław Forenc, PhD

j.forenc@pb.edu.pl