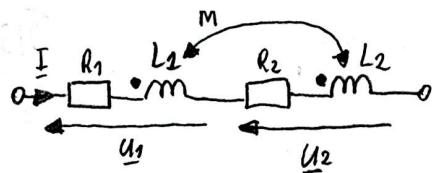


* INDUCTORS IN SERIES WITH MUTUAL COUPLING




$$\underline{U}_1 = R_1 \underline{I} + j\omega L_1 \underline{I} + j\omega M \underline{I}$$

$$\underline{U}_2 = R_2 \underline{I} + j\omega L_2 \underline{I} + j\omega M \underline{I}$$

$+j\omega M$ when current enters the dots in both inductors
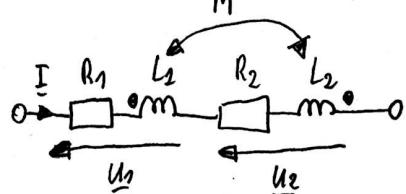
$$\underline{U} = \underline{U}_1 + \underline{U}_2 = (R_1 + R_2 + j\omega L_1 + j\omega L_2 + j2\omega M) \underline{I}$$




$$\underline{U}_1 = R_1 \underline{I} + j\omega L_1 \underline{I} - j\omega M \underline{I}$$

$$\underline{U}_2 = R_2 \underline{I} + j\omega L_2 \underline{I} - j\omega M \underline{I}$$

$-j\omega M$ when current enters a dot in one inductor and leaves a dot in other inductor


$$\underline{U} = \underline{U}_1 + \underline{U}_2 = (R_1 + R_2 + j\omega L_1 + j\omega L_2 - j2\omega M) \underline{I}$$

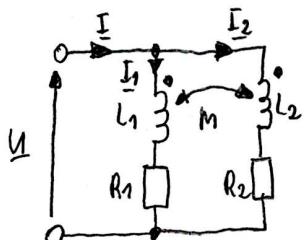* INDUCTORS IN PARALLEL WITH MUTUAL COUPLING



$$\left\{ \begin{array}{l} \underline{I} = \underline{I}_1 + \underline{I}_2 \\ \underline{U} = R_1 \underline{I}_1 + j\omega L_1 \underline{I}_1 + j\omega M \underline{I}_2 \\ \underline{U} = R_2 \underline{I}_2 + j\omega L_2 \underline{I}_2 + j\omega M \underline{I}_1 \end{array} \right.$$

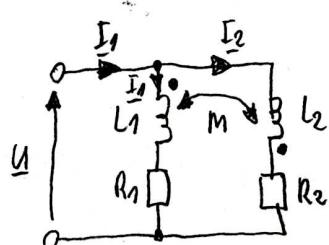$+j\omega M$ when both currents enter the dots





$$\left\{ \begin{array}{l} \underline{I} = \underline{I}_1 + \underline{I}_2 \\ \underline{U} = R_1 \underline{I}_1 + j\omega L_1 \underline{I}_1 - j\omega M \underline{I}_2 \\ \underline{U} = R_2 \underline{I}_2 + j\omega L_2 \underline{I}_2 - j\omega M \underline{I}_1 \end{array} \right.$$

$-j\omega M$ when one current enters a dot and the other current leaves a dot

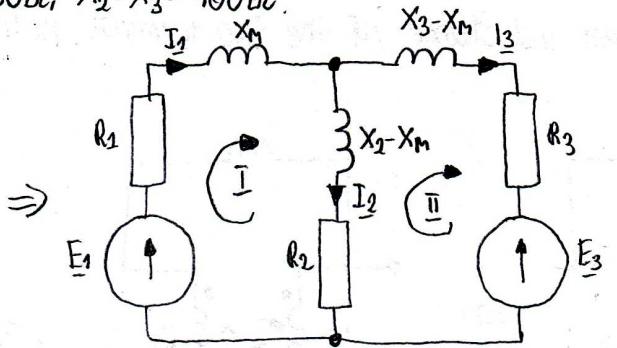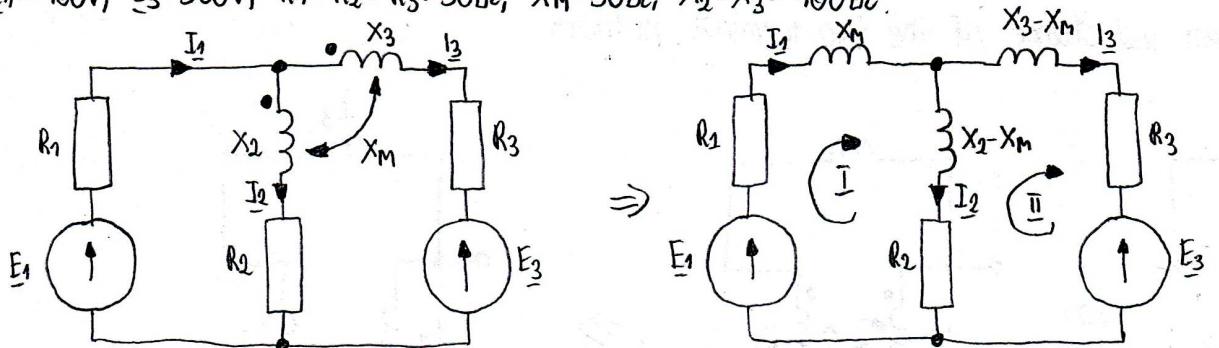PROBLEM #1

Calculate the currents in all branches of the circuit presented in the figure.

$$E_1 = 100V, E_3 = 500V, R_1 = R_2 = R_3 = 50\Omega, X_M = 50\Omega, X_2 = X_3 = 100\Omega$$



Method 1 (Elimination of coupling)

$$\begin{cases} \underline{I}_1 (R_1 + R_2 + jX_M + jX_2 - jX_M) - \underline{I}_{1\bar{1}} (R_2 + jX_2 - jX_M) = E_1 \\ -\underline{I}_1 (R_2 + jX_2 - jX_M) + \underline{I}_{\bar{1}\bar{1}} (R_2 + R_3 + jX_2 - jX_M + jX_3 - jX_M) = -E_3 \end{cases}$$

$$W = \begin{vmatrix} 2+j2 & -1-j1 \\ -1-j1 & 2+j2 \end{vmatrix} = j6$$

$$\begin{cases} \underline{I}_1 (50 + 50 + j100) - \underline{I}_{1\bar{1}} (50 + j100 - j50) = 100 \\ -\underline{I}_1 (50 + j100 - j50) + \underline{I}_{\bar{1}\bar{1}} (50 + 50 + j100 - j50 + j100 - j50) = -500 \end{cases}$$

$$W_I = \begin{vmatrix} 2 & -1-j1 \\ -10 & 2+j2 \end{vmatrix} = -6-j6$$

$$\underline{I}_1 (100 + j100) - \underline{I}_{1\bar{1}} (50 + j50) = 100 \quad | : 50$$

$$W_{\bar{1}\bar{1}} = \begin{vmatrix} 2+j2 & 2 \\ -1-j1 & -10 \end{vmatrix} = -18-j18$$

$$-\underline{I}_1 (50 + j50) + \underline{I}_{\bar{1}\bar{1}} (100 + j100) = -500 \quad | : 50$$

$$\begin{cases} \underline{I}_1 (2+j2) - \underline{I}_{1\bar{1}} (1+j1) = 2 \\ -\underline{I}_1 (1+j1) + \underline{I}_{\bar{1}\bar{1}} (2+j2) = -10 \end{cases}$$

$$\underline{I}_{1\bar{1}} = \frac{W_I}{W} = \frac{-6-j6}{j6} = (-1+j1) A$$


$$\underline{I}_1 = \underline{I}_{1\bar{1}} = \boxed{(-1+j1) A}$$

$$\underline{I}_{\bar{1}\bar{1}} = \frac{W_{\bar{1}\bar{1}}}{W} = \frac{-18-j18}{j6} = (-3+j3) A$$

$$\underline{I}_2 = \underline{I}_1 - \underline{I}_{1\bar{1}} = -1+j1 + 3-j3 = \boxed{(2-j2) A}$$

$$\underline{I}_3 = \underline{I}_{\bar{1}\bar{1}} = \boxed{(-3+j3) A}$$

Method 2 (KCL + KVL)

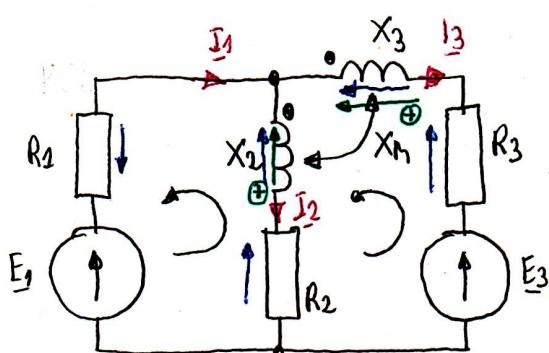

$$\text{KCL: } \underline{I}_1 - \underline{I}_2 - \underline{I}_3 = 0$$

$$\text{KVL: } R_1 \underline{I}_1 + jX_2 \underline{I}_2 + R_2 \underline{I}_2 + jX_M \underline{I}_3 - E_1 = 0$$


$$\text{KVL: } -R_2 \underline{I}_2 - jX_2 \underline{I}_2 + jX_3 \underline{I}_3 + R_3 \underline{I}_3 - jX_M \underline{I}_3 + jX_M \underline{I}_2 + E_3 = 0$$

PROBLEM #2

What should be the power of the Resistor R_1 so that it is not damaged during operation in the circuit shown in the figure.

$$U = 10V, R_1 = 10\Omega, X_L = 25\Omega, X_M = 40\Omega, X_C = 10\Omega, X_C = 20\Omega.$$

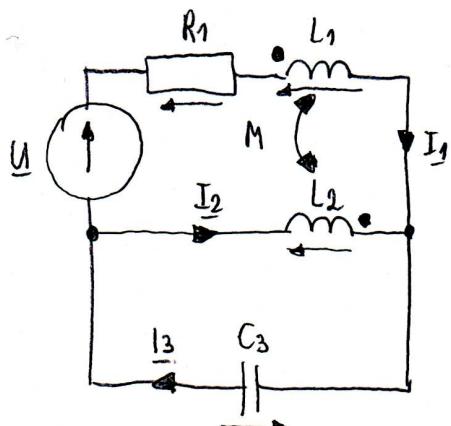Standard resistor power: 0.125W, 0.25W, 0.4W, 0.5W, 0.6W, 0.75W, 1W, 1.2W, 2W, 3W, 5W, 7W, 8W, 9W.



$$\left\{ \begin{array}{l} \underline{I}_1 + \underline{I}_2 = \underline{I}_3 \quad (1) \\ \underline{U} = R_1 \underline{I}_1 + jX_{L_1} \underline{I}_1 - jX_M \underline{I}_2 - jX_{L_2} \underline{I}_2 - (-jX_M \underline{I}_3) \quad (2) \\ 0 = jX_{L_2} \underline{I}_2 - jX_M \underline{I}_1 + (-jX_C \underline{I}_3) \quad (3) \end{array} \right.$$

← KCL
← KVL
← KVL

① $-jX_M$ when one current enters a dot and the other leaves a dot

$+jX_M$ when both currents enter the dot
(or both leave the dots)

$$10\underline{I}_1 + j25\underline{I}_1 - j10\underline{I}_2 - j40\underline{I}_2 + j10\underline{I}_3 = 10$$

$$(10+j35)\underline{I}_1 - j50\underline{I}_2 = 10$$

$$j40\underline{I}_2 - j10\underline{I}_1 - j20\underline{I}_3 = 0$$

$$\uparrow \underline{I}_3 = \underline{I}_1 + \underline{I}_2$$

$$j40\underline{I}_2 - j10\underline{I}_1 - j20\underline{I}_1 - j20\underline{I}_2 = 0$$

$$-j30\underline{I}_1 + j20\underline{I}_2 = 0$$

$$j20\underline{I}_2 = j30\underline{I}_1 \quad / : j20$$

$$\underline{I}_2 = \frac{3}{2}\underline{I}_1$$

$$(10+j35)\underline{I}_1 - j50 \cdot \frac{3}{2}\underline{I}_1 = 10$$

$$10+j35\underline{I}_1 - j75\underline{I}_1 = 10$$

$$(10-j40)\underline{I}_1 = 10$$

$$\underline{I}_1 = \frac{10}{10-j40} = (0.0588 + j0.2353)A$$

$$\underline{U}_1 = R_1 \underline{I}_1 = 10(0.0588 + j0.2353) =$$

$$= (0.588 + j2.353)V$$


$$\underline{S}_1 = \underline{U}_1 \cdot \underline{I}_1^* = (0.588 + j2.353)(0.0588 - j0.2353) = \\ = 0.5878 VA$$

$$P_1 = \operatorname{Re} \{ \underline{S}_1 \} = [0.5878 W]$$

The power of resistor R_1 should be $[0.6W]$.

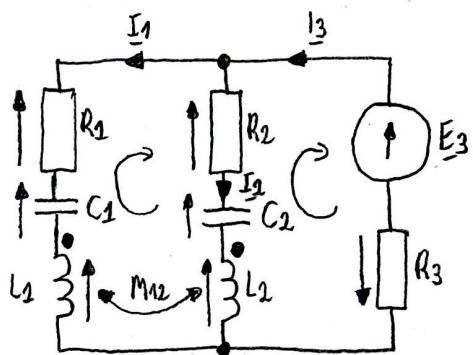PROBLEM #3 (this problem was not solved during the class)

Write equations according to KCL and KVL for the circuit presented in the figure.



$$\text{KCL} \rightarrow \underline{I_1} + \underline{I_2} = \underline{I_3}$$



$$\text{KVL} \rightarrow \begin{cases} R_1 \underline{I_1} - jX_{C1} \cdot \underline{I_1} + jX_{L1} \cdot \underline{I_1} - R_2 \underline{I_2} + jX_{C2} \cdot \underline{I_2} - jX_{L2} \cdot \underline{I_2}, \\ + jX_{M12} \cdot \underline{I_2}, - jX_{M12} \cdot \underline{I_1} = 0 \end{cases}$$

$$\text{KVL} \rightarrow R_2 \underline{I_2} - jX_{C2} \cdot \underline{I_2} + jX_{L2} \cdot \underline{I_2} + R_3 \cdot \underline{I_3} + jX_{M12} \cdot \underline{I_1} - E_3 = 0$$

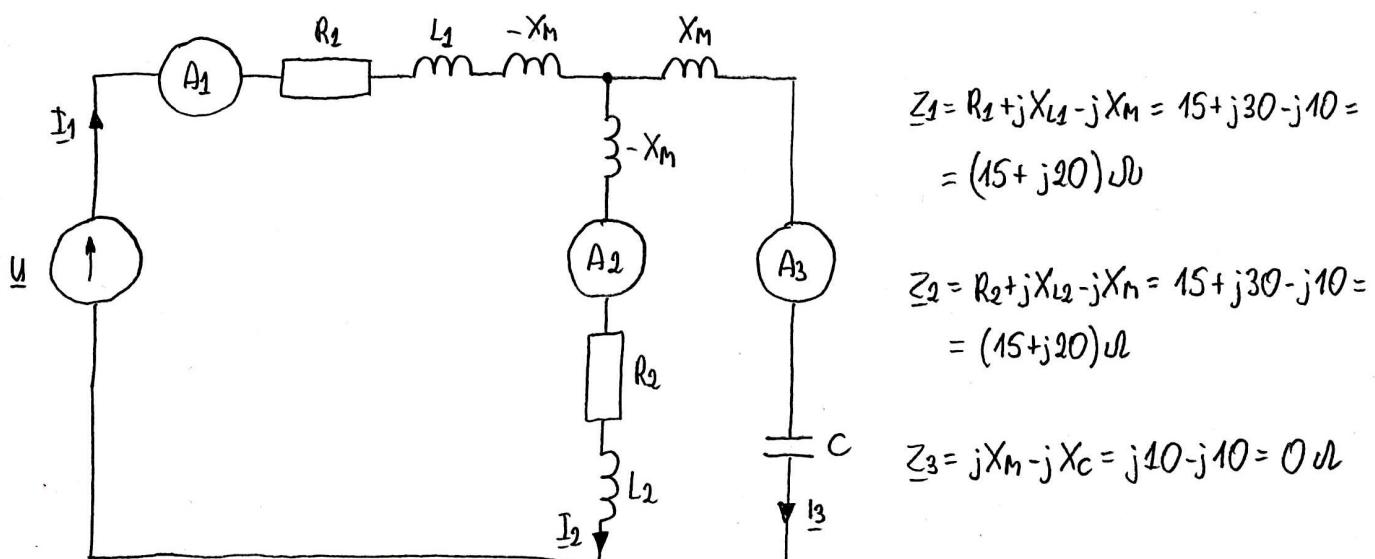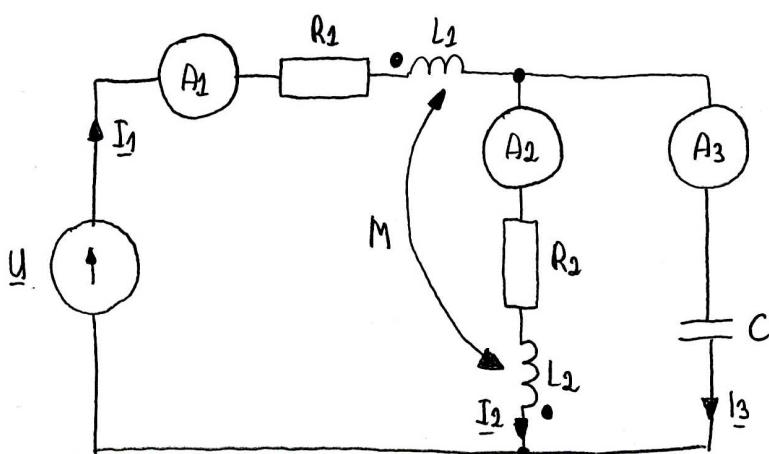PROBLEM #4 (this problem was not solved during the class)

Calculate meter readings in the circuit shown in the figure.

$$U = 100V, R_1 = R_2 = 15\Omega, X_{L1} = X_{L2} = 30\Omega, X_M = X_C = 10\Omega.$$



because $Z_3 = 0 \Omega$ then $I_{A2} = 0 A$ and $\underline{I_1} = \underline{I_3}$, $I_{A1} = I_{A3}$ $Z_{eq} = Z_1 = (15 + j20) \Omega$

$$I_1 = \frac{U}{Z_{eq}} = \frac{100}{15 + j20} = (2.4 - j3.2) A = 4 e^{-j53.1^\circ} A \Rightarrow I_{A1} = I_{A3} = |I_1| = 4 A$$