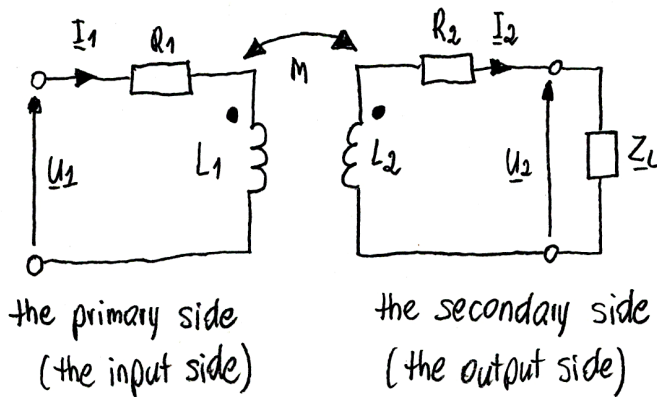


ELECTRICAL CIRCUITS 2 - CLASS NO. 4 (19.03.2024)

AIR-CORE TRANSFORMER

* circuit diagram



\underline{U}_1 - primary voltage

\underline{I}_1 - primary current

\underline{U}_2 - secondary voltage

\underline{I}_2 - secondary current

\underline{Z}_L - load impedance

* equations

$$\begin{cases} R_1 \underline{I}_1 + j\omega L_1 \underline{I}_1 - j\omega M \underline{I}_2 = \underline{U}_1 \\ R_2 \underline{I}_2 + j\omega L_2 \underline{I}_2 - j\omega M \underline{I}_1 + \underline{Z}_L \underline{I}_2 = 0 \end{cases}$$

* equations (open-circuited output), $\underline{Z}_L \rightarrow \infty$, $\underline{I}_2 = 0$


$$\begin{cases} R_1 \underline{I}_1 + j\omega L_1 \underline{I}_1 = \underline{U}_1 \\ -j\omega M \underline{I}_1 = \underline{U}_2 \end{cases}$$

* equations (short-circuited output), $\underline{Z}_L = 0$, $\underline{U}_2 = 0$

$$\begin{cases} R_1 \underline{I}_1 + j\omega L_1 \underline{I}_1 - j\omega M \underline{I}_2 = \underline{U}_1 \\ R_2 \underline{I}_2 + j\omega L_2 \underline{I}_2 - j\omega M \underline{I}_1 = 0 \end{cases}$$

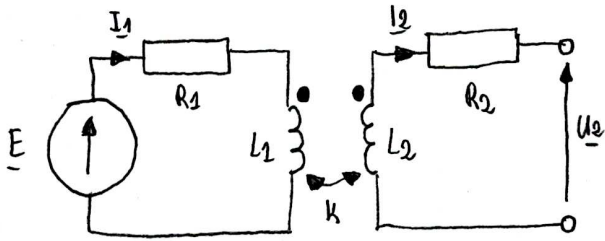PROBLEM #1

The air transformer was connected to the voltage source E . Calculate the readings of:
 a) ammeter, b) voltmeter, connected to the terminals of the secondary winding.
 $E = 200V$, $k = 0.8$, $R_1 = R_2 = 20\Omega$, $X_{L1} = X_{L2} = 40\Omega$.



$$M = k\sqrt{L_1 \cdot L_2} \quad X_M = k\sqrt{X_{L1} \cdot X_{L2}} = 0.8\sqrt{40^2} = 0.8 \cdot 40 = 32\Omega$$

$$I_1 = \frac{W_I}{W} = \frac{4000 + j8000}{-176 + j1600} = (4.6685 - j30.135)A$$

$$I_2 = \frac{W_{II}}{W} = \frac{j6400}{-176 + j1600} = (3.9522 - j0.4347)A$$

a) ammeter - short circuit in the secondary winding


$$\begin{cases} R_1 I_1 + jX_{L1} I_1 - jX_M I_2 = E \\ -jX_M I_1 + R_2 I_2 + jX_{L2} I_2 = 0 \end{cases} \quad W = \begin{vmatrix} 20+j40 & -j32 \\ -j32 & 20+j40 \end{vmatrix} = -176 + j1600$$

$$\begin{cases} 20I_1 + j40I_1 - j32I_2 = 200 \\ -j32I_1 + 20I_2 + j40I_2 = 0 \end{cases} \quad W_I = \begin{vmatrix} 200 & -j32 \\ 0 & 20+j40 \end{vmatrix} = 4000 + j8000$$

$$\begin{cases} (20+j40)I_1 - j32I_2 = 200 \\ -j32I_1 + (20+j40)I_2 = 0 \end{cases} \quad W_{II} = \begin{vmatrix} 20+j40 & 200 \\ -j32 & 0 \end{vmatrix} = 0 + j6400$$

$$|I_2| = 3.976A$$

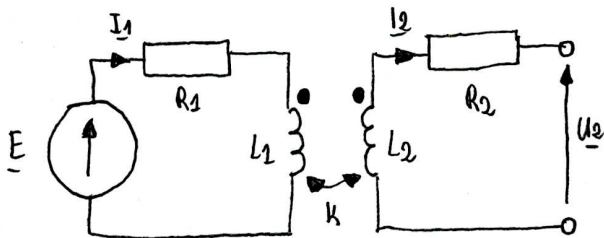b) voltmeter - open circuit in the secondary windings, $I_2 = 0A$



$$R_1 I_1 + jX_{L1} I_1 = E$$


$$(R_1 + jX_{L1}) I_1 = E \rightarrow I_1 = \frac{E}{R_1 + jX_{L1}} = \frac{200}{20 + j40} = (2 - 4j)A$$

$$U_2 = -jX_M I_1 = j32(2 - 4j) = (128 + j64)V$$

$$|U_2| = 143.1084V$$

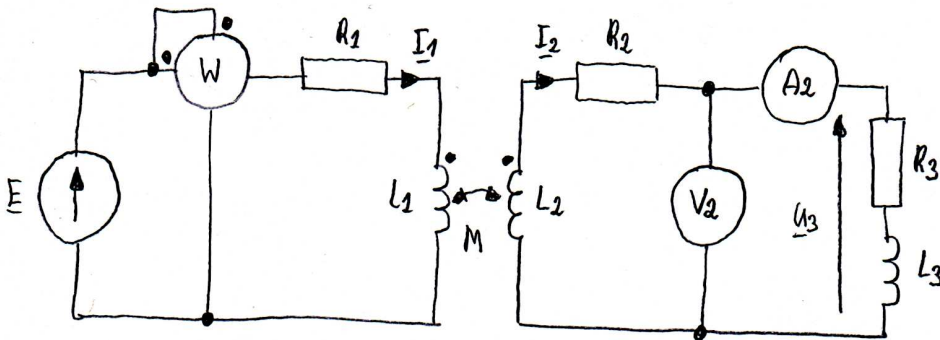PROBLEM #2

For the circuit below determine the results of measurements.
 $E = 230V$, $R_1 = X_{L2} = X_M = 10\Omega$, $R_2 = 5\Omega$, $R_3 = X_{L1} = X_{L3} = 20\Omega$.



$$\begin{cases} R_1 \underline{I}_1 + jX_{L1} \underline{I}_2 - jX_M \underline{I}_2 = \underline{E} \\ R_2 \underline{I}_2 + jX_{L2} \underline{I}_2 - jX_M \underline{I}_1 + R_3 \underline{I}_2 + jX_{L3} \underline{I}_2 = 0 \end{cases}$$

$$W = \begin{vmatrix} 10+j20 & -j10 \\ -j10 & 25+j30 \end{vmatrix} = -250 + j800$$

$$\begin{cases} 10\underline{I}_1 + j20\underline{I}_1 - j10\underline{I}_2 = 230 \\ 5\underline{I}_2 + j10\underline{I}_2 - j10\underline{I}_1 + 20\underline{I}_2 + j20\underline{I}_2 = 0 \end{cases}$$

$$W_1 = \begin{vmatrix} 230 & -j10 \\ 0 & 25+j30 \end{vmatrix} = 5750 + j6800$$

$$\begin{cases} (10+j20)\underline{I}_1 + (-j10)\underline{I}_2 = 230 \\ (-j10)\underline{I}_1 + (25+j30)\underline{I}_2 = 0 \end{cases}$$

$$W_2 = \begin{vmatrix} 10+j20 & 230 \\ -j10 & 0 \end{vmatrix} = j2300$$

$$\underline{I}_1 = \frac{W_1}{W} = \frac{5750 + j6800}{-250 + j800} = (5.81 - j9.00) A$$

$$\underline{I}_2 = \frac{W_2}{W} = \frac{j2300}{-250 + j800} = (2.62 - j0.82) A$$

$$P_W = \operatorname{Re}[\underline{E} \cdot \underline{I}_1^*] = \operatorname{Re}[230 \cdot (5.81 - j9.00)] = \operatorname{Re}[1336.3 - j2070] = \boxed{1336.3 \text{ W}}$$

$$I_{A2} = |\underline{I}_2| = \sqrt{2.62^2 + 0.82^2} = \boxed{2.75 \text{ A}}$$

$$U_{V2} = |\underline{U}_3| = |(R_3 + jX_{L3}) \cdot \underline{I}_2| = |(20 + j20) \cdot (2.62 - j0.82)| = |68.8 + j36| = \boxed{77.65 \text{ V}}$$