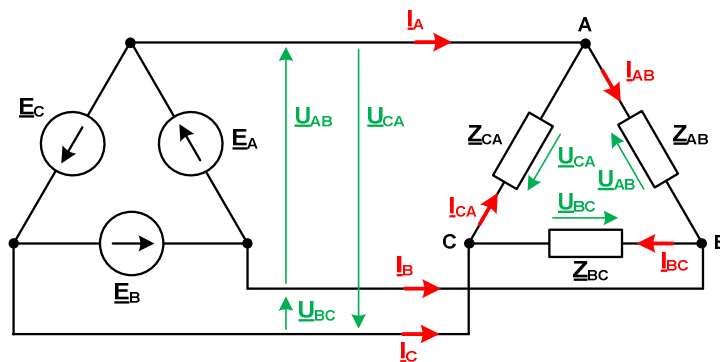


# ELECTRICAL CIRCUITS 2 - CLASS 7 (23.04.2024)

## Balanced Delta-Delta ( $\Delta$ - $\Delta$ ) connection



- Symbols in the circuit:

$\underline{E}_A, \underline{E}_B, \underline{E}_C$  - phase voltages of the generator

$\underline{I}_A, \underline{I}_B, \underline{I}_C$  - the line currents

$\underline{U}_{AB}, \underline{U}_{BC}, \underline{U}_{CA}$  - phase voltages of the load

$\underline{I}_{AB}, \underline{I}_{BC}, \underline{I}_{CA}$  - the phase currents

$\underline{Z}_{AB}, \underline{Z}_{BC}, \underline{Z}_{CA}$  - the load impedances

- Balanced load:

$$\underline{Z}_A = \underline{Z}_B = \underline{Z}_C = \underline{Z}$$

- Phase voltages of the load are equal to phase voltages of the generator:

$$\underline{U}_{AB} = \underline{E}_A, \quad \underline{U}_{BC} = \underline{E}_B, \quad \underline{U}_{CA} = \underline{E}_C$$

the complex values (phasors):  $\underline{U}_{AB} + \underline{U}_{BC} + \underline{U}_{CA} = 0$

the rms (effective) values:  $U_{AB} = U_{BC} = U_{CA}$

- The phase currents:

$$\underline{I}_{AB} = \frac{\underline{U}_{AB}}{\underline{Z}_{AB}}, \quad \underline{I}_{BC} = \frac{\underline{U}_{BC}}{\underline{Z}_{BC}}, \quad \underline{I}_{CA} = \frac{\underline{U}_{CA}}{\underline{Z}_{CA}}$$

the complex values (phasors):  $\underline{I}_{AB} + \underline{I}_{BC} + \underline{I}_{CA} = 0$

the rms (effective) values:  $I_{AB} = I_{BC} = I_{CA}$

- The line currents:

$$\underline{I}_A = \underline{I}_{AB} - \underline{I}_{CA}$$


$$\underline{I}_B = \underline{I}_{BC} - \underline{I}_{AB}$$

$$\underline{I}_C = \underline{I}_{CA} - \underline{I}_{BC}$$

the complex values (phasors):  $\underline{I}_A + \underline{I}_B + \underline{I}_C = 0$

the rms (effective) values:  $I_A = I_B = I_C$

- Phasor diagram of currents:

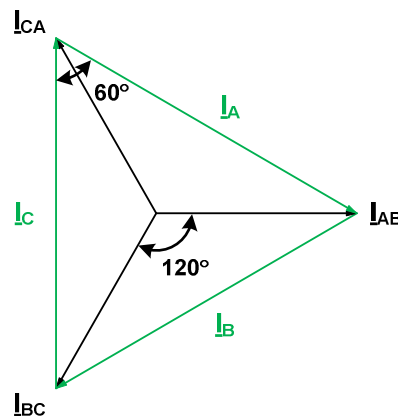

- Active, reactive and apparent power:

$$P = U_{AB} \cdot I_{AB} \cdot \cos \varphi_{AB} + U_{BC} \cdot I_{BC} \cdot \cos \varphi_{BC} + U_{CA} \cdot I_{CA} \cdot \cos \varphi_{CA}$$

$$Q = U_{AB} \cdot I_{AB} \cdot \sin \varphi_{AB} + U_{BC} \cdot I_{BC} \cdot \sin \varphi_{BC} + U_{CA} \cdot I_{CA} \cdot \sin \varphi_{CA}$$

$$S = U_{AB} \cdot I_{AB} + U_{BC} \cdot I_{BC} + U_{CA} \cdot I_{CA}$$

Complex power:

$$\underline{S} = \underline{U}_{AB} \cdot \underline{I}_{AB}^* + \underline{U}_{BC} \cdot \underline{I}_{BC}^* + \underline{U}_{CA} \cdot \underline{I}_{CA}^*$$

$$\underline{S} = P + jQ$$

$$P = \operatorname{Re}\{\underline{S}\}, \quad Q = \operatorname{Im}\{\underline{S}\}, \quad S = \|\underline{S}\|$$

in the case of balanced load:

$$U_{AB} = U_{BC} = U_{CA} = U_{ph}, \quad I_{AB} = I_{BC} = I_{CA} = I_{ph}, \quad \cos \varphi_{AB} = \cos \varphi_{BC} = \cos \varphi_{CA} = \cos \varphi_{ph}$$


then:

$$P = 3 \cdot U_{ph} \cdot I_{ph} \cdot \cos \varphi_{ph}, \quad Q = 3 \cdot U_{ph} \cdot I_{ph} \cdot \sin \varphi_{ph}, \quad S = 3 \cdot U_{ph} \cdot I_{ph}$$

**ELECTRICAL CIRCUITS 2 - CLASS NO. 7 (23.04.2024)**

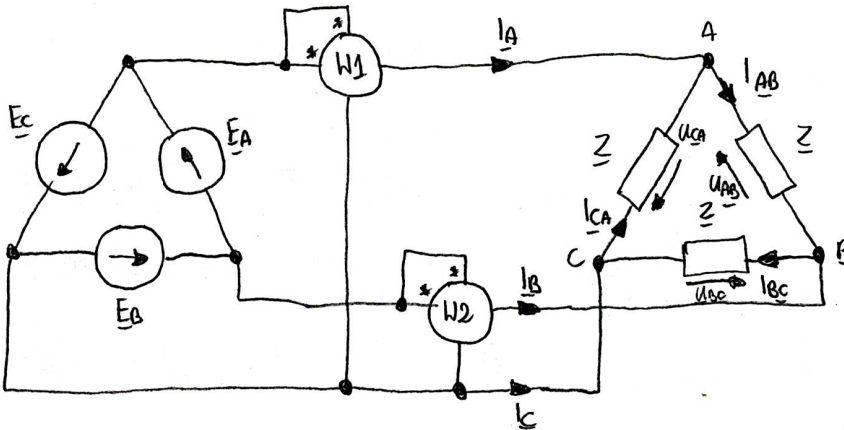**PROBLEM #1**

In a 3-phase balanced  $\Delta$ - $\Delta$  system the source voltage  $E_{ph} = 230\text{ V rms}$ . The impedance per phase is  $Z = (8+j6)\Omega$ . Find the line currents, active power of the load and wattmeters readings.



$$\underline{E}_A = 230e^{j0^\circ} \text{ V} = 230 \text{ V}$$

$$\underline{E}_B = 230e^{j120^\circ} \text{ V} = -115 - j199.19 \text{ V}$$

$$\underline{E}_C = 230e^{j240^\circ} \text{ V} = -115 + j199.19 \text{ V}$$

$$\underline{U}_{AB} = \underline{E}_A$$

$$\underline{U}_{BC} = \underline{E}_B$$

$$\underline{U}_{CA} = \underline{E}_C$$

Note: for  $\underline{I}_B$  current, the calculated angle is positive. After changing the angle to negative ( $173.13^\circ - 360^\circ = -186.87^\circ$ ), we can see that the angle between the phase and line current is  $30^\circ$ .

$$\underline{I}_{AB} = \frac{\underline{E}_A}{Z} = \frac{230}{8+j6} = (18.4 - j13.8) \text{ A} = 23e^{-j36.87^\circ} \text{ A}$$

$$\underline{I}_{BC} = \frac{\underline{E}_B}{Z} = \frac{-115 - j199.19}{8+j6} = (-21.15 - j9.03) \text{ A} = 23e^{-j156.87^\circ} \text{ A}$$

$$\underline{I}_{CA} = \frac{\underline{E}_C}{Z} = \frac{-115 + j199.19}{8+j6} = (2.75 + j22.83) \text{ A} = 23e^{j83.13^\circ} \text{ A}$$

$$\underline{I}_A = \underline{I}_{AB} - \underline{I}_{CA} = 18.4 - j13.8 - 2.75 - j22.83 = (15.65 - j36.63) \text{ A} = 39.84e^{-j66.87^\circ} \text{ A}$$

$$\underline{I}_B = \underline{I}_{BC} - \underline{I}_{AB} = -21.15 - j9.03 - 18.4 + j13.8 = (-39.55 + j4.77) \text{ A} = 39.84e^{j173.13^\circ} \text{ A} = 39.84e^{-j186.87^\circ} \text{ A}$$

$$\underline{I}_C = \underline{I}_{CA} - \underline{I}_{BC} = 2.75 + j22.83 + 21.15 + j9.03 = (23.9 + j31.87) \text{ A} = 39.84e^{j53.13^\circ} \text{ A} = 39.84e^{-j306.87^\circ} \text{ A}$$

$$\underline{S}_1 = (-\underline{E}_C) \cdot \underline{I}_A^* = (115 - j199.19) \cdot (15.65 + j36.63) = \underbrace{(9096.76 + j1095.98)}_{P_{W1}} \text{ VA} \rightarrow P_{W1} = 9096.76 \text{ W}$$

$$\underline{S}_2 = \underline{E}_B \cdot \underline{I}_B^* = (-115 - j199.19) \cdot (-39.55 - j4.77) = \underbrace{(3599.23 + j8426.02)}_{P_{W2}} \text{ VA} \rightarrow P_{W2} = 3599.23 \text{ W}$$

$$\underline{S} = \underline{E}_A \cdot \underline{I}_{AB}^* + \underline{E}_B \cdot \underline{I}_{BC}^* + \underline{E}_C \cdot \underline{I}_{CA}^* = 230 \cdot (18.4 - j13.8) + (-115 - j199.19) \cdot (-21.15 - j9.03) + (-115 + j199.19) \cdot (2.75 + j22.83)$$


$$P_{\text{load}} = P_{W1} + P_{W2} = 4232 + j3174 + 4232 + j3174 + 4232 + j3174 = \underbrace{(12696 + j9522)}_{P_{\text{load}}} \text{ VA}$$

$$P_{\text{load}} = \boxed{12696 \text{ W}} \quad P_{W1} + P_{W2} = 9096.76 + 3599.23 = \boxed{12695.99 \text{ W}}$$

## PROBLEM #2

The three-phase electric heater consists of three heating coils Y-connected. The nominal power of the heater is  $P_n = 3 \text{ kW}$ , and the nominal voltage  $U_n = 230 \text{ V rms}$ . The heater has been damaged. After its repair the length of the first coil decreased by 5% and the length of the second coil by 10%.

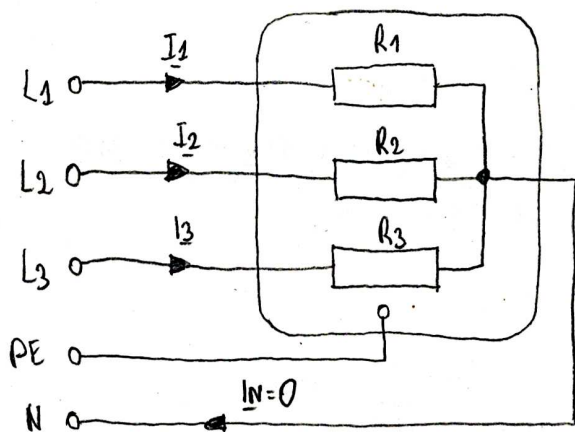a) calculate the line currents before repairing the heater,



$$P = \frac{P_n}{3} = \frac{3000}{3} = 1000 \text{ W}$$

$$R_1 = R_2 = R_3 = R \quad R = \frac{U_n^2}{P} = \frac{230^2}{1000} = 52.8 \text{ } \Omega$$

$$\underline{E}_1 = 230 e^{j0^\circ} = 230 \text{ V}$$

$$\underline{E}_2 = 230 e^{-j120^\circ} = (-115 - j119.18) \text{ V}$$

$$\underline{E}_3 = 230 e^{+j120^\circ} = (-115 + j119.18) \text{ V}$$

$$\underline{I}_1 = \frac{\underline{E}_1}{R} = \frac{230}{52.8} = 4.3478 = 4.3478 e^{j0^\circ} \text{ A}$$


$$\underline{I}_1 + \underline{I}_2 + \underline{I}_3 = 0$$

$$\underline{I}_2 = \frac{\underline{E}_2}{R} = \frac{-115 - j119.18}{52.8} = (-2.1739 - j3.7653) = 4.3478 e^{-j120^\circ} \text{ A}$$

$$\underline{I}_1 = \underline{I}_2 = \underline{I}_3$$

$$\underline{I}_3 = \frac{\underline{E}_3}{R} = \frac{-115 + j119.18}{52.8} = (-2.1739 + j3.7653) = 4.3478 e^{+j120^\circ} \text{ A}$$

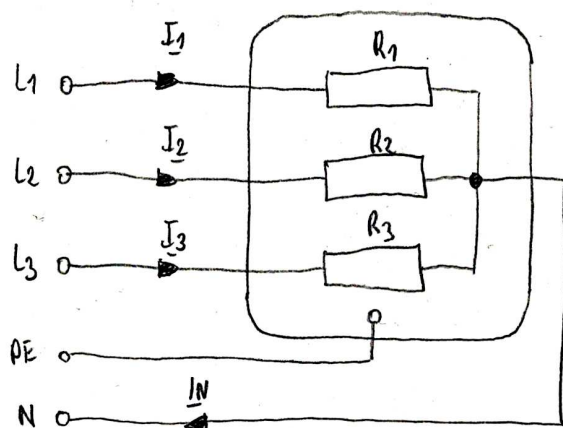b) calculate line currents, the current in the neutral line and the power of the repaired heater



$$R_1 = 0.95 R = 0.95 \cdot 52.8 = 50.256 \text{ } \Omega$$

$$R_2 = 0.9 R = 0.9 \cdot 52.8 = 47.616 \text{ } \Omega$$

$$R_3 = R = 52.8 \text{ } \Omega$$

$$\underline{I}_1 = \frac{\underline{E}_1}{R_1}$$

$$\underline{I}_2 = \frac{\underline{E}_2}{R_2}$$

$$\underline{I}_3 = \frac{\underline{E}_3}{R_3}$$

$$\underline{I}_N = \underline{I}_1 + \underline{I}_2 + \underline{I}_3$$

$$P_n = \frac{U_n^2}{R_1} + \frac{U_n^2}{R_2} + \frac{U_n^2}{R_3}$$

$$P_n = \operatorname{Re} \{ \underline{S} \} = \operatorname{Re} \{ \underline{E}_1 \cdot \underline{I}_1^* + \underline{E}_2 \cdot \underline{I}_2^* + \underline{E}_3 \cdot \underline{I}_3^* \}$$