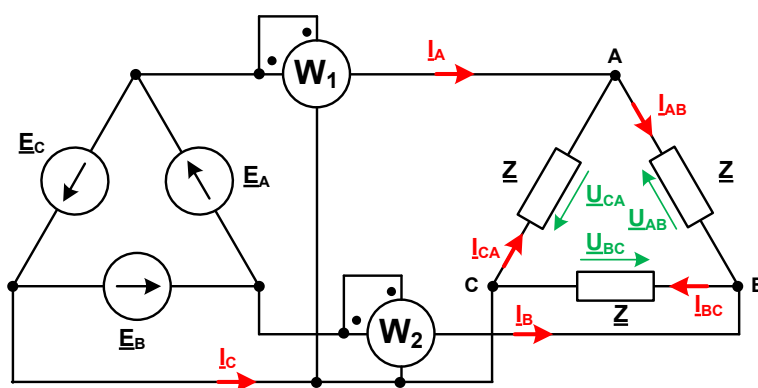


Module name: **Electrical Circuits 2**
 Module ID: **IS-FEE-10085S**
 Module type: **Class**
 Semester: **summer 2023/2024**
 Instructor: **Jarosław Forenc, j.forenc@pb.edu.pl**


Class 7 (23.04.2024)

1. In a 3-phase balanced Δ - Δ system, the source voltage is $E_{ph} = 230 \text{ V rms}$. The impedance per phase $\underline{Z} = (8+j6) \Omega$. Find the line currents, active power of the load and wattmeters readings.



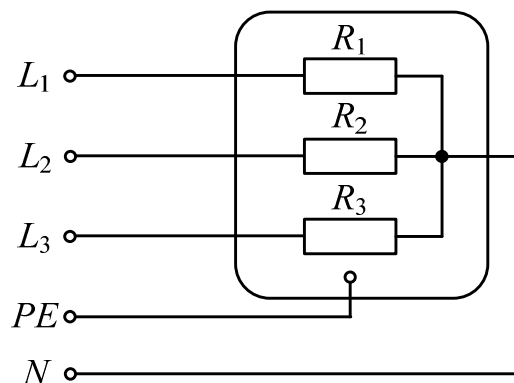2. The three-phase electric heater consists of three heating coils Y-connected (Fig). The nominal power of the heater is $P_n = 3 \text{ kW}$, and the nominal voltage $U_n = 230 \text{ V rms}$. The heater has been damaged. After its repair the length of the first coil decreased by 5% and the length of the second coil by 10%.

- calculate line currents before repairing the heater,
- calculate line currents, the current in the neutral line and the power of the repaired heater,
- calculate line currents and the power of the repaired heater, when the neutral line is not connected.



23.04.2024

Jarosław Forenc, PhD

j.forenc@pb.edu.pl