

Unbalanced Wye-Wye (Y-Y) connection

- Generator voltages (positive phase sequence)

$$e_A(t) = E_m \sin(\omega t)$$

$$\underline{E}_A = E e^{j0^\circ}$$

E_m - the peak (maximum) value

$$e_B(t) = E_m \sin(\omega t - 120^\circ)$$


$$\underline{E}_B = E e^{-j120^\circ}$$

\underline{E} - the complex value (phasor)

$$e_C(t) = E_m \sin(\omega t + 120^\circ)$$

$$\underline{E}_C = E e^{j120^\circ}$$

E - the rms (effective) value

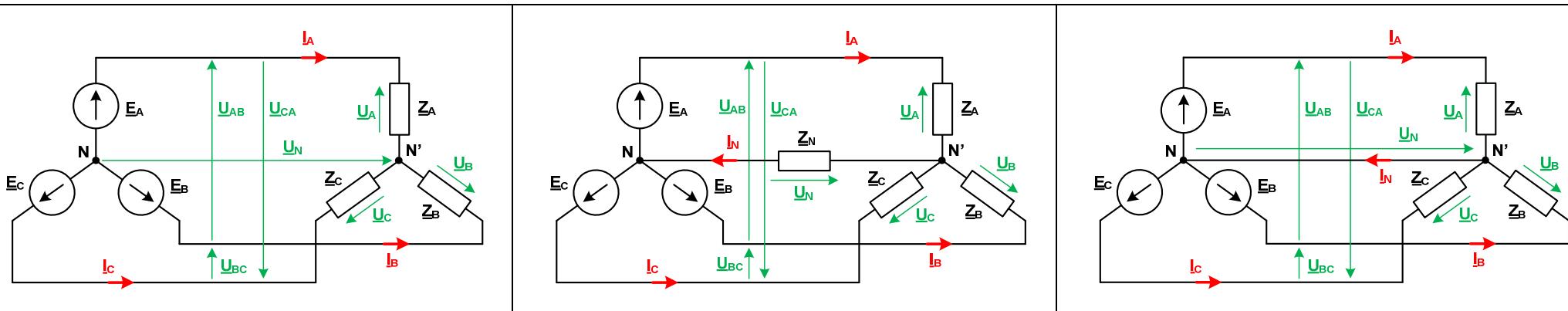

- Unbalanced load:

$$\underline{Z}_A \neq \underline{Z}_B \neq \underline{Z}_C$$

- U_N voltage:

$$\underline{U}_N = \frac{\underline{E}_A \cdot \underline{Y}_A + \underline{E}_B \cdot \underline{Y}_B + \underline{E}_C \cdot \underline{Y}_C}{\underline{Y}_A + \underline{Y}_B + \underline{Y}_C} \neq 0$$

where:

$$\underline{Y}_A = \frac{1}{\underline{Z}_A}, \quad \underline{Y}_B = \frac{1}{\underline{Z}_B}, \quad \underline{Y}_C = \frac{1}{\underline{Z}_C}$$

- U_N voltage:

$$\underline{U}_N = \frac{\underline{E}_A \cdot \underline{Y}_A + \underline{E}_B \cdot \underline{Y}_B + \underline{E}_C \cdot \underline{Y}_C}{\underline{Y}_A + \underline{Y}_B + \underline{Y}_C + \underline{Y}_N} \neq 0$$

where:

$$\underline{Y}_A = \frac{1}{\underline{Z}_A}, \quad \underline{Y}_B = \frac{1}{\underline{Z}_B}, \quad \underline{Y}_C = \frac{1}{\underline{Z}_C}, \quad \underline{Y}_N = \frac{1}{\underline{Z}_N}$$

- Phase voltages of the load:

$$\underline{U}_A = \underline{E}_A - \underline{U}_N, \quad \underline{U}_B = \underline{E}_B - \underline{U}_N, \quad \underline{U}_C = \underline{E}_C - \underline{U}_N$$

- U_N voltage:

$$\underline{U}_N = 0$$

- Phase voltages of the load:

$$\underline{U}_A = \underline{E}_A - \underline{U}_N, \quad \underline{U}_B = \underline{E}_B - \underline{U}_N, \quad \underline{U}_C = \underline{E}_C - \underline{U}_N$$

- Phase voltages of the load:

$$\underline{U}_A = \underline{E}_A, \quad \underline{U}_B = \underline{E}_B, \quad \underline{U}_C = \underline{E}_C$$

- The line currents:

$$\underline{I}_A = \frac{\underline{U}_A}{\underline{Z}_A}, \quad \underline{I}_B = \frac{\underline{U}_B}{\underline{Z}_B}, \quad \underline{I}_C = \frac{\underline{U}_C}{\underline{Z}_C}$$

$$\underline{I}_A + \underline{I}_B + \underline{I}_C = 0$$

- The line currents:

$$\underline{I}_A = \frac{\underline{U}_A}{\underline{Z}_A}, \quad \underline{I}_B = \frac{\underline{U}_B}{\underline{Z}_B}, \quad \underline{I}_C = \frac{\underline{U}_C}{\underline{Z}_C}$$

$$\underline{I}_A + \underline{I}_B + \underline{I}_C = \underline{I}_N, \quad \underline{I}_N = \frac{\underline{U}_N}{\underline{Z}_N}$$

- The line currents:

$$\underline{I}_A = \frac{\underline{U}_A}{\underline{Z}_A}, \quad \underline{I}_B = \frac{\underline{U}_B}{\underline{Z}_B}, \quad \underline{I}_C = \frac{\underline{U}_C}{\underline{Z}_C}$$

$$\underline{I}_A + \underline{I}_B + \underline{I}_C = \underline{I}_N$$

- The line voltages (line-to-line):

$$\underline{U}_{AB} = \underline{E}_A - \underline{E}_B = \sqrt{3}Ee^{j30^\circ}$$

$$\underline{U}_{BC} = \underline{E}_B - \underline{E}_C = \sqrt{3}Ee^{-j90^\circ}$$

$$\underline{U}_{CA} = \underline{E}_C - \underline{E}_A = \sqrt{3}Ee^{j150^\circ}$$

- Active, reactive and apparent power:

$$P = \underline{U}_A \cdot \underline{I}_A \cdot \cos \varphi_A + \underline{U}_B \cdot \underline{I}_B \cdot \cos \varphi_B + \underline{U}_C \cdot \underline{I}_C \cdot \cos \varphi_C$$

$$Q = \underline{U}_A \cdot \underline{I}_A \cdot \sin \varphi_A + \underline{U}_B \cdot \underline{I}_B \cdot \sin \varphi_B + \underline{U}_C \cdot \underline{I}_C \cdot \sin \varphi_C$$


$$S = \underline{U}_A \cdot \underline{I}_A + \underline{U}_B \cdot \underline{I}_B + \underline{U}_C \cdot \underline{I}_C$$

- Complex power:


$$\underline{S} = \underline{U}_A \cdot \underline{I}_A^* + \underline{U}_B \cdot \underline{I}_B^* + \underline{U}_C \cdot \underline{I}_C^*$$

$$\underline{S} = P + jQ, \quad P = \text{Re}\{\underline{S}\}, \quad Q = \text{Im}\{\underline{S}\}$$


- Phasor diagram of voltages:

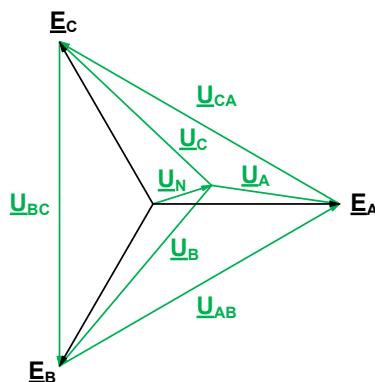

- Phasor diagram of voltages:

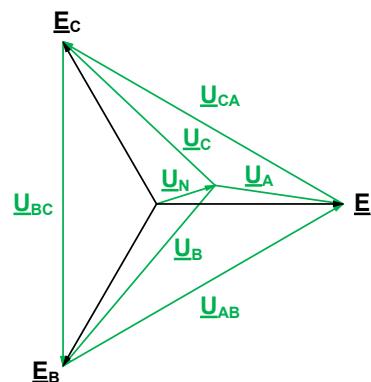

- Phasor diagram of voltages:

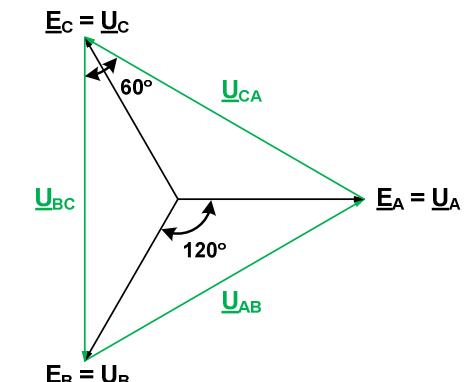

POWER IN AC CIRCUITS

* P - ACTIVE POWER (TRUE POWER, REAL POWER) unit: Watt [W]

$$P = U_{\text{rms}} \cdot I_{\text{rms}} \cdot \cos \varphi, \quad \text{where } \varphi = \psi_u - \psi_i \quad (\text{angle between voltage and current})$$

$$U_{\text{rms}} = \frac{U_m}{\sqrt{2}} \quad I_{\text{rms}} = \frac{I_m}{\sqrt{2}} \quad \rightarrow P = \frac{U_m \cdot I_m}{2} \cdot \cos \varphi \quad P = R \cdot I_{\text{rms}}^2 = \frac{U_{\text{rms}}^2}{R}$$

* Q - REACTIVE POWER unit: voltampere (reactive) [var]

$$Q = U_{\text{rms}} \cdot I_{\text{rms}} \cdot \sin \varphi \quad \varphi = \psi_u - \psi_i \quad (\text{angle between voltage and current})$$

$$Q = \frac{U_m \cdot I_m}{2} \sin \varphi \quad Q = X \cdot I_{\text{rms}}^2 = \frac{U_{\text{rms}}^2}{X}$$



* S - APPARENT POWER unit: voltampere [VA]

$$S = U_{\text{rms}} \cdot I_{\text{rms}} \quad S = I_{\text{rms}}^2 \cdot Z = \frac{U_{\text{rms}}^2}{Z}$$

* S - PHASOR POWER (COMPLEX POWER)

$$\underline{S} = \underline{U} \cdot \underline{I}^* \quad \underline{S} = P + jQ \quad P = \text{Re}[\underline{S}] \quad Q = \text{Im}[\underline{S}]$$

* THE POWER TRIANGLE

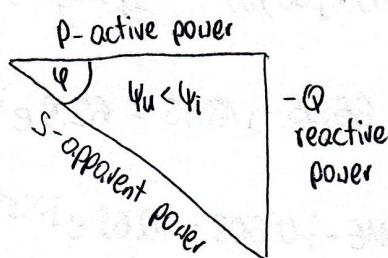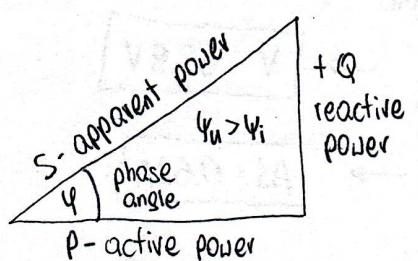


$$S = \sqrt{P^2 + Q^2}$$

* THE POWER FACTOR (pf)

$$(pf) = \frac{P}{S} = \cos \varphi$$

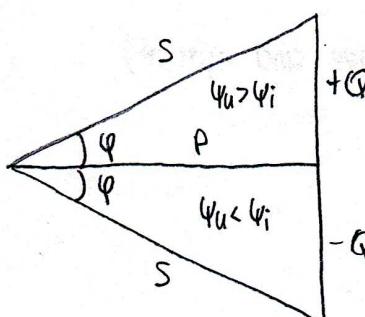* the ratio between the active power and the apparent power of a load is called the power factor of the load



lagging power factor

leading power factor

* inductive loads always have a lagging power factor


* capacitive loads always have a leading power factor

ELECTRICAL CIRCUITS 2 - CLASS NO. 8 (30.04.2024)

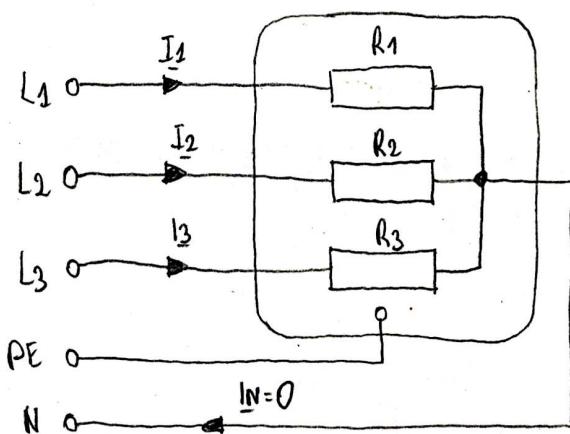PROBLEM #2, CLASS 7

The three-phase electric heater consists of three heating coils V-connected. The nominal power of the heater is $P_n = 3 \text{ kW}$, and the nominal voltage $U_n = 230 \text{ V}_{\text{rms}}$. The heater has been damaged. After its repair the length of the first coil decreased by 5% and the length of the second coil by 10%.

- calculate the line currents before repairing the heater,



$$\underline{I}_1 = \frac{\underline{E}_1}{R} = \frac{230}{52.8} = 4.3478 = 4.3478 e^{j0^\circ} \text{ A}$$


$$\underline{I}_2 = \frac{\underline{E}_2}{R} = \frac{-115-j118.18}{52.8} = (-2.1738-j3.7653) = 4.3478 e^{j120^\circ} \text{ A}$$

$$\underline{I}_3 = \frac{\underline{E}_3}{R} = \frac{-115+j118.18}{52.8} = (-2.1738+j3.7653) = 4.3478 e^{+j120^\circ} \text{ A}$$

$$\underline{I}_1 + \underline{I}_2 + \underline{I}_3 = 0$$

$$I_1 = I_2 = I_3$$

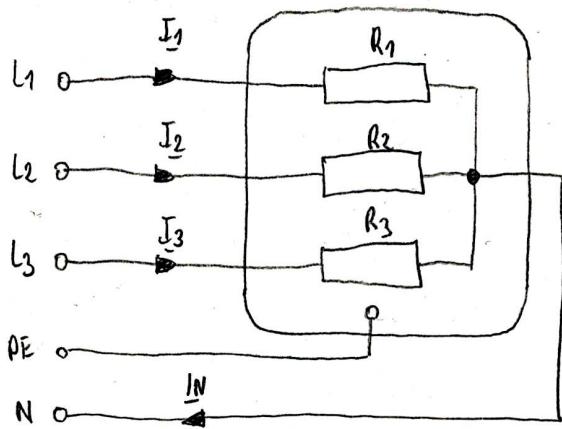- calculate line currents, the current in the neutral line and the power of the repaired heater



$$R_1 = 0.95 R = 0.95 \cdot 52.8 = 50.255 \Omega$$

$$R_2 = 0.8 R = 0.8 \cdot 52.8 = 49.61 \Omega$$

$$R_3 = R = 52.8 \Omega$$

$$\underline{I}_1 = \frac{\underline{E}_1}{R_1} = \frac{230}{50.255} = 4.5769 = 4.5769 e^{j0^\circ} \text{ A}$$

$$\underline{I}_2 = \frac{\underline{E}_2}{R_2} = \frac{(-115-j118.18)}{49.61} = (-2.4155-j4.1839) = 4.8308 e^{-j120^\circ} \text{ A}$$


$$\underline{I}_3 = \frac{\underline{E}_3}{R_3} = \frac{(-115+j118.18)}{52.8} = (-2.1738+j3.7653) = 4.3478 e^{+j120^\circ} \text{ A}$$

$$\underline{I}_N = \underline{I}_1 + \underline{I}_2 + \underline{I}_3 = 4.5769 - 2.4155 - j4.1839 - 2.1738 + j3.7653 = (-0.0127 - j0.4184) = 0.4186 e^{-j81.76^\circ} \text{ A}$$

$$P_n = \frac{U_n^2}{R_1} + \frac{U_n^2}{R_2} + \frac{U_n^2}{R_3} = \frac{230^2}{50.255} + \frac{230^2}{49.61} + \frac{230^2}{52.8} = 3163.7 \text{ W}$$

$$P_n = \operatorname{Re} \{ S \} = \operatorname{Re} \{ E_1 \underline{I}_1^* + E_2 \underline{I}_2^* + E_3 \underline{I}_3^* \} = \operatorname{Re} \{ 230 \cdot (4.5769) + (-115-j118.18)(-2.4155+j4.1839) + (-115+j118.18)(-2.1738-j3.7653) \} = 3163.7 \text{ W}$$

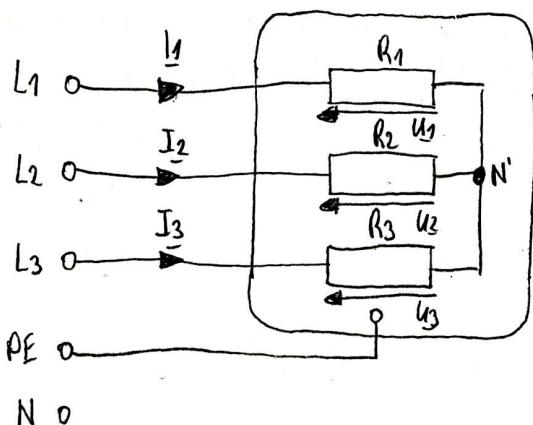c) calculate line currents and the power of the repaired heater, when the neutral line is not connected



$$Y_1 = \frac{1}{Z_1} = \frac{1}{R_1} = \frac{1}{50.255} = 0.0188 \Omega^{-1}$$

$$Y_2 = \frac{1}{Z_2} = \frac{1}{R_2} = \frac{1}{49.61} = 0.021 \Omega^{-1}$$

$$Y_3 = \frac{1}{Z_3} = \frac{1}{R_3} = \frac{1}{52.8} = 0.0188 \Omega^{-1}$$

N 0

$$U_{NN'} = \frac{E_1 \cdot Y_1 + E_2 \cdot Y_2 + E_3 \cdot Y_3}{Y_1 + Y_2 + Y_3} = \frac{230 \cdot 0.0188 + (-115 - j 188.18) \cdot 0.021 + (-115 + j 188.18) \cdot 0.0188}{0.0188 + 0.021 + 0.0188} = \\ = (-0.2126 - j 6.8854) V$$

$$\underline{I}_1 = \frac{\underline{U}_1}{R_1} = \frac{E_1 - U_{NN'}}{R_1} = \frac{230 + 0.2126 + j 6.8854}{50.255} = 4.5808 + j 0.1382 = 4.583 e^{+j 1.74^\circ} A$$

$$\underline{I}_2 = \frac{\underline{U}_2}{R_2} = \frac{E_2 - U_{NN'}}{R_2} = \frac{(-115 - j 188.18) + 0.2126 + j 6.8854}{49.61} = -2.411 - j 4.0368 = 4.902 e^{-j 190.85^\circ} A$$

$$\underline{I}_3 = \frac{\underline{U}_3}{R_3} = \frac{E_3 - U_{NN'}}{R_3} = \frac{(-115 + j 188.18) + 0.2126 + j 6.8854}{52.8} = -2.1688 + j 3.8976 = 4.4608 e^{+j 118.11^\circ} A$$


PROBLEM #1

In a 3-phase unbalanced Y-Y system, the source voltage is $E_{ph} = 230 \text{ V rms}$. The load impedances are: $\underline{Z}_A = (6+j8)\Omega$, $\underline{Z}_B = (8+j6)\Omega$, $\underline{Z}_C = 20\Omega$. What should be the rated current of the overcurrent circuit breakers protecting this circuit? Standard rated currents are: 6 A, 10 A, 16 A, 20 A, 25 A, 32 A, 40 A, 50 A, 63 A, 80 A, 125 A. What is the cost of active energy used by this load during one week (8 h per day, 5 days, 0.283 €/kWh)? Consider two cases:

a) without a neutral wire, b) with a neutral wire.

Draw phasor diagrams of currents and voltages for both cases.

a)

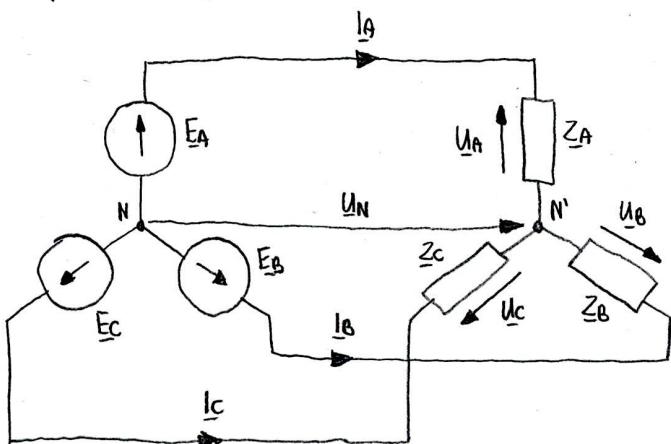

$$E_A = 230 e^{j 0^\circ} = 230 \text{ V}$$

$$E_B = 230 e^{-j 120^\circ} = (-115 - j 188.18) \text{ V}$$

$$E_C = 230 e^{+j 120^\circ} = (-115 + j 188.18) \text{ V}$$

$$Y_A = 1/Z_A = 1/(6+j8) = (0.06 - j0.08) S$$

$$Y_B = 1/Z_B = 1/(8+j6) = (0.08 - j0.06) S$$

$$Y_C = 1/Z_C = 1/20 = 0.05 S$$

$$\underline{U}_N = \frac{\underline{E}_A \cdot \underline{Y}_A + \underline{E}_B \cdot \underline{Y}_B + \underline{E}_C \cdot \underline{Y}_C}{\underline{Y}_A + \underline{Y}_B + \underline{Y}_C} = \frac{(230) \cdot (0.06 - j0.08) + (-115 - j198.18) \cdot (0.08 - j0.06) + (-115 + j188.18) \cdot (0.05)}{0.06 - j0.08 + 0.08 - j0.06 + 0.05} = \\ = (-0.77 - j89.54) = 99.54 e^{-j90.47^\circ} V$$

$$\underline{U}_A = \underline{E}_A - \underline{U}_N = 230 - (-0.77 - j89.54) = (230.77 + j89.54) V = 248.63 e^{j21.85^\circ} V$$

$$\underline{U}_B = \underline{E}_B - \underline{U}_N = (-115 - j198.18) - (-0.77 - j89.54) = (-114.23 - j106.65) V = 156.18 e^{-j136.87^\circ} V$$

$$\underline{U}_C = \underline{E}_C - \underline{U}_N = (-115 + j188.18) - (-0.77 - j89.54) = (-114.23 + j98.73) V = 156.18 e^{j111.38^\circ} V$$

$$\underline{I}_A = \frac{\underline{U}_A}{Z_A} = \frac{230.77 + j89.54}{6+j8} = (21.25 - j12.81) A = 24.86 e^{-j31.28^\circ} A$$

$$\underline{I}_B = \frac{\underline{U}_B}{Z_B} = \frac{-114.23 - j106.65}{8+j6} = (-15.54 - j1.68) A = 15.63 e^{-j173.86^\circ} A$$

$$\underline{I}_C = \frac{\underline{U}_C}{Z_C} = \frac{-114.23 + j98.73}{20} = (-5.71 + j4.58) A = 15.66 e^{j111.38^\circ} A$$



The rated current of the overcurrent circuit breaker:

$$I_n = 25 A$$


$$P_{TOTAL} = \operatorname{Re}\{\underline{Z}_A\} I_A^2 + \operatorname{Re}\{\underline{Z}_B\} I_B^2 + \operatorname{Re}\{\underline{Z}_C\} I_C^2 = \\ = 6 \cdot 24.86^2 + 8 \cdot 15.63^2 + 20 \cdot 15.66^2 = \\ = 10570.5 W$$

$$W = P_{TOTAL} \cdot \text{time} = 10570.5 \cdot 8 \cdot 5 = \\ = 422820 \text{ Wh} = 422.82 \text{ kWh}$$

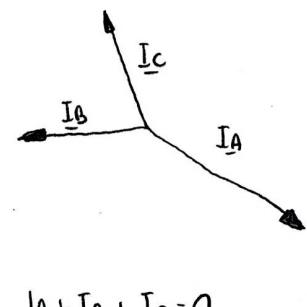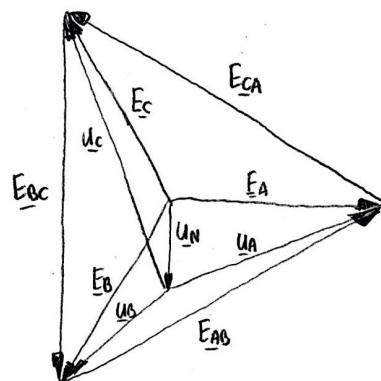
$$\text{cost} = 422.82 \cdot 0.288 = 122.2 \text{ Euro}$$



$$I_A + I_B + I_C = 0$$

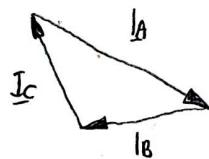

6)

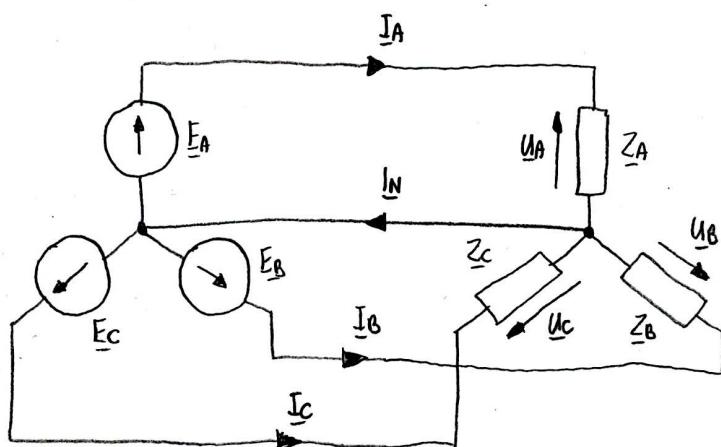

$$\underline{E}_A = 230 e^{j0^\circ} = 230 V$$

$$\underline{E}_B = 230 e^{-j120^\circ} = (-115 - j198.18) V$$

$$\underline{E}_C = 230 e^{+j120^\circ} = (-115 + j188.18) V$$

$$\underline{U}_A = \underline{E}_A \quad \underline{U}_B = \underline{E}_B \quad \underline{U}_C = \underline{E}_C$$

The rated current of the overcurrent circuit breaker:

$$I_n = 25 A$$

$$\underline{I}_A = \frac{\underline{U}_A}{Z_A} = \frac{230}{6+j8} = (13.8 - j18.4) = 23 e^{-j53.13^\circ} A$$

$$\underline{I}_B = \frac{\underline{U}_B}{Z_B} = \frac{(-115 - j198.18)}{8+j6} = (-21.15 - j9.04) A = 23 e^{-j156.87^\circ} A$$

$$\underline{I}_C = \frac{\underline{U}_C}{Z_C} = \frac{(-115 + j188.18)}{20} = (-5.75 + j9.96) A = 11.5 e^{+j190^\circ} A$$




$$\underline{I}_N = \underline{I}_A + \underline{I}_B + \underline{I}_C = (13.8 - j18.4) + (-21.15 - j9.04) + (-5.75 + j8.86) = (-13.10 - j17.48) A = 21.84 e^{-j126.86^\circ} A$$

$$P_{\text{TOTAL}} = \operatorname{Re}\{\underline{Z}_A\} \cdot I_A^2 + \operatorname{Re}\{\underline{Z}_B\} \cdot I_B^2 + \operatorname{Re}\{\underline{Z}_C\} \cdot I_C^2 = 6 \cdot 23^2 + 8 \cdot 23^2 + 20 \cdot 11.5^2 = 10051 \text{ W}$$

$$W = P_{\text{TOTAL}} \cdot \text{time} = 10051 \cdot 8.5 = 402.040 \text{ Wh} = 402.04 \text{ kWh}$$

$$\text{cost} = 402.04 \cdot 0.288 = 116.18 \text{ Euro}$$
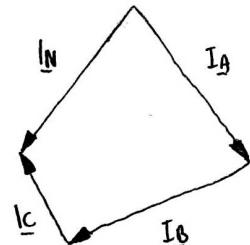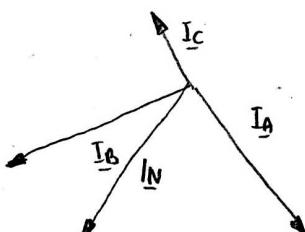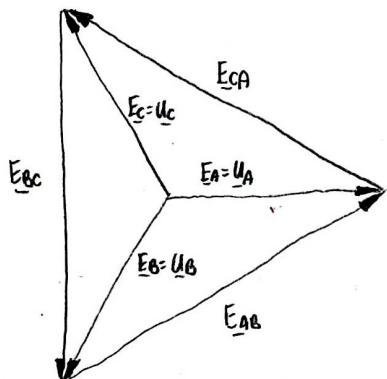
$$\underline{I}_A + \underline{I}_B + \underline{I}_C = \underline{I}_N$$




PROBLEM #2

A balanced 3-phase distribution line is used to supply three balanced Y-loads that are connected in parallel: Load 1: 37 kVA at 0.72 pf, lagging

Load 2: 64 kVA at 0.83 pf, leading

Load 3: 55 kW and 28 kVAr.

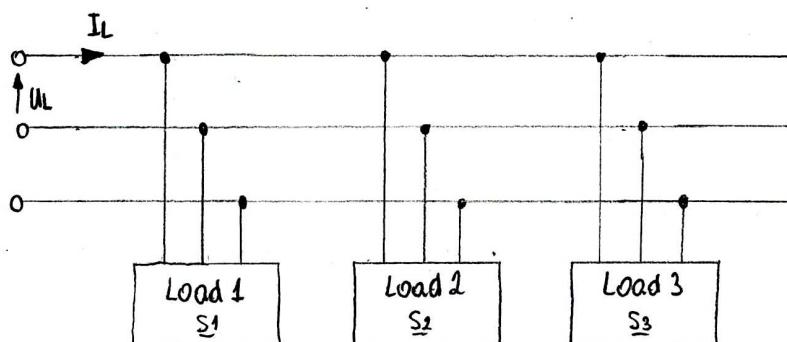The line voltage at the load is 600V rms. Find the line current in the distribution line and the combined power factor (pf) at the load.



$$\underline{S} = P + jQ \quad P = S \cdot \cos \varphi \quad Q = S \cdot \sin \varphi \quad S = \sqrt{P^2 + Q^2} \rightarrow Q = \sqrt{S^2 - P^2}$$

Load 1

$$\underline{S}_1 = 37000 \text{ VA} \quad \cos \varphi_1 = 0.72$$

$$P_1 = S_1 \cdot \cos \varphi_1 = 37000 \cdot 0.72 = 26640 \text{ W} \quad Q_1 = \sqrt{S_1^2 - P_1^2} = \sqrt{37000^2 - 26640^2} = 25677 \text{ VAr}$$

$$\underline{S}_1 = P_1 + jQ_1 = (26640 + j25677) \text{ VA} \quad \text{pf is lagging} \rightarrow Q > 0$$

Load 2

$$\underline{S}_2 = 64000 \text{ VA} \quad \cos \varphi_2 = 0.83$$

$$P_2 = S_2 \cdot \cos \varphi_2 = 64000 \cdot 0.83 = 53120 \text{ W} \quad Q_2 = \sqrt{S_2^2 - P_2^2} = \sqrt{64000^2 - 53120^2} = 35687 \text{ VAr}$$

$$\underline{S}_2 = P_2 - jQ_2 = (53120 - j35687) \text{ VA} \quad \text{pf is leading} \rightarrow Q < 0$$

Load 3

$$P_3 = 55000 \text{ W} \quad Q_3 = 28000 \text{ VAr}$$

$$S_3 = P_3 + jQ_3 = (55000 + j28000) \text{ VA}$$

S_T - total apparent power

$$\begin{aligned} S_T &= S_1 + S_2 + S_3 = 26640 + j25677 + 53120 - j35687 + 55000 + j28000 = (134760 + j18880) \text{ VA} = \\ &= 136090 e^{j8.02^\circ} \text{ VA} \end{aligned}$$

In the case of balanced load

$$S_T = 3 \cdot V_p \cdot I_p \quad V_p - \text{phase voltage}, \quad I_p - \text{phase current}$$

or

$$S_T = \sqrt{3} \cdot V_L \cdot I_L \quad V_L - \text{line voltage}, \quad I_L - \text{line current}$$

↓

$$I_L = \frac{S_T}{\sqrt{3} \cdot V_L} = \frac{136090}{\sqrt{3} \cdot 660} = 119.05 \text{ A}$$

Combined power factor

$$\varphi = 8.02^\circ \quad \cos \varphi = \cos 8.02^\circ = 0.88$$

$$\text{pf load} = 0.88$$

PROBLEM #3

A 3-phase electric heater with nominal power $P_n = 15 \text{ kW}$ is used to heat the warehouse. The heater is supplied from a power network with a phase voltage of $U_n = 230 \text{ V}$. The heating elements are Δ -connected. The heater operates at full power for 12 hours a day. A photovoltaic installation has been installed in close proximity to the warehouse, which has caused the phase voltage increase from $U_n = 230 \text{ V}$ to $U_n' = 242 \text{ V}$. Calculate the percentage increase in warehouse heating costs in one day due to the increase in phase voltage.

The energy consumption: $W = P_n \cdot t = 15000 \cdot 12 = 180 \text{ kWh}$

$$\text{Power of one phase of the heater: } P_1 = \frac{P_n}{3} = \frac{15000}{3} = 5 \text{ kW}$$

$$P_1 = U_{\text{phase}} \cdot I_{\text{phase}} \cdot \cos \varphi = \frac{U_{\text{phase}}^2}{R} \cdot \cos \varphi \quad U_{\text{phase}} = U_L = \sqrt{3} U_n$$

$$R = \frac{U_{\text{phase}}^2}{P_1} = \frac{(\sqrt{3} U_n)^2}{P_1} = \frac{(\sqrt{3} \cdot 230)^2}{5000} = 31.74 \text{ }\Omega$$

$$\cos \varphi = 1 \quad (\text{the heater is resistive in nature})$$

$$U_n = 230 \text{ V} \rightarrow U_n' = 242 \text{ V} \quad (\text{increase by } 5.2\%)$$

$$\text{Power of one phase of the heater: } P_2 = \frac{U_L^2}{R} = \frac{(\sqrt{3} \cdot U_n')^2}{R} = \frac{(\sqrt{3} \cdot 242)^2}{31.74} = 5535.35 \text{ W}$$

$$W' = 3 \cdot 12 \cdot P_2 = 3 \cdot 12 \cdot 5535.35 = 188.27 \text{ kWh}$$

The percentage increase in costs:

$$\frac{W' - W}{W} \cdot 100\% = \frac{188.27 - 180}{180} \cdot 100\% = 10.71\%$$

PROBLEM #4

In the room, there is a three-phase electric motor supplied from a power network with a voltage of $U_n = 230 / 400 \text{ V}$. The motor windings are Δ -connected. The motors parameters are: nominal power $P_1 = 15 \text{ kW}$, motor efficiency $\eta_1 = 0.885$, power factor $\cos \varphi_1 = 0.8$. It was decided to install a second three-phase motor in the same room with the parameters: $P_2 = 7.5 \text{ kW}$, $\eta_2 = 0.88$, $\cos \varphi_2 = 0.88$. The room is supplied with power by a copper wire $5 \times 6 \text{ mm}^2$. Check whether, after installing the second motor, the cable cross-section will be sufficient due to its long-term current carrying capacity. In the case of 5-core copper conductors laid in the room, the long-term current carrying capacities are: $1.5 \text{ mm}^2 - 17 \text{ A}$, $2.5 \text{ mm}^2 - 24 \text{ A}$, $4 \text{ mm}^2 - 31 \text{ A}$, $6 \text{ mm}^2 - 40 \text{ A}$, $10 \text{ mm}^2 - 55 \text{ A}$.

$$\eta = \frac{\text{mechanical power}}{\text{electrical power}} \Rightarrow \text{electrical power} = \frac{\text{mechanical power}}{\eta}$$

$$P_{1e} = \frac{P_1}{\eta_1} = \frac{15000}{0.885} = 16758.8 \text{ W}$$

$$P_{2e} = \frac{P_2}{\eta_2} = \frac{7500}{0.88} = 8522.7 \text{ W}$$

$$S = \frac{P}{\cos \varphi} \quad Q = \sqrt{S^2 - P^2}$$

$$S_1 = \frac{P_{1e}}{\cos \varphi_1} = \frac{16758.8}{0.8} = 18622 \text{ VA}$$

$$Q_1 = \sqrt{S_1^2 - P_{1e}^2} = \sqrt{18622^2 - 16758.8^2} = 8117.1 \text{ VAr}$$

$$S_2 = \frac{P_{2e}}{\cos \varphi_2} = \frac{8522.7}{0.88} = 9684.9 \text{ VA}$$

$$Q_2 = \sqrt{S_2^2 - P_{2e}^2} = \sqrt{9684.9^2 - 8522.7^2} = 4600 \text{ VAr}$$

$$S_1 = P_{1e} + j Q_1 = (16758.8 + j 8117.1) \text{ VA}$$

$$S_2 = P_{2e} + j Q_2 = (8522.7 + j 4600) \text{ VA}$$

$$S_T = S_1 + S_2 = (25282.5 + j 12717.1) \text{ VA}$$

$$S_T = |S_T| = 28300 \text{ VA}$$

$$S = 3 \cdot U_{\text{phase}} \cdot I_{\text{phase}} = \sqrt{3} \cdot U_{\text{line}} \cdot I_{\text{line}}$$

$$I_{\text{line}} = \frac{S}{\sqrt{3} \cdot U_{\text{line}}} = \frac{28300}{\sqrt{3} \cdot \sqrt{3} \cdot 230} = 41.02 \text{ A}$$

The cross section of the cable supplying the motors will be too small.