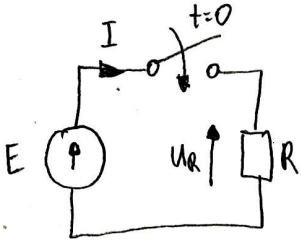




ELECTRICAL CIRCUITS 2 - CLASS NO. 10 (21.05.2024)

TRANSIENT AND STEADY STATE

*** R CIRCUIT**




$t < 0$	$t \gg 0$
$I = 0$	$I = \frac{E}{R}$
$U_R = 0$	$U_R = E$

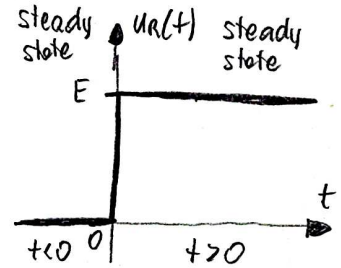
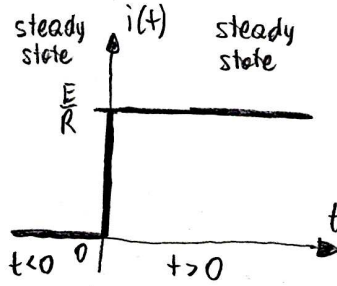


E - DC voltage source


*** RC CIRCUIT**

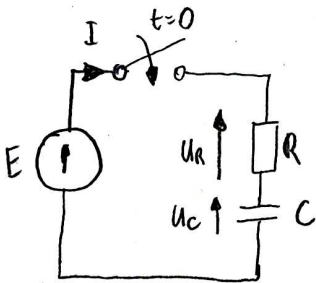




$t < 0$	$t \gg 0$
$I = 0$	$I = 0$
$U_R = 0$	$U_R = 0$
$U_C = 0$	$U_C = E$

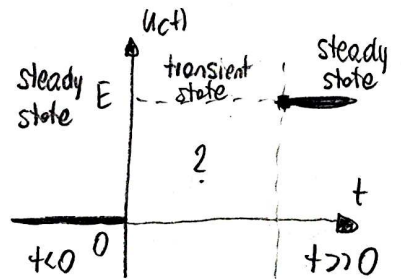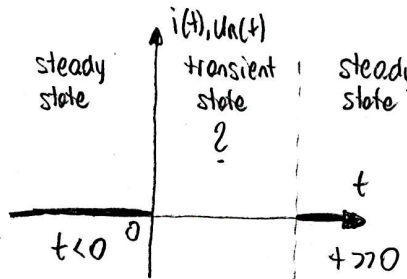

*** RL CIRCUIT**

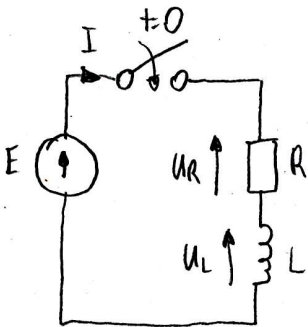

$t < 0$	$t \gg 0$
$I = 0$	$I = \frac{E}{R}$
$U_R = 0$	$U_R = E$
$U_L = 0$	$U_L = 0$

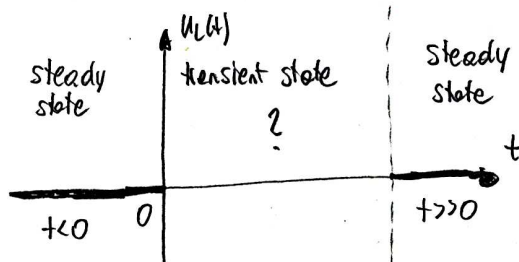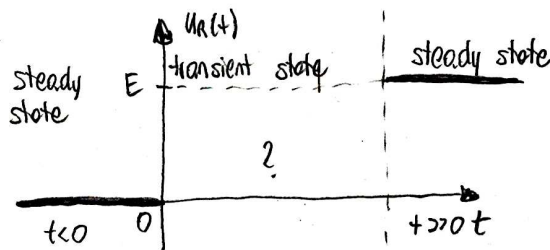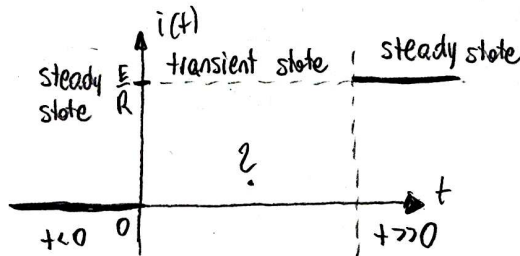


INITIAL AND STEADY STATE VALUES

* initial conditions

- for C \rightarrow U_C at $t=0$
- for L \rightarrow I_L at $t=0$

* example 1

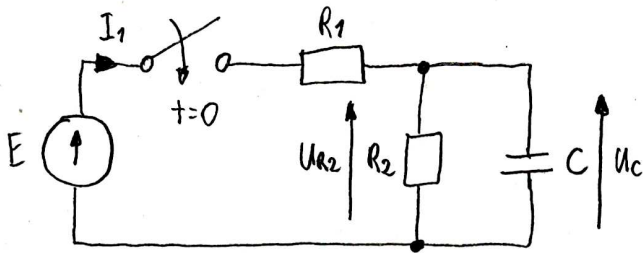


$t < 0$
 $U_C = 0$

$t \gg 0$
 $U_C = U_{R2}$
 $I_1 = \frac{E}{R_1 + R_2}$
 $U_{R2} = U_C = I_1 \cdot R_2 = \frac{R_2 \cdot E}{R_1 + R_2}$

$U_C = \frac{R_2 \cdot E}{R_1 + R_2}$


* example 2

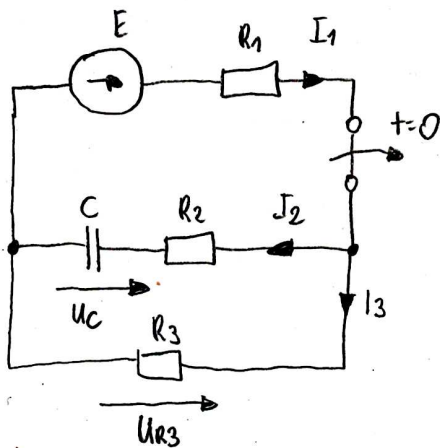

$t < 0$
 $U_C = U_{R3}$
 $I_2 = 0$, C \rightarrow open circuit for DC


$I_1 = I_3$
 $I_1 = \frac{E}{R_1 + R_3}$
 $U_{R3} = I_1 \cdot R_3 = \frac{R_3 \cdot E}{R_1 + R_3}$

$U_C = \frac{R_3 \cdot E}{R_1 + R_3}$

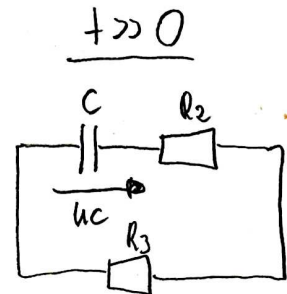


$t \gg 0$
 no source \rightarrow $U_C = 0$

* example 3

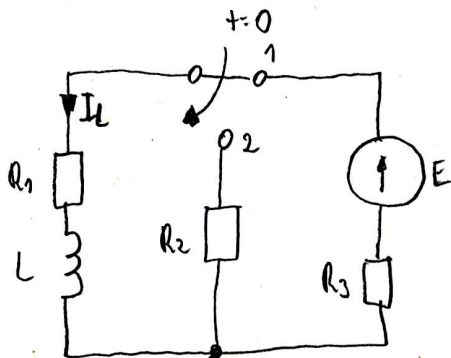

$t < 0$
 L \rightarrow short circuit for DC


$I_L = \frac{E}{R_1 + R_3}$

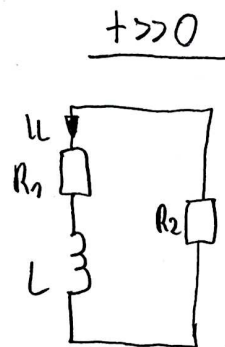

$t \gg 0$
 no source \rightarrow $I_L = 0$

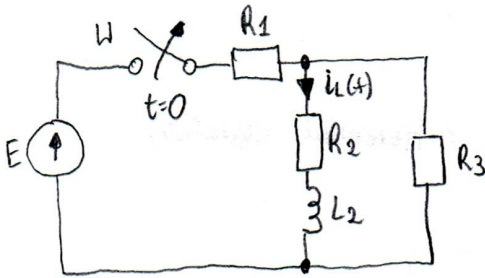PROBLEM #1

The circuit shown in the figure has been in a steady-state. The switch was open at $t=0$. Find $i_L(t)$. $E=80V$, $R_1=120\Omega$, $R_2=50\Omega$, $R_3=200\Omega$, $L_2=0.75H$.




* INITIAL VALUES ($t < 0$), steady-state before opening the switch

Notes:

- We consider circuit as a DC circuit
- in the case of a DC circuit, we replace inductor with a short-circuit and capacitor with an open-circuit
- We use classical methods: Ohm's Law, KCL, KVL

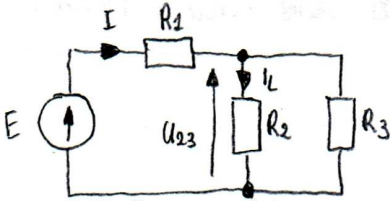our circuit before opening the switch (DC circuit), $I_L = ?$



$$I = \frac{E}{R_1 + \frac{R_2 \cdot R_3}{R_2 + R_3}} = \frac{80}{120 + \frac{50 \cdot 200}{50 + 200}} = \frac{80}{120 + 40} = \frac{80}{160} = 0.5 \text{ A}$$

$$U_{23} = I \cdot \frac{R_2 \cdot R_3}{R_2 + R_3} = 0.5 \cdot \frac{50 \cdot 200}{50 + 200} = 0.5 \cdot 40 = 20 \text{ V}$$

$$I_L = \frac{U_{23}}{R_2} = \frac{20}{50} = 0.4 \text{ A}$$

* TRANSIENT ANALYSIS ($t > 0$), circuit after opening the switch

Notes:

- We write differential equation with the use of KVL or KCL
- note that: $u_L = L \frac{di_L(t)}{dt}$ $i_C(t) = C \frac{du_C(t)}{dt}$
- general form of differential equation:

$$a_n \frac{d^n x(t)}{dt^n} + a_{n-1} \frac{d^{n-1} x(t)}{dt^{n-1}} + \dots + a_1 \frac{dx(t)}{dt} + a_0 x(t) = f(t) \quad (1)$$

where:


$x(t)$ - searched quantity (current (voltage))

$a_n, a_{n-1}, \dots, a_1, a_0$ - constant coefficients (R, L, C, M in the circuit)

$f(t)$ - voltage and current sources

n - the order of differential equation (the number of inductors/capacitors in the circuit)

our circuit after opening the switch

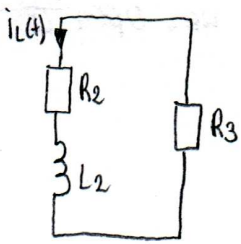

using KVL:

$$u_{R_2}(t) + u_{L_2}(t) + u_{R_3}(t) = 0$$

$$R_2 \cdot i_L(t) + L_2 \frac{di_L(t)}{dt} + R_3 \cdot i_L(t) = 0$$

$$\boxed{L_2 \frac{di_L(t)}{dt} + (R_2 + R_3) i_L(t) = 0} \quad \text{- a first-order differential equation}$$

Notes:

- the solution of equation (1) has a form

$$x(t) = x_p(t) + x_c(t) \quad (2)$$

where:

$x_p(t)$ - the particular integral solution (forced response)


$x_c(t)$ - the complementary solution (natural response)

in our case: $i_L(t) = i_{LP}(t) + i_{LC}(t)$

Notes:

- the particular integral solution we obtain by solving the steady state circuit ($t \rightarrow \infty$)

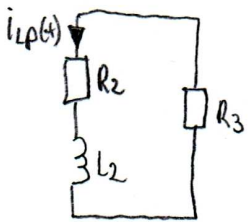in steady state ($t \rightarrow \infty$) $i_{LP}(t) = ?$



$i_{LP}(t) = 0$ ← because there is no voltage source in the circuit

Notes:

- we obtain the complementary solution by solving the homogeneous equation (1)

$$a_n \frac{d^n x_c(t)}{dt^n} + a_{n-1} \frac{d^{n-1} x_c(t)}{dt^{n-1}} + \dots + a_1 \frac{dx_c(t)}{dt} + a_0 x_c(t) = 0 \quad (3)$$

- the solution of (3) has a form:

$$x_c(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + \dots + A_n e^{s_n t}$$

where:

s_1, s_2, \dots, s_n - roots of characteristic equation: $a_n s^n + a_{n-1} s^{n-1} + \dots + a_1 s + a_0 = 0$

A_1, A_2, \dots, A_n - integration constants determined with the use of initial values

$i_{lc}(t)$ - the complementary solution
 a first-order differential equation:

$$L_2 \frac{di_{lc}(t)}{dt} + (R_2 + R_3) i_{lc}(t) = 0$$

has a solution in the form:

$$i_{lc}(t) = A_1 \cdot e^{s_1 t}$$

s_1 is determined from the characteristic equation:

$$L_2 \cdot s_1 + (R_2 + R_3) = 0 \Rightarrow s_1 = -\frac{R_2 + R_3}{L_2} = -\frac{50 + 100}{0.75} = -333.33$$

A_1 is determined with the use of initial conditions

$$\text{at } t=0: i_L(0^-) = i_L(0^+) \quad i_L(0^-) = i_L(0^+) = I_L = 0.4 \text{ A}$$

$$i_L(t) = i_{lp}(t) + i_{lc}(t)$$

$$i_L(t) = 0 + A_1 e^{s_1 t}$$


$$i_L(t) = A_1 e^{-\frac{R_2 + R_3}{L_2} \cdot t}$$

$$t=0 \Rightarrow 0.4 = A_1 e^{-\frac{R_2 + R_3}{L_2} \cdot 0} = 1$$


$$A_1 = 0.4$$

finally:
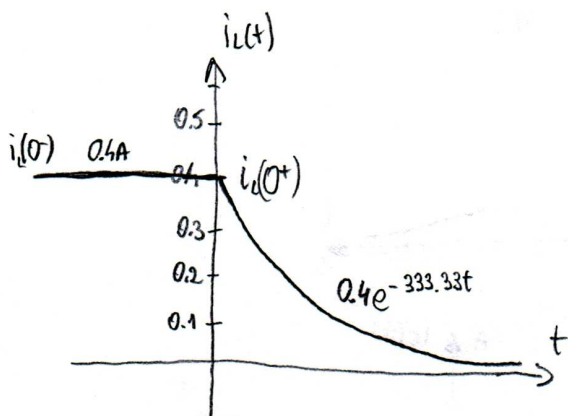
$$i_L(t) = i_{lp}(t) + i_{lc}(t) = 0 + 0.4 e^{-333.33t} = 0.4 e^{-333.33t} \text{ A}$$



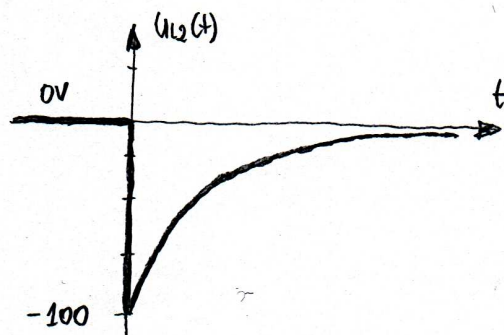
$$u_{L2}(t) = L_2 \frac{di_L(t)}{dt} = 0.75 \frac{d}{dt} (0.4 e^{-333.33t}) = 0.75 \cdot 0.4 \cdot (-333.33) e^{-333.33t} = -100 e^{-333.33t}$$




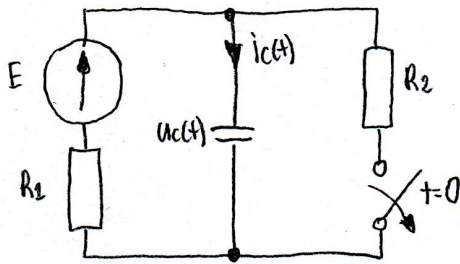PROBLEM #2

The circuit shown in the figure has been in a steady-state. The switch was open at $t=0$. Calculate and plot $i_c(t)$ and $U_c(t)$ for $t < 0$, $t=0$ and $t > 0$. $E=100V$, $R_1=20\Omega$, $R_2=40\Omega$, $C=10mF$.



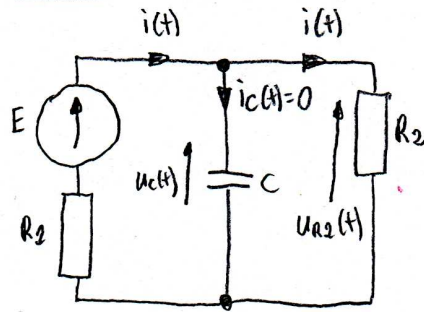steady-state before opening the switch ($t < 0$)



$$i_c(t) = 0 \text{ A}$$


$$U_c(t) = U_{R_2}(t)$$

$$i(t) = \frac{E}{R_1 + R_2}$$

$$U_{R_2}(t) = R_2 \cdot i(t) = \frac{R_2}{R_1 + R_2} \cdot E$$

$$U_{R_2}(t) = \frac{40}{20+40} \cdot 100 = 66,67 \text{ V}$$

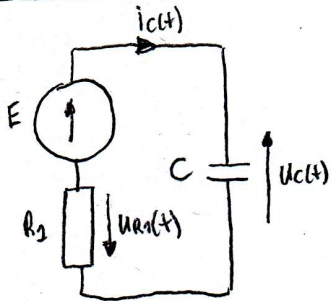circuit after opening the switch ($t > 0$)



$$U_{R_1}(t) + U_c(t) = E$$

$$R_1 \cdot i_c(t) + U_c(t) = E$$


$$i_c(t) = C \frac{dU_c(t)}{dt}$$

$$R_1 C \frac{dU_c(t)}{dt} + U_c(t) = E$$

$$U_c(t < 0) = 66,67 \text{ V}$$

$$U_c(t = 0) = 66,67 \text{ V}$$
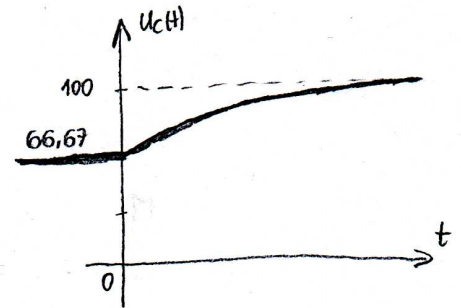
$$U_c(t \rightarrow \infty) = 100 \text{ V}$$



$$U_c(t) = U_{cp}(t) + U_{cc}(t)$$

$U_{cp}(t)$ - the particular solution ($t \gg 0$)

$$U_{cp}(t) = E = 100 \text{ V}$$

$U_{cc}(t)$ - the complementary solution

$$R_1 C \frac{dU_{cc}(t)}{dt} + U_{cc}(t) = 0 \quad U_{cc}(t) = A_1 e^{s_1 t}$$

$$R_1 C s_1 + 1 = 0 \Rightarrow s_1 = -\frac{1}{R_1 C} = -\frac{1}{20 \cdot 0,01} = -\frac{1}{0,2} = -5 \text{ s}^{-1}$$

at $t=0$

$$U_c(t) = U_{cp}(t) + U_{cc}(t)$$

$$66,67 = 100 + A_1 e^0 \Rightarrow A_1 = 66,67 - 100 = -33,33 \text{ V}$$

$$U_{cc}(t) = -33,33 e^{-5t} \text{ V}$$


$$U_c(t) = U_{cp}(t) + U_{cc}(t) = 100 - 33,33 e^{-5t} \text{ V}$$

$$i_c(t) = C \frac{dU_c(t)}{dt} = 0,01 \frac{d}{dt} (100 - 33,33 e^{-5t}) = 0,01 \cdot 33,33 \cdot 5 e^{-5t} = 1,67 e^{-5t} \text{ A}$$

$$i_c(t < 0) = 0 \text{ A}$$


$$i_c(t = 0) = 1,67 \text{ A}$$
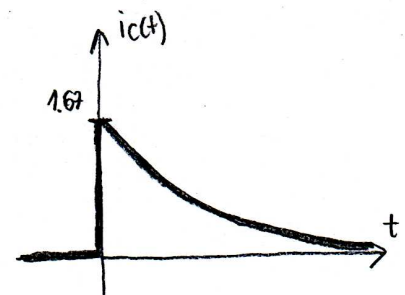
$$i_c(t \rightarrow \infty) = 0 \text{ A}$$



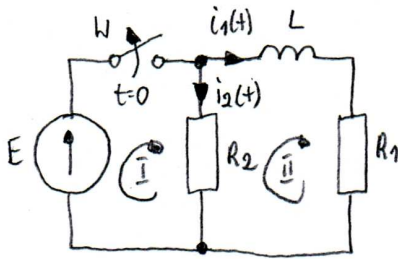PROBLEM #3

The circuit shown in the figure has been in a steady-state. The switch was open at $t=0$. Plot $i_1(t)$ and $i_2(t)$ for $t < 0$, $t=0$ and $t > 0$. Use the classical method. $E=100V$, $L=0.1H$, $R_1=25\Omega$, $R_2=75\Omega$.



steady-state before opening switch ($t < 0$)

$$\begin{cases} I_I R_2 - I_{II} R_2 = E \\ -I_I R_2 + I_{II} (R_1 + R_2) = 0 \end{cases}$$

$$I_I R_2 = E + I_{II} R_2$$

$$I_I = \frac{E + I_{II} R_2}{R_2} = \frac{100 + 4 \cdot 75}{75} = \frac{400}{75} = 5.33 \text{ A}$$


$$\begin{cases} 75 I_I - 75 I_{II} = 100 \\ -75 I_I + 100 I_{II} = 0 \end{cases} +$$

$$i_I = I_{II} = \boxed{4 \text{ A}}$$

$$\begin{aligned} 25 I_{II} &= 100 \\ I_{II} &= 4 \text{ A} \end{aligned}$$

$$i_a = I_I - I_{II} = 5.33 - 4 = \boxed{1.33 \text{ A}}$$

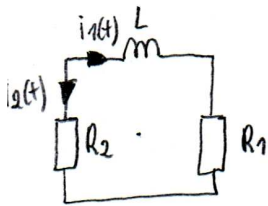circuit after opening the switch ($t > 0$)



using KVL:

$$i_2(t) \cdot R_2 + i_1(t) \cdot R_2 + L \frac{di_1(t)}{dt} = 0$$

$$L \frac{di_1(t)}{dt} + (R_1 + R_2) i_1(t) = 0$$

$$i_2(t) = i_{sp}(t) + i_{sc}(t)$$

$i_{sp}(t)$ - the particular solution

$$i_{sp}(t) = 0$$

$i_{sc}(t)$ - the complementary solution

$$L \frac{di_{sc}(t)}{dt} + (R_1 + R_2) i_{sc}(t) = 0$$

$$L s_1 + R_1 + R_2 = 0 \quad s_1 = -\frac{R_1 + R_2}{L}$$

$$i_{sc} = A_2 e^{s_1 t}$$

$$\text{at } t=0: i_2(t) = i_{sp}(t) + i_{sc}(t)$$

$$4 = 0 + A_2 e^0 \Rightarrow A_2 = 4$$

$$i_2(t) = 4e^{-1000t} \text{ A}$$

$$i_1(t) = -i_2(t) = -4e^{-1000t} \text{ A}$$

