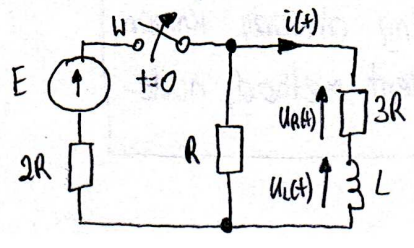


# ELECTRICAL CIRCUITS 2 - CLASS NO. 11 (28.05.2024)


## PROBLEM #1

The circuit shown in the figure has been in a steady-state. The switch was open at  $t=0$ . Find and plot  $i(t)$ ,  $u_L(t)$ ,  $u_R(t)$ . Use the Laplace transform.



- \* We start from determining the initial values in the circuit - we solve circuit for initial capacitor voltages ( $u_C(0^-)$ ) and inductor currents ( $i_L(0^-)$ )
- \* this requires the analysis of a circuit valid for  $t < 0$  drawn with all capacitors replaced by open circuits and all inductors replaced by short circuits

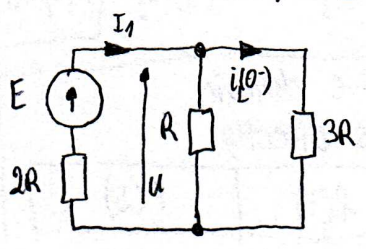circuit for  $t < 0, t = 0^-$  ( $i_L(0^-) = ?$ )



$$R_{eq} = 2R$$

$$I_1 = \frac{E}{R_{eq}}$$

$$R_{eq} = 2R + \frac{R \cdot 3R}{R + 3R} = 2R + \frac{3R^2}{4R} = 2R + \frac{3}{4}R = \frac{11}{4}R$$



$$I_1 = \frac{E}{R_{eq}} = \frac{E}{\frac{11}{4}R} = \frac{4E}{11R}$$

$$U = I_1 \cdot \frac{R \cdot 3R}{R + 3R} = \frac{4E}{11R} \cdot \frac{3R^2}{4R} = \frac{3E}{11}$$


$$i_L(0^-) = \frac{U}{3R} = \frac{3E}{11 \cdot 3R} = \frac{E}{11R}$$

\* next, we transform the problem from the time domain to the complex frequency domain (that is, s-domain)

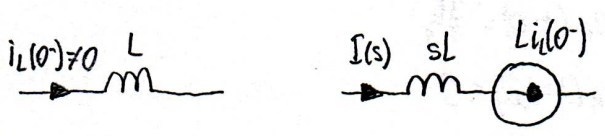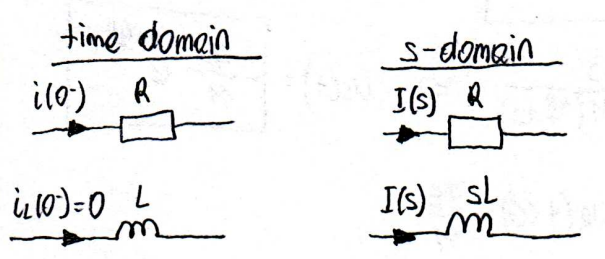\* we draw an s-domain circuit by substituting an s-domain representation for all circuit elements



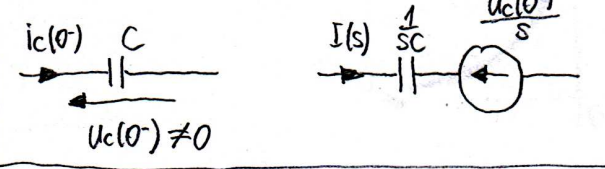
the initial condition of inductor is represented by a voltage source ( $Li_L(0^-)$ ), whose direction is the same as the  $i_L(0^-)$  current direction



the initial condition of capacitor is represented by a voltage source  $\frac{u_C(0^-)}{s}$ , whose direction is the same as the voltage drop  $u_C(0^-)$



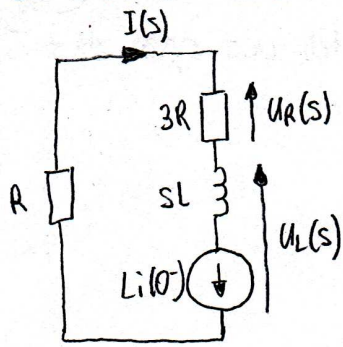on s-domain circuit,  $t > 0$ ,  $i_L(0^-) = i_L(0^+)$



\* next, we solve the circuit equations algebraically in the complex frequency domain using already known methods: Ohm's Law, KVL, KCL, loop-current method, node-voltage method, etc.

$$I(s) = \frac{Li(0^-)}{R+3R+sL} = \frac{L \cdot E}{11R(4R+sL)} = \frac{LE}{11R(4\frac{R}{L}+s)} = \boxed{\frac{E}{11R(4\frac{R}{L}+s)}}$$

$$U_R(s) = 3R \cdot I(s) = \frac{3RE}{11R(4\frac{R}{L}+s)} = \boxed{\frac{3E}{11(4\frac{R}{L}+s)}}$$

$$U_L(s) = sL \cdot I(s) - Li(0^-) = \frac{sLE}{11R(4\frac{R}{L}+s)} - \frac{LE}{11R} = \frac{LE}{11R} \left[ \frac{s}{4\frac{R}{L}+s} - 1 \right] = \frac{LE}{11R} \left[ \frac{s - 4\frac{R}{L} - s}{4\frac{R}{L}+s} \right] = \frac{-4RLE}{11R(4\frac{R}{L}+s)} = \boxed{\frac{-4E}{11(4\frac{R}{L}+s)}}$$

\* finally, we transform the solution from the s-domain back to the time domain  
 \* for simple solutions, we can use table of Laplace transform pairs directly

$f(t)$	$F(s)$
$\epsilon(t)$	$\frac{1}{s}$
$\epsilon(t+a)$	$\frac{1}{s} e^{-as}$
$\delta(t)$	1

$f(t)$	$F(s)$
$e^{-at} (a > 0)$	$\frac{1}{s+a}$
$e^{at} (a < 0)$	$\frac{1}{s-a}$
$t$	$\frac{1}{s^2}$

$f(t)$	$F(s)$
$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$
$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$
$\frac{t^{n-1}}{(n-1)!}$	$\frac{1}{s^n} (n=1, 2, \dots)$

$$I(s) = \frac{E}{11R(4\frac{R}{L}+s)} \quad \mathcal{L}^{-1} \left[ \frac{1}{a+s} \right] = e^{-at} \quad \Rightarrow \quad i(t) = \boxed{\frac{E}{11R} e^{-\frac{4R}{L}t}}$$

$$U_R(s) = \frac{3E}{11(4\frac{R}{L}+s)} \quad \Rightarrow \quad U_R(t) = \boxed{\frac{3E}{11} e^{-\frac{4R}{L}t}}$$

$$U_L(s) = \frac{-4E}{11(4\frac{R}{L}+s)} \quad \Rightarrow \quad U_L(t) = \boxed{-\frac{4E}{11} e^{-\frac{4R}{L}t}}$$

$$i(t < 0) = \frac{E}{11R}$$

$$i(t = 0) = \frac{E}{11R}$$

$$i(t \rightarrow \infty) = 0$$

$$U_L(t < 0) = 0$$




$$U_L(t = 0) = -\frac{4E}{11}$$

$$U_L(t \rightarrow \infty) = 0$$

$$U_R(t < 0) = \frac{3E}{11}$$

$$U_R(t = 0) = \frac{3E}{11}$$



$$U_R(t \rightarrow \infty) = 0$$

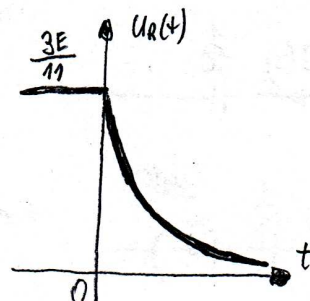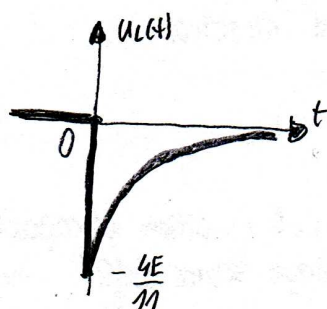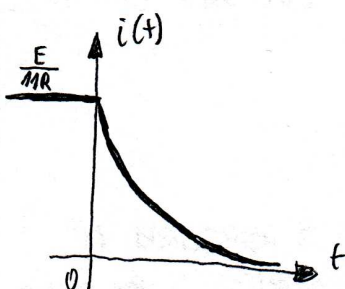


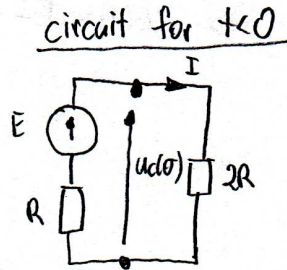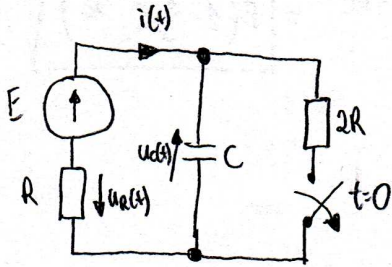
## PROBLEM #2


The circuit shown in the figure has been in a steady-state. The switch was open at  $t=0$ , find and plot  $i(t)$ ,  $u_C(t)$ ,  $u_R(t)$ .



$$I = \frac{E}{R+2R} = \frac{E}{3R}$$

$$u_C(0^-) = 2R \cdot I = 2R \cdot \frac{E}{3R} = \boxed{\frac{2E}{3}}$$

circuit for  $t > 0$  (s-domain circuit)

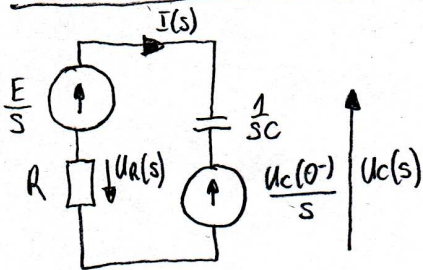

$$I(s) = \frac{\frac{E}{s} - \frac{u_C(0^-)}{s}}{R + \frac{1}{sC}} = \frac{E - u_C(0^-)}{s(R + \frac{1}{sC})} = \frac{E - \frac{2E}{3}}{sR + \frac{1}{C}} = \frac{\frac{1}{3}E}{R(s + \frac{1}{RC})} = \boxed{\frac{E}{3R(s + \frac{1}{RC})}}$$

$$u_C(s) = I(s) \cdot \frac{1}{sC} + \frac{u_C(0^-)}{s}$$

$$u_C(s) = \frac{E}{3R(s + \frac{1}{RC})} \cdot \frac{1}{sC} + \frac{2E}{3s} = \frac{E}{3R s C (s + \frac{1}{RC})} + \frac{2E}{3s} = \boxed{\frac{E}{3s(RCs + 1)}} + \frac{2E}{3s} = \boxed{\frac{A_1}{s - s_1} + \frac{A_2}{s - s_2}} + \frac{2E}{3s}$$

this transformation requires partial fraction decomposition

\* we have a rational function of  $s$  of the form:

$$F(s) = \frac{P(s)}{Q(s)} = \frac{a_m s^m + a_{m-1} s^{m-1} + \dots + a_1 s + a_0}{b_n s^n + b_{n-1} s^{n-1} + \dots + b_1 s + b_0}$$

the roots of the polynomial  $P(s)$  are called the zeros of the function  $F(s)$

if  $m < n$  and zeros are different from poles:

the roots of the polynomial  $Q(s)$  are called the poles of the function  $F(s)$

$$\frac{P(s)}{Q(s)} = \frac{A_1}{s - s_1} + \frac{A_2}{s - s_2} + \dots + \frac{A_n}{s - s_n} \quad \text{where } A_k = \frac{P(s_k)}{Q'(s_k)}, \quad k = 1, 2, \dots, n$$

$$F(s) = \frac{P(s)}{Q(s)} = \frac{E}{3s(RCs + 1)} = \frac{A_1}{s - s_1} + \frac{A_2}{s - s_2}$$

$$P(s) = E$$

$$Q(s) = 3s(RCs + 1) = 3RCs^2 + 3s \quad Q'(s) = 6RCs + 3$$

poles  $Q(s) = 0 \quad 3s(RCs + 1) = 0$  when  $3s = 0$  and  $RCs + 1 = 0$

$$s_1 = 0 \quad s_2 = -\frac{1}{RC}$$

$$A_1 = \frac{P(s_1)}{Q'(s_1)} = \frac{E}{6RC \cdot 0 + 3} = \frac{E}{3}$$

$$A_2 = \frac{P(s_2)}{Q'(s_2)} = \frac{E}{6RC \cdot (-\frac{1}{RC}) + 3} = \frac{E}{-6+3} = -\frac{E}{3}$$

$$F(s) = \frac{E}{3s} - \frac{E}{3(s+\frac{1}{RC})}$$

$$U_C(s) = \frac{E}{3s} - \frac{E}{3(s+\frac{1}{RC})} + \frac{2E}{3s} = \frac{E}{s} - \frac{E}{3(s+\frac{1}{RC})} \Rightarrow u_C(t) = E - \frac{E}{3}e^{-\frac{t}{RC}} = \boxed{E(1 - \frac{1}{3}e^{-\frac{t}{RC}})}$$

$$I(s) = \frac{E}{3R(s+\frac{1}{RC})} \Rightarrow i(t) = \boxed{\frac{E}{3R}e^{-\frac{t}{RC}}}$$

or

$$i(t) = C \frac{du_C(t)}{dt} = C \frac{d}{dt} \left( E - \frac{E}{3}e^{-\frac{t}{RC}} \right) = C \frac{E}{3} \frac{1}{RC} e^{-\frac{t}{RC}} = \boxed{\frac{E}{3R}e^{-\frac{t}{RC}}}$$

$$U_R(s) = R \cdot I(s) = \frac{ER}{3R(s+\frac{1}{RC})} = \boxed{\frac{E}{3}e^{-\frac{t}{RC}}}$$

or

$$U_R(t) = R \cdot i(t) = \frac{R \cdot E}{3R} e^{-\frac{t}{RC}} = \boxed{\frac{E}{3}e^{-\frac{t}{RC}}}$$

$$u_C(t < 0) = \frac{2E}{3}$$

$$i(t < 0) = \frac{E}{3R}$$

$$U_R(t < 0) = \frac{E}{3}$$

$$u_C(t=0) = \frac{2E}{3}$$




$$i(t=0) = \frac{E}{3R}$$

$$U_R(t=0) = \frac{E}{3}$$

$$u_C(t \rightarrow \infty) = E$$

$$i(t \rightarrow \infty) = 0$$

$$U_R(t \rightarrow \infty) = 0$$

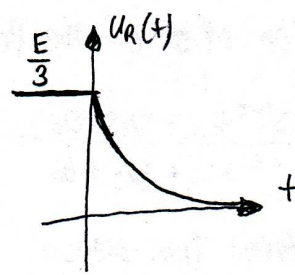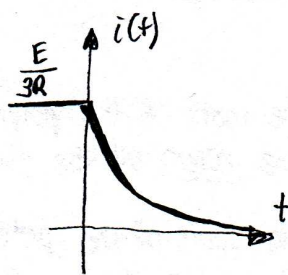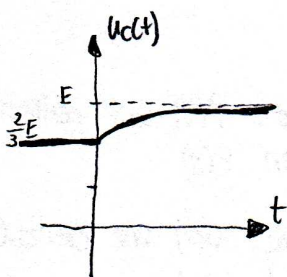




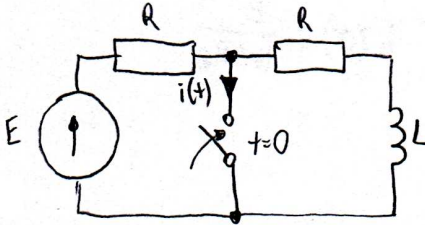
### PROBLEM #3

a)

The circuit shown in the figure has been in a steady-state. The switch was close at  $t=0$ . Calculate and plot  $i(t)$ . Use the Laplace transform.




circuit for  $t < 0$

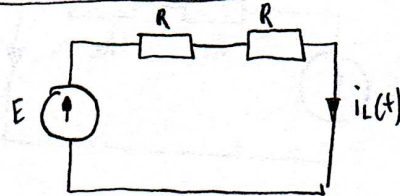

$$i_L(0^-) = \frac{E}{R+R} = \frac{E}{2R}$$

$$i(t) = 0$$

circuit for  $t > 0$  (s-domain circuit)

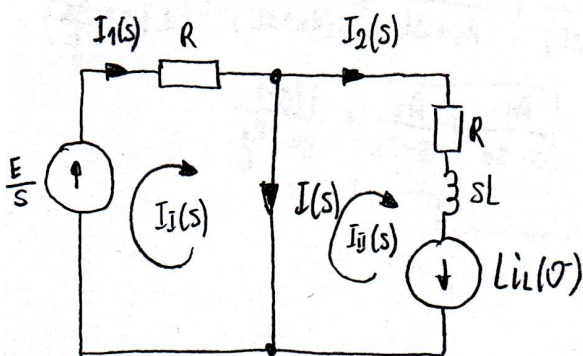

$$\begin{cases} I_I(s) \cdot R = \frac{E}{s} \\ I_{II}(s)(R+sL) = Li_L(0^-) \end{cases}$$

$$\Rightarrow I_I(s) = \frac{E}{Rs}$$

$$\Rightarrow I_{II}(s) = \frac{Li_L(0^-)}{R+sL}$$


$$I(s) = I_I(s) - I_{II}(s) = \frac{E}{sR} - \frac{Li_L(0^-)}{R+sL} = \frac{E}{sR} - \frac{L \cdot \frac{E}{2R}}{R+sL} = \frac{1}{R} \cdot \frac{E}{s} - \frac{E}{2R(\frac{R}{L}+s)}$$

$$i(t) = \frac{E}{R} - \frac{E}{2R} e^{-\frac{R}{L}t}$$


$$\frac{1}{s} \leftrightarrow \mathcal{E}(t) \quad \frac{1}{s+a} \leftrightarrow e^{-at}$$

$$i(0) = \frac{E}{R} - \frac{E}{2R} = \frac{E}{2R}$$
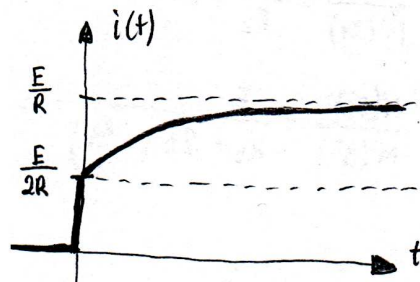
$$i(t \rightarrow \infty) = \frac{E}{R}$$



b)

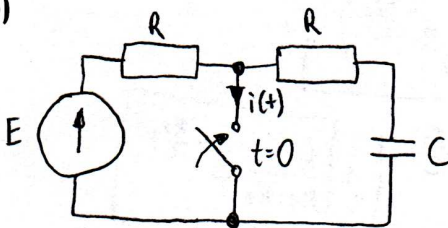


circuit for  $t < 0$

$$u_C(0^-) = E, \quad i(t) = 0$$

$$i(0) = \frac{E}{R} + \frac{E}{R} = \frac{2E}{R}$$

$$i(t \rightarrow \infty) = \frac{E}{R}$$

circuit for  $t > 0$  (s-domain circuit)

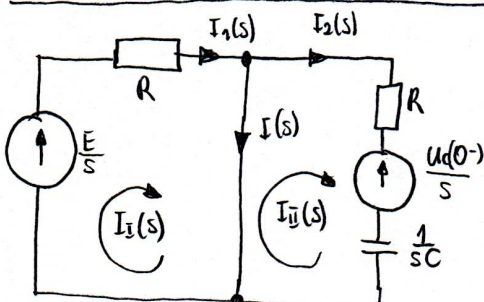

$$\begin{cases} I_I(s) \cdot R = \frac{E}{s} \\ I_{II}(s)(R + \frac{1}{sC}) = -\frac{u_C(0^-)}{s} \end{cases}$$


$$\begin{cases} I_I(s) = \frac{E}{sR} \\ I_{II}(s) = \frac{u_C(0^-)}{s(R + \frac{1}{sC})} = \frac{u_C(0^-)}{sR + \frac{1}{C}} \end{cases}$$

$$I(s) = I_I(s) - I_{II}(s) = \frac{E}{sR} + \frac{u_C(0^-)}{sR + \frac{1}{C}} = \frac{E}{sR} + \frac{E}{R(s + \frac{1}{RC})}$$

$$i(t) = \frac{E}{R} + \frac{E}{R} e^{-\frac{t}{RC}}$$


$$\frac{1}{s} \leftrightarrow \mathcal{E}(t)$$
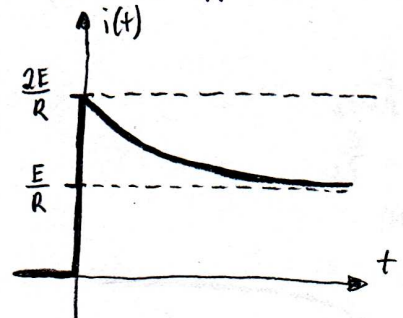
$$\frac{1}{s+a} \leftrightarrow e^{-at}$$




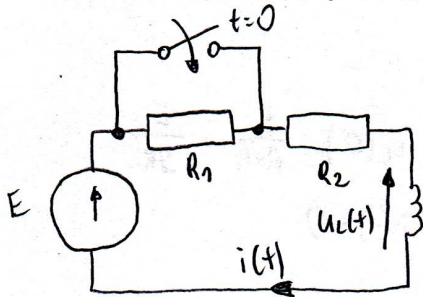**PROBLEM #4**

The circuit shown in the figure has been in a steady-state. The switch was close at  $t=0$ . Calculate and plot  $i(t)$  and  $u_L(t)$ . Use the Laplace transform.




circuit for  $t < 0$

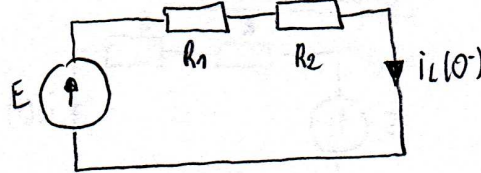

$$i_L(0^-) = \frac{E}{R_1 + R_2}$$

circuit for  $t > 0$  (s-domain circuit)

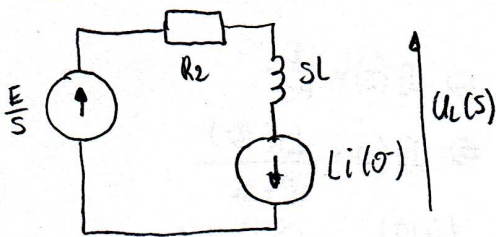

$$I(s) = \frac{\frac{E}{s} + Li(0^-)}{R_2 + sL} = \frac{E}{s(R_2 + sL)} + \frac{Li(0^-)}{R_2 + sL} = \frac{E}{s(R_2 + sL)} + \frac{Li(0^-)}{L(s + \frac{R_2}{L})}$$

$$= \frac{E}{s(R_2 + sL)} + \frac{i(0^-)}{s + \frac{R_2}{L}} = \frac{A_1}{s - s_1} + \frac{A_2}{s - s_2} + \frac{i(0^-)}{s + \frac{R_2}{L}}$$

$$s(R_2 + sL) = 0 \Rightarrow s_1 = 0, s_2 = -\frac{R_2}{L}$$

$$N(s) = E$$

$$M(s) = s(R_2 + sL) = R_2s + Ls^2$$

$$M'(s) = R_2 + 2sL$$

$$A_1 = \frac{N(s_1)}{M'(s_1)} = \frac{E}{R_2} \quad A_2 = \frac{N(s_2)}{M'(s_2)} = \frac{E}{R_2 + 2L(-\frac{R_2}{L})} = \frac{E}{R_2 - 2R_2} = -\frac{E}{R_2}$$

$$I(s) = \frac{E}{R_2s} - \frac{E}{R_2(s + \frac{R_2}{L})} + \frac{i(0^-)}{s + \frac{R_2}{L}}$$

$$i(t) = \frac{E}{R_2} - \frac{E}{R_2} e^{-\frac{R_2}{L}t} + i(0^-) e^{-\frac{R_2}{L}t} = \frac{E}{R_2} - \frac{E}{R_2} e^{-\frac{R_2}{L}t} + \frac{E}{R_1 + R_2} e^{-\frac{R_2}{L}t} = \frac{E}{R_2} - \left( \frac{E}{R_2} - \frac{E}{R_1 + R_2} \right) e^{-\frac{R_2}{L}t} =$$

$$= \frac{E}{R_2} - \left( \frac{ER_2 + ER_2 - ER_2}{(R_1 + R_2) \cdot R_2} \right) e^{-\frac{R_2}{L}t} = \frac{E}{R_2} - \frac{ER_1}{(R_1 + R_2)R_2} e^{-\frac{R_2}{L}t} = \boxed{\frac{E}{R_2} \left( 1 - \frac{R_1}{R_1 + R_2} e^{-\frac{R_2}{L}t} \right)}$$

$$u_L(t) = L \frac{di(t)}{dt} = L \frac{d}{dt} \left[ \frac{E}{R_2} - \frac{ER_1}{R_2(R_1 + R_2)} e^{-\frac{R_2}{L}t} \right] = \left[ 0 + \frac{ER_1 R_2}{R_2(R_1 + R_2)} e^{-\frac{R_2}{L}t} \right] = \boxed{\frac{ER_1}{R_1 + R_2} e^{-\frac{R_2}{L}t}}$$

$$i(t=0) = \frac{E}{R_1 + R_2}$$

$$i(t \rightarrow \infty) = \frac{E}{R_2}$$

$$u_L(t=0) = \frac{ER_1}{R_1 + R_2}$$

$$u_L(t \rightarrow \infty) = 0$$

$$u_L(t < 0) = 0$$

